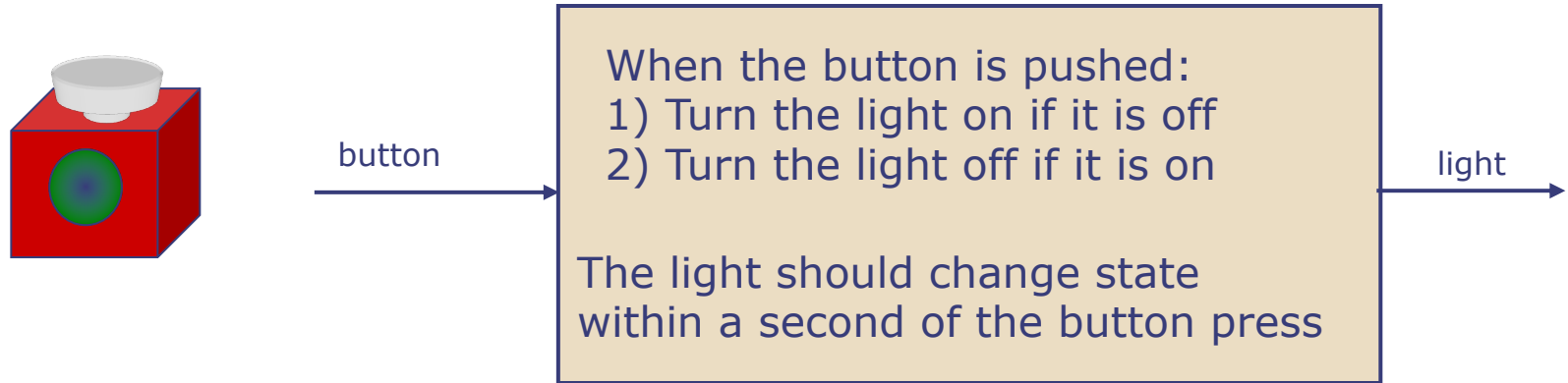


Sequential Circuits

Circuits with state


Something We Cannot Build (Yet)

What if you were given the following design specification:




Something We Cannot Build (Yet)

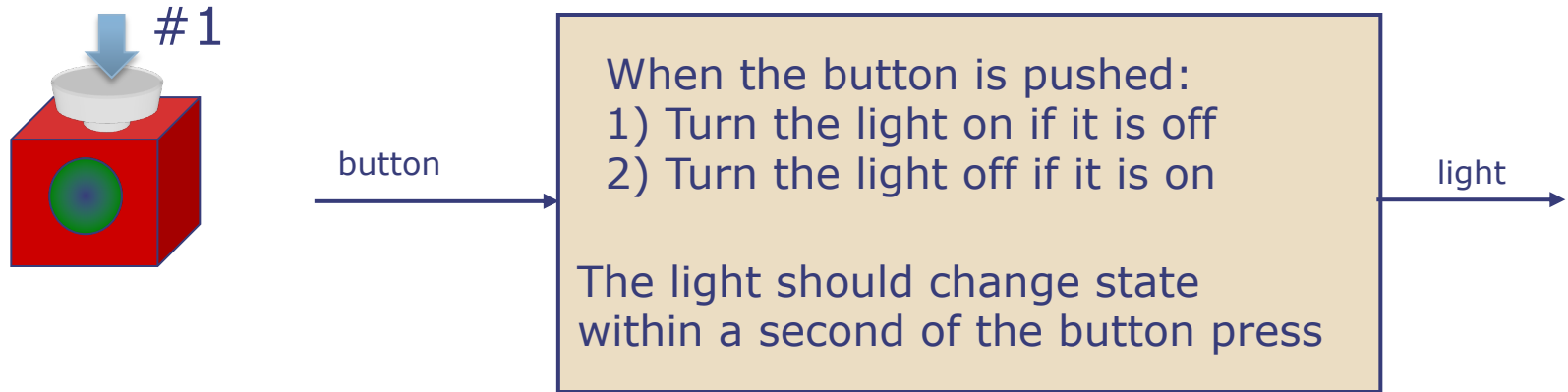What if you were given the following design specification:




Something We Cannot Build (Yet)

 What if you were given the following design specification:




Something We Cannot Build (Yet)

 What if you were given the following design specification:




Something We Cannot Build (Yet)

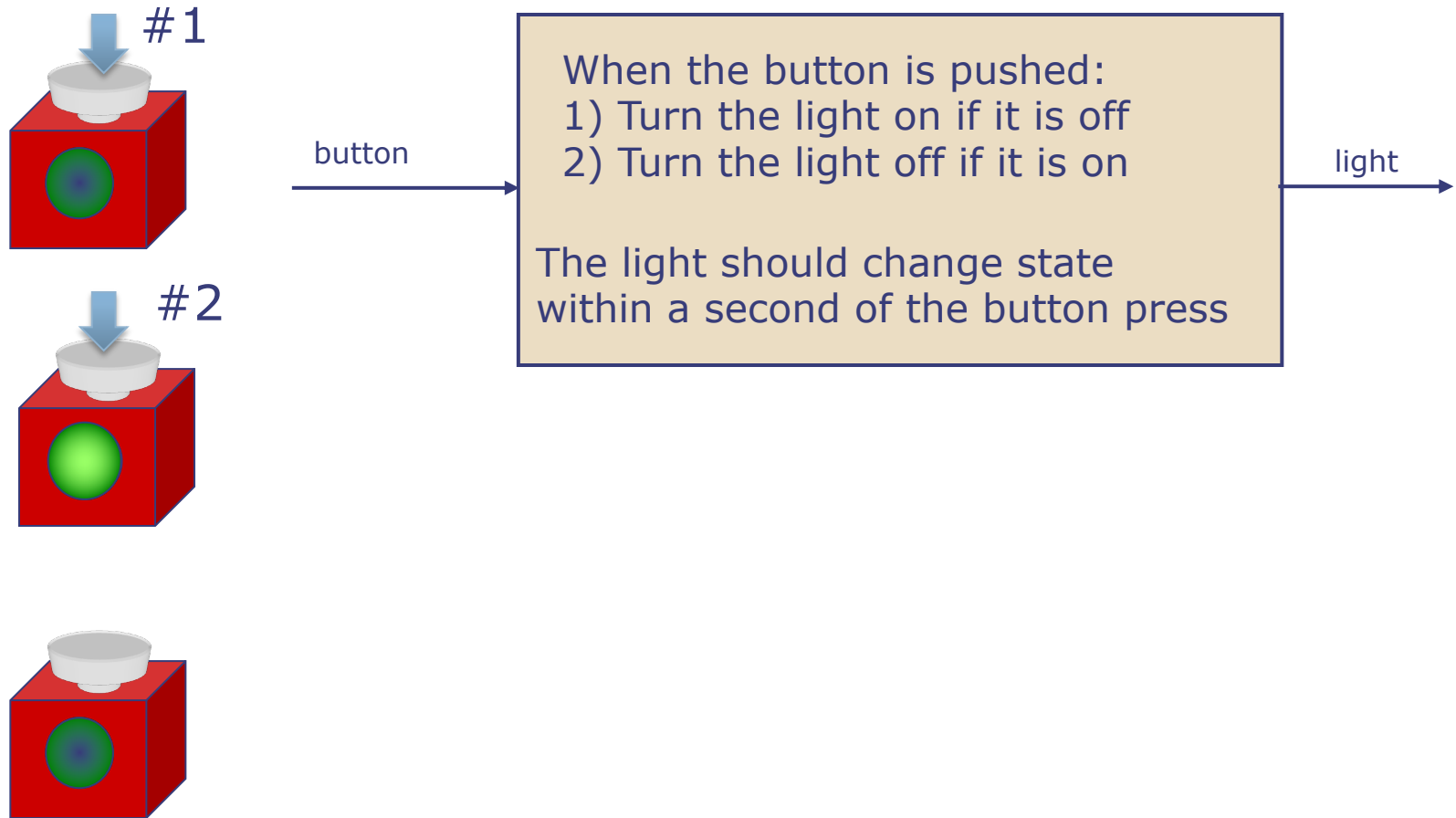What if you were given the following design specification:



Something We Cannot Build (Yet)

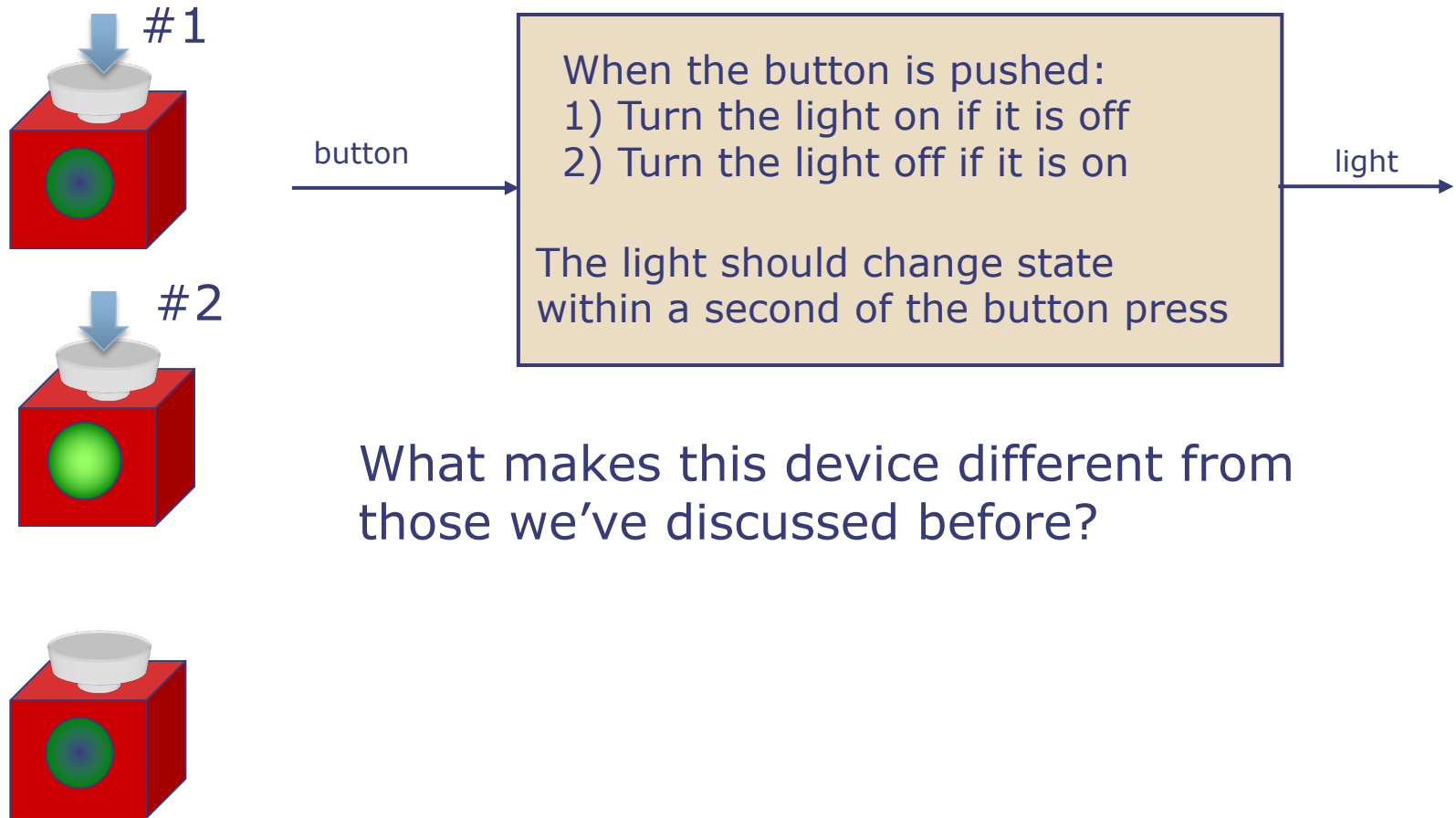
What if you were given the following design specification:



What makes this device different from those we've discussed before?

Something We Cannot Build (Yet)

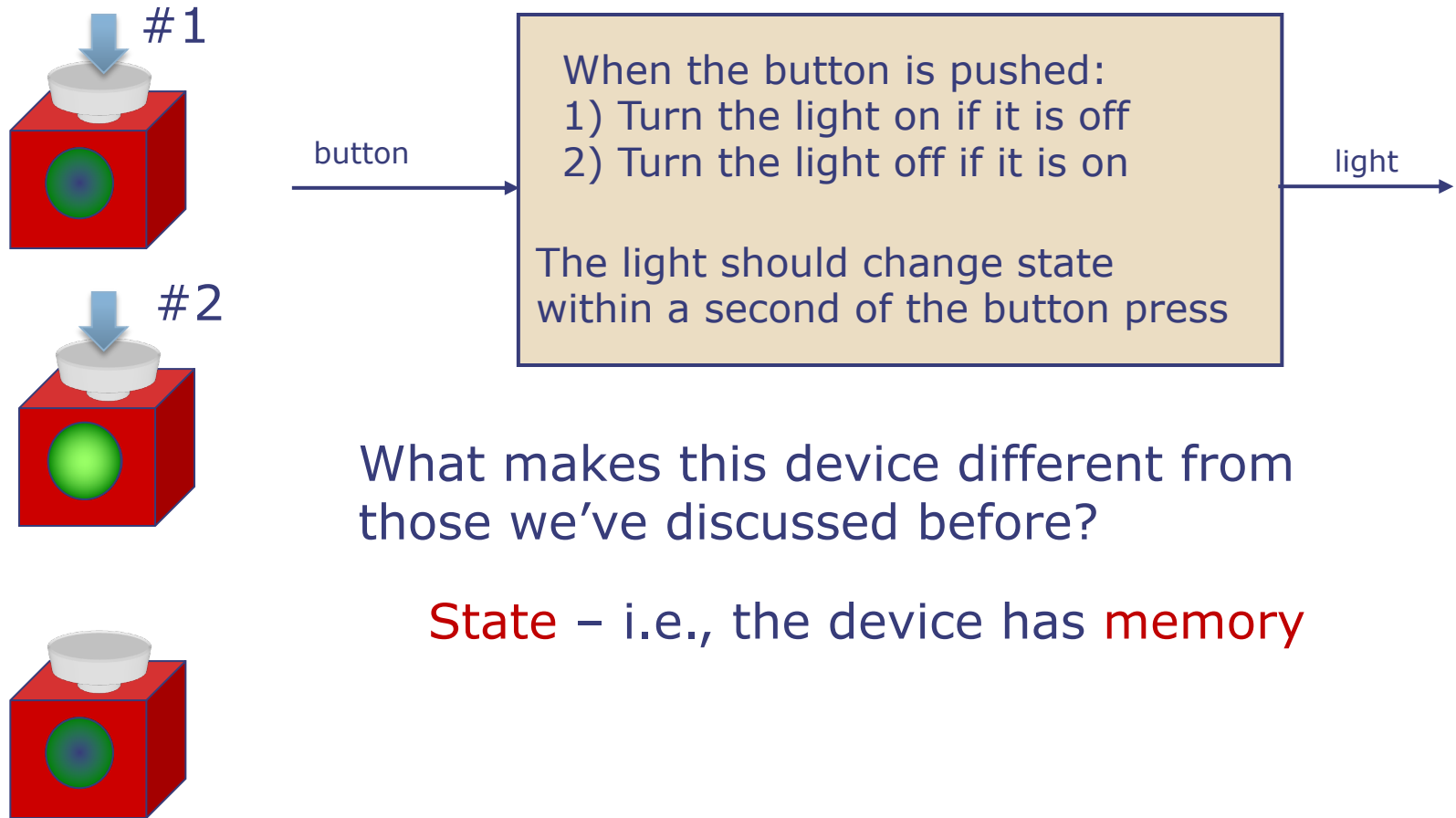
What if you were given the following design specification:



What makes this device different from those we've discussed before?


State – i.e., the device has **memory**

Sequential Circuits

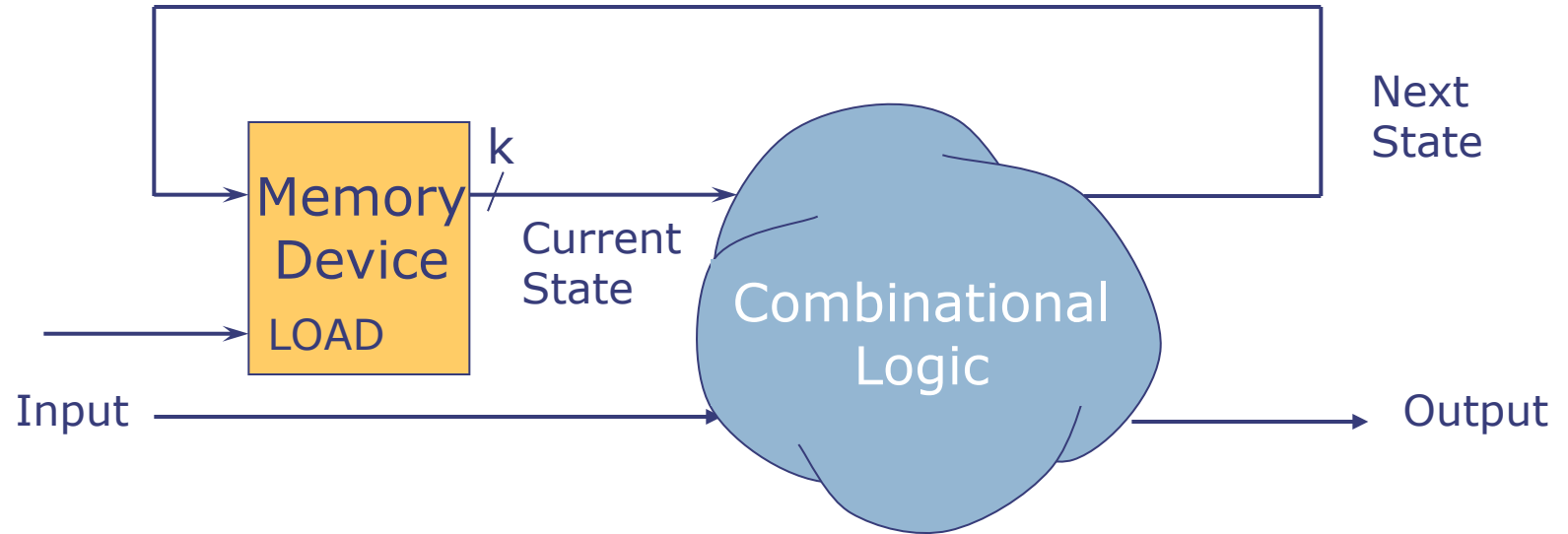

Sequential circuits contain digital memory and combinational logic


Sequential Circuits

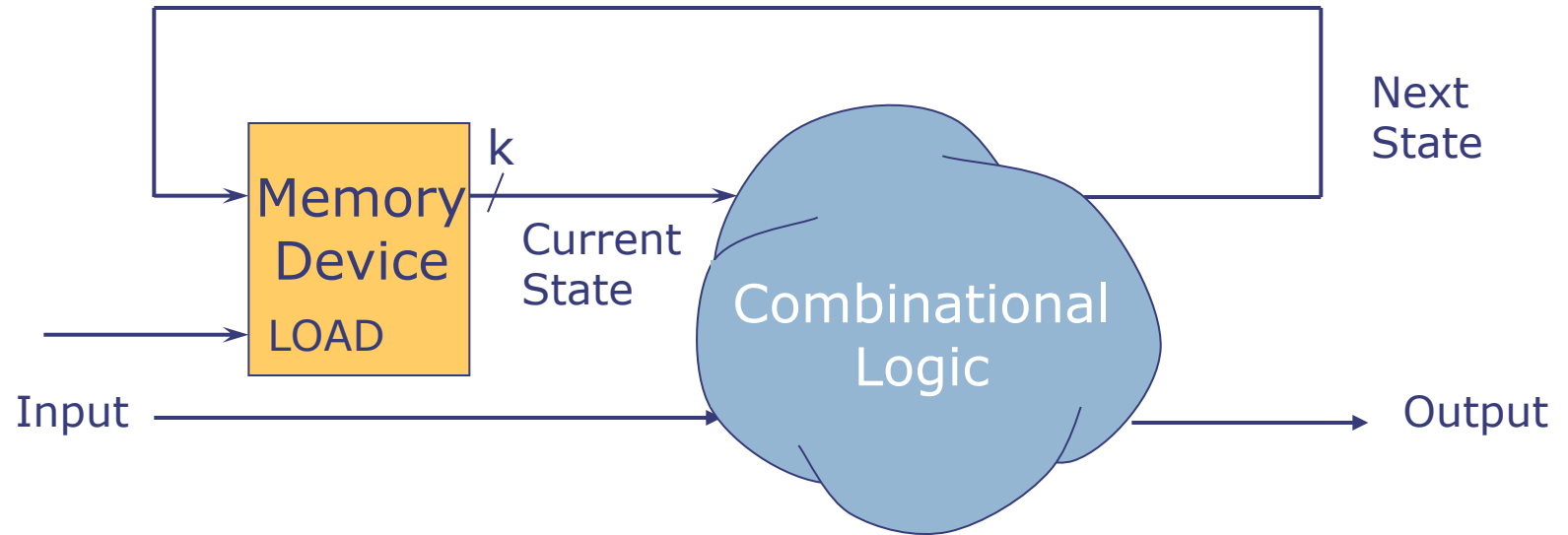

Sequential circuits contain digital memory and combinational logic

- Memory stores **current state**


Sequential Circuits

 

Sequential circuits contain digital memory and combinational logic

- Memory stores **current state**
- Combinational logic computes:


Sequential Circuits

 

Sequential circuits contain digital memory and combinational logic

- Memory stores **current state**
- Combinational logic computes:
 - **Next state** (from input + current state)


Sequential Circuits

 

Sequential circuits contain digital memory and combinational logic

- Memory stores **current state**
- Combinational logic computes:
 - **Next state** (from input + current state)
 - **Output** bits (from input + current state)


Sequential Circuits

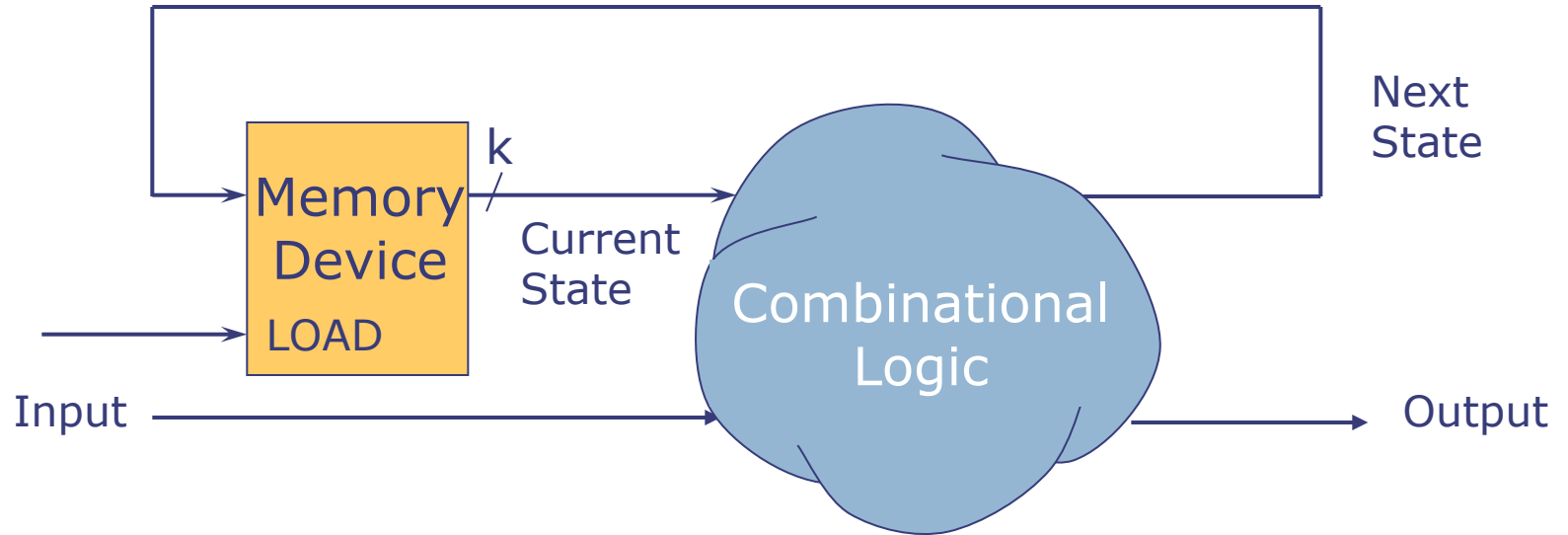

Sequential circuits contain digital memory and combinational logic

- Memory stores **current state**
- Combinational logic computes:
 - **Next state** (from input + current state)
 - **Output** bits (from input + current state)
- State changes on LOAD control input


Sequential Circuits

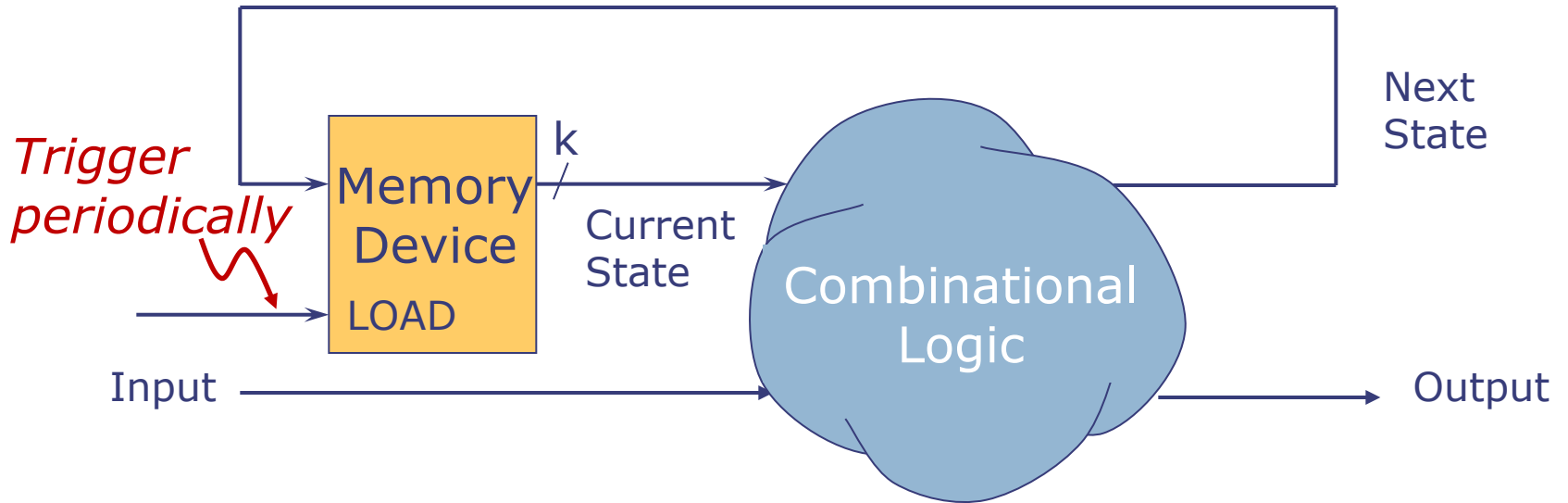

Sequential circuits contain digital memory and combinational logic

- Memory stores **current state**
- Combinational logic computes:
 - **Next state** (from input + current state)
 - **Output** bits (from input + current state)
- State changes on LOAD control input


Sequential Circuits

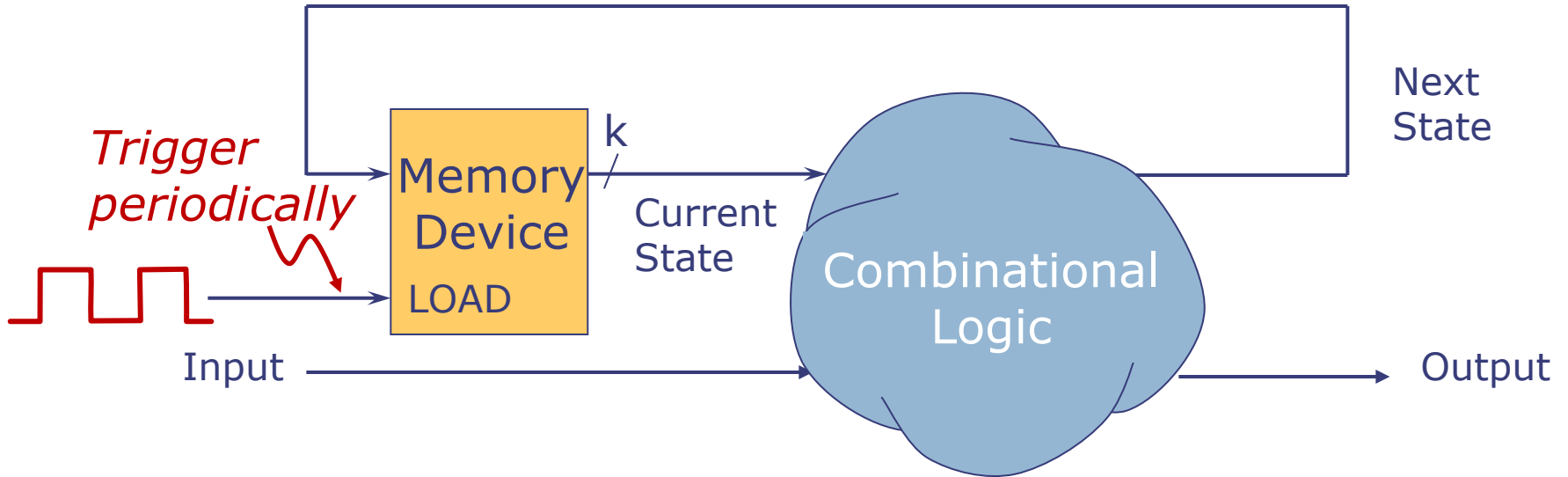

Sequential circuits contain digital memory and combinational logic

- Memory stores **current state**
- Combinational logic computes:
 - **Next state** (from input + current state)
 - **Output** bits (from input + current state)
- State changes on LOAD control input


Sequential Circuits

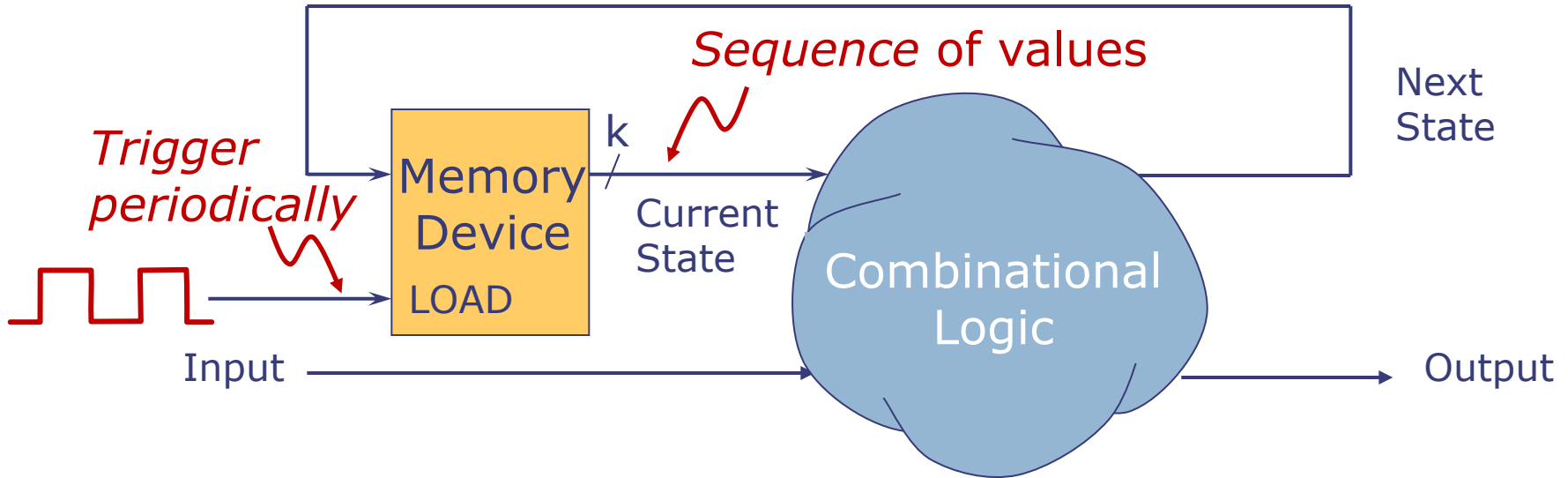

Sequential circuits contain digital memory and combinational logic

- Memory stores **current state**
- Combinational logic computes:
 - **Next state** (from input + current state)
 - **Output** bits (from input + current state)
- State changes on LOAD control input

Sequential Circuits

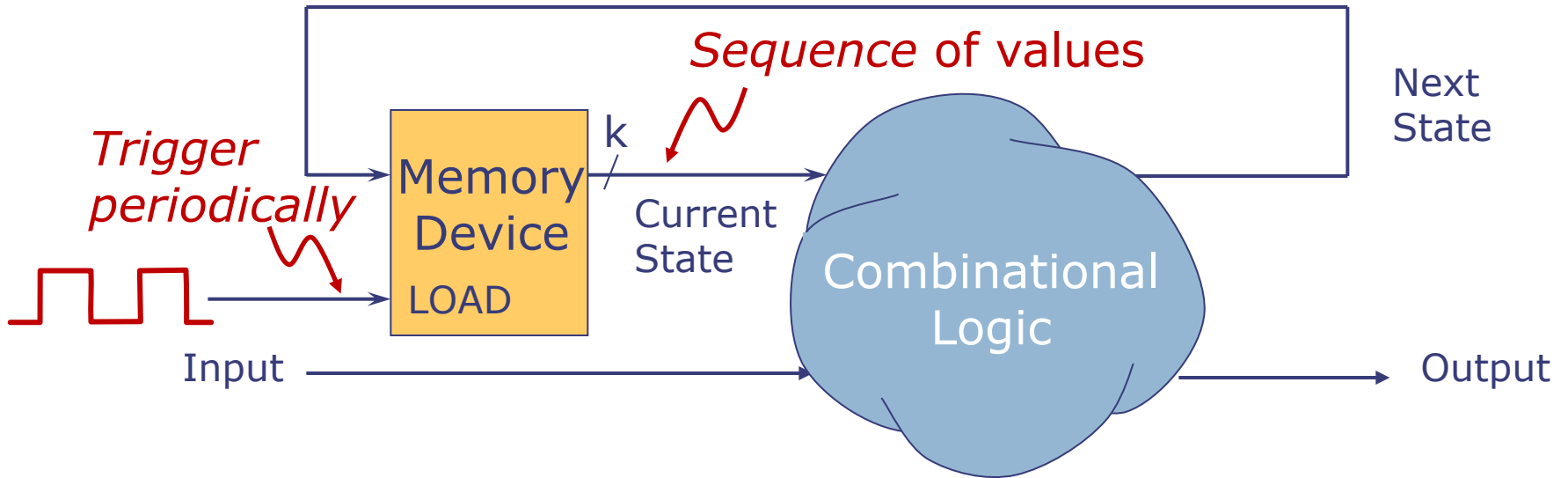


Sequential circuits contain digital memory and combinational logic

- Memory stores **current state**
- Combinational logic computes:
 - **Next state** (from input + current state)
 - **Output** bits (from input + current state)
- State changes on LOAD control input

Need
loadable
memory


Memory: Using Feedback

 Idea: use **feedback** to maintain storage indefinitely.




Memory: Using Feedback

 Idea: use **feedback** to maintain storage indefinitely.




Memory: Using Feedback

 Idea: use **feedback** to maintain storage indefinitely.




Memory: Using Feedback

 Idea: use **feedback** to maintain storage indefinitely.




Memory: Using Feedback

 Idea: use **feedback** to maintain storage indefinitely.




Memory: Using Feedback

 Idea: use **feedback** to maintain storage indefinitely.
Our logic gates are built to restore marginal signal levels, so noise shouldn't be a problem!



Memory: Using Feedback

 
Idea: use **feedback** to maintain storage indefinitely.
Our logic gates are built to restore marginal signal levels, so noise shouldn't be a problem!




Result: a **bistable**
storage element

Memory: Using Feedback

 Idea: use **feedback** to maintain storage indefinitely.
Our logic gates are built to restore marginal signal levels, so noise shouldn't be a problem!




Result: a **bistable** storage element

 


Memory: Using Feedback

 Idea: use **feedback** to maintain storage indefinitely.
Our logic gates are built to restore marginal signal levels, so noise shouldn't be a problem!




Result: a **bistable** storage element

 


Memory: Using Feedback

 Idea: use **feedback** to maintain storage indefinitely.
Our logic gates are built to restore marginal signal levels, so noise shouldn't be a problem!



Result: a **bistable** storage element

 

Not affected by noise


Three solutions:

- two end-points are **stable**
- middle point is metastable

We'll get back to this!


D Latch

A simple circuit that can hold state

 


D Latch

A simple circuit that can hold state

 

D Latch


A simple circuit that can hold state

 

if $C=1$, the value of Q *holds*

D Latch

A simple circuit that can hold state

 


if $C=1$, the value of Q *holds*

if $C=0$, the value of D *passes* to Q


D Latch

A simple circuit that can hold state

 



if $C=1$, the value of Q *holds*

if $C=0$, the value of D *passes* to Q

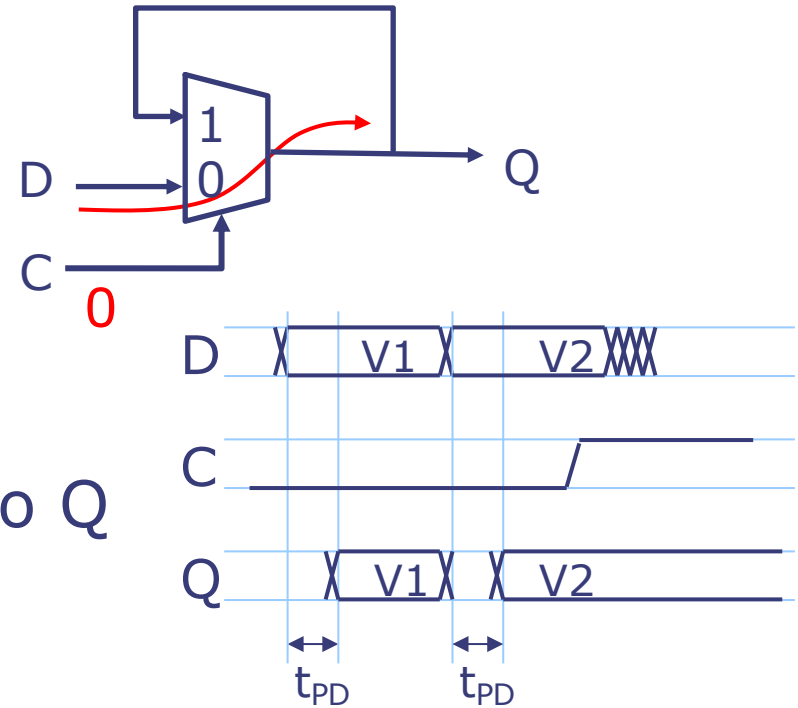


D Latch

A simple circuit that can hold state

  


if $C=1$, the value of Q *holds*

if $C=0$, the value of D *passes* to Q

 

D Latch


A simple circuit that can hold state

 

if $C=1$, the value of Q *holds*
if $C=0$, the value of D *passes* to Q




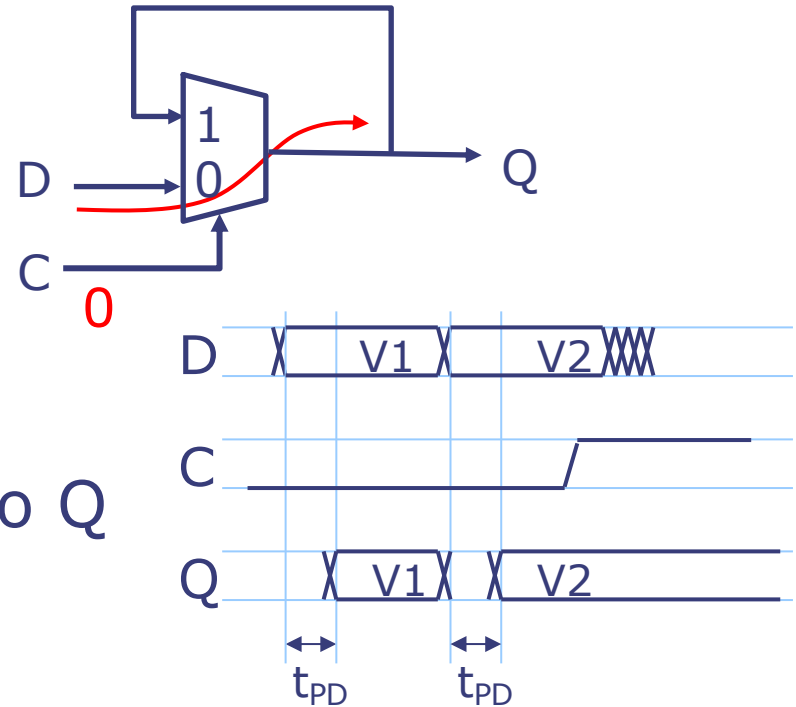
Q^{t-1} represents the value previously held in DL;
 Q^t represents the current value.



C	D	Q^{t-1}	Q^t
0	0	X	0
0	1	X	1
1	X	0	0
1	X	1	1

D Latch

A simple circuit that can hold state

  


if $C=1$, the value of Q *holds*

if $C=0$, the value of D *passes* to Q



Q^{t-1} represents the value previously held in DL;

Q^t represents the current value.

 


C	D	Q^{t-1}	Q^t
0	0	X	0
0	1	X	1
1	X	0	0
1	X	1	1

} pass

D Latch

A simple circuit that can hold state

 


if $C=1$, the value of Q *holds*

if $C=0$, the value of D *passes* to Q



Q^{t-1} represents the value previously held in DL;


Q^t represents the current value.

 

C	D	Q^{t-1}	Q^t	
0	0	X	0	pass
0	1	X	1	
1	X	0	0	hold
1	X	1	1	


Sequential circuits using D latches?

A terrible idea

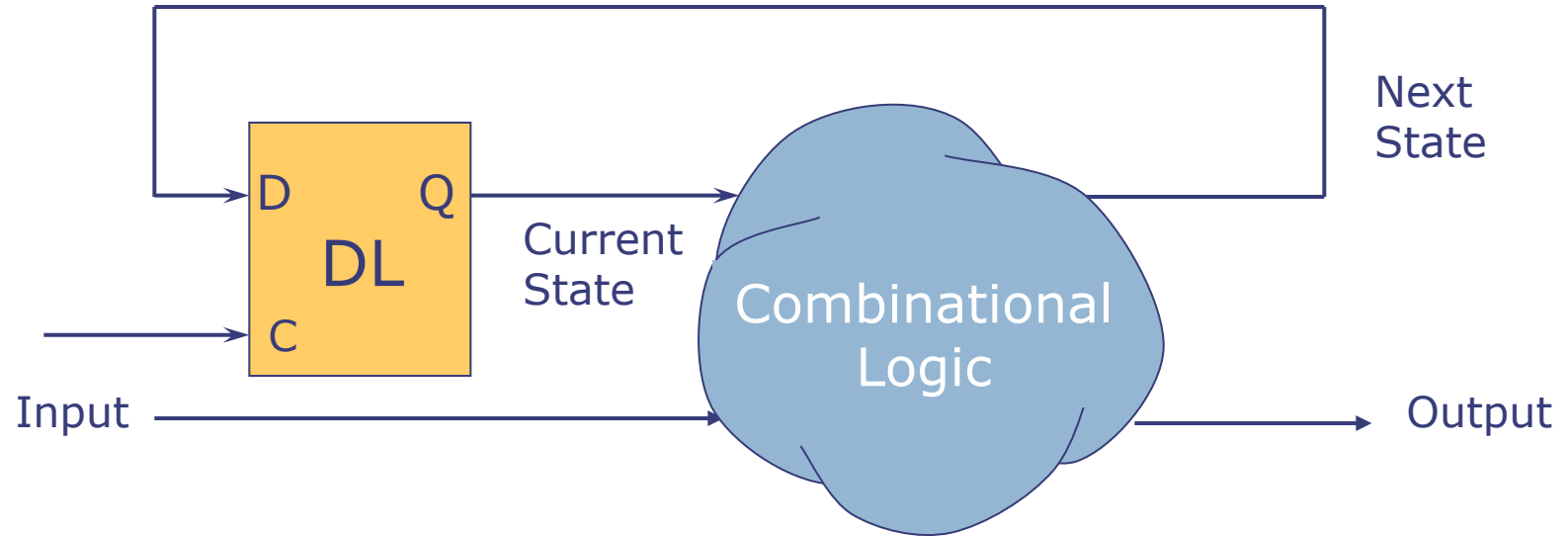


Sequential circuits using D latches?

A terrible idea

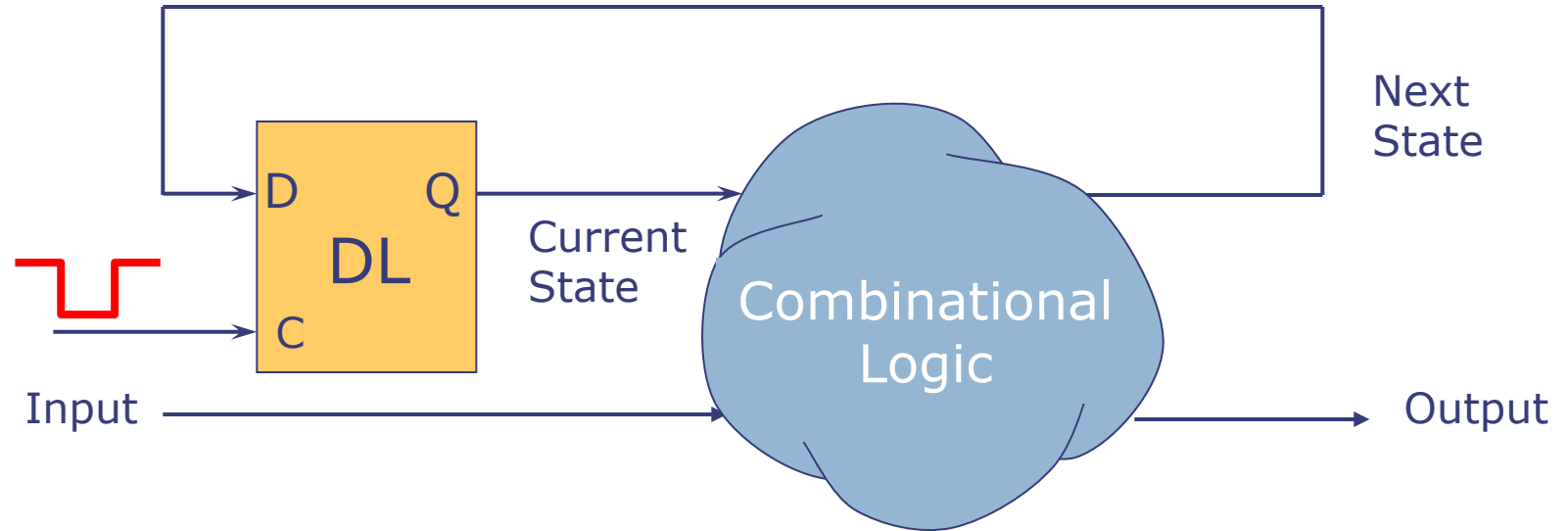


Sequential circuits using D latches?

A terrible idea

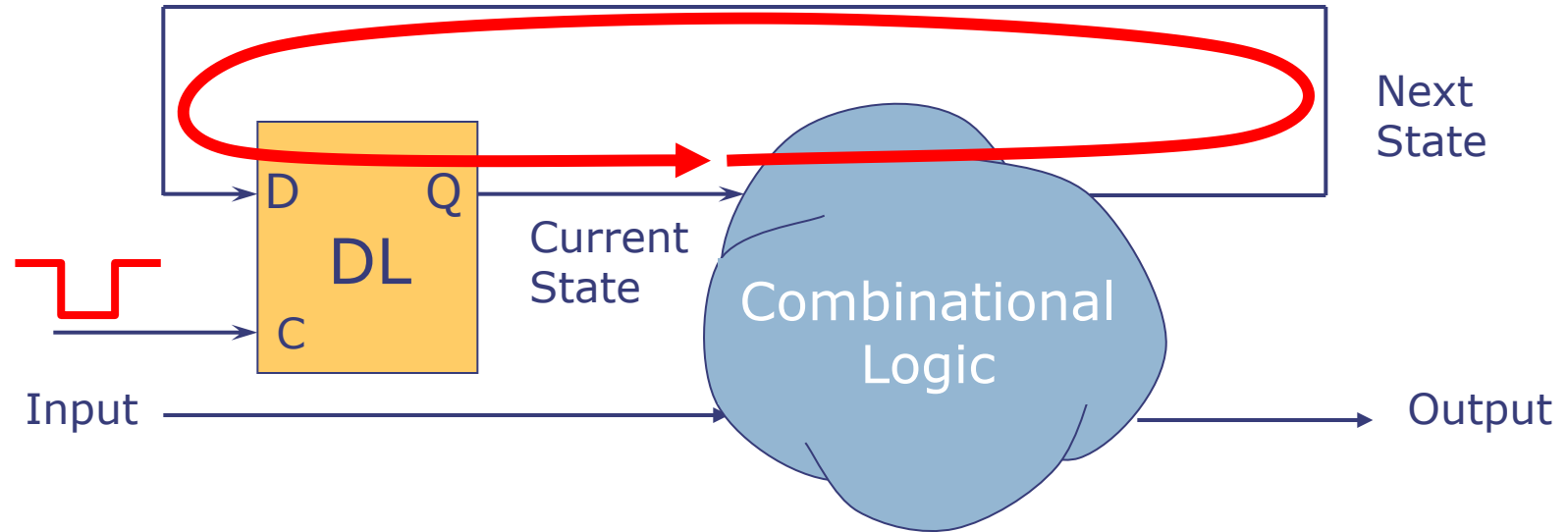

Sequential circuits using D latches?


A terrible idea

 

- When $C=0$, D latch passes input to output...
 - Creates a cycle from Q to D!
 - Our combinational logic stops being combinational ☹️

Sequential circuits using D latches?


A terrible idea

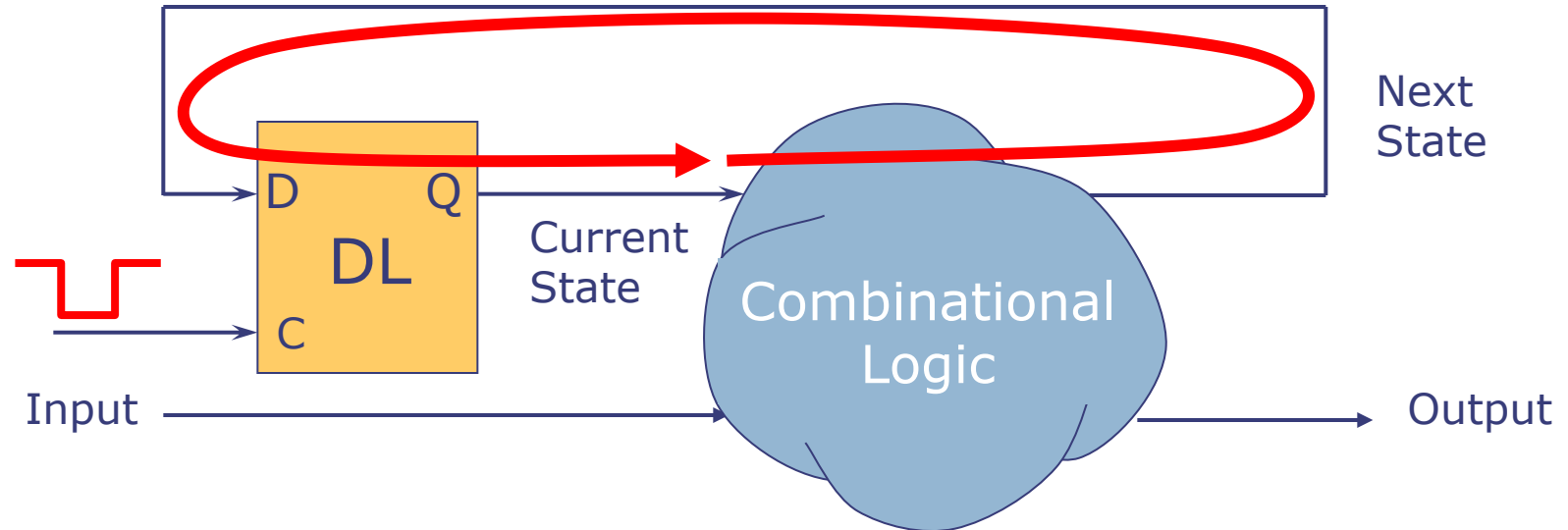

- When $C=0$, D latch passes input to output...
 - Creates a cycle from Q to D!
 - Our combinational logic stops being combinational ☹
- In practice, very hard to get right: Needs tricky timing constraints on $C=0$ pulse + comb logic

Sequential circuits using D latches?

A terrible idea

 


- When $C=0$, D latch passes input to output...
 - Creates a cycle from Q to D!
 - Our combinational logic stops being combinational ☹
- In practice, very hard to get right: Needs tricky timing constraints on $C=0$ pulse + comb logic

Memory should sample an *instant*, not an *interval*


A Similar Problem...

Gate closed

 


A Similar Problem...

Gate closed

 


Gate open

 


A Similar Problem...

Gate closed

 


Gate open

 

Sequence
of values


A Similar Problem...

Gate closed

 


Sequence
of values

Gate open

 


*How can we ensure
only one car gets
through?*

Solution: Use two gates!

 

Gate 1: open
Gate 2: closed


Solution: Use two gates!

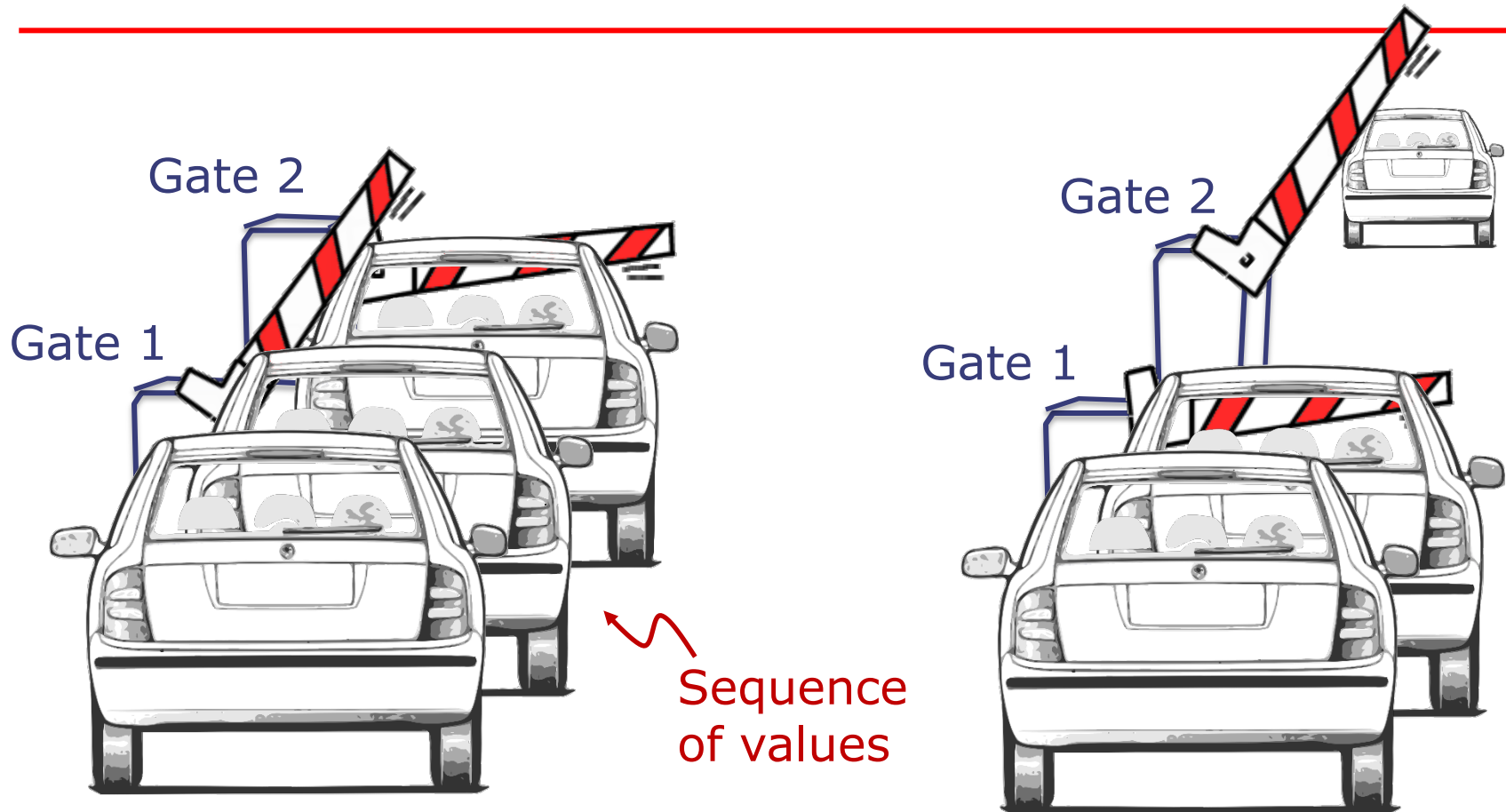

Gate 1: open
Gate 2: closed


Gate 1: closed
Gate 2: open

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D , but Q holds its old value

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D, but Q holds its old value

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D , but Q holds its old value
 - $C = 1$: Q^{int} holds its old value, but Q follows Q^{int}

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D, but Q holds its old value
 - $C = 1$: Q^{int} holds its old value, but Q follows Q^{int}
 - Q doesn't change when $C=0$ or $C=1$

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D, but Q holds its old value
 - $C = 1$: Q^{int} holds its old value, but Q follows Q^{int}
 - Q doesn't change when $C=0$ or $C=1$
 - It changes when **C transitions from 0 to 1 (a *rising-edge* of C)**

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D, but Q holds its old value
 - $C = 1$: Q^{int} holds its old value, but Q follows Q^{int}
 - Q doesn't change when $C=0$ or $C=1$
 - It changes when **C transitions from 0 to 1 (a *rising-edge* of C)**

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D, but Q holds its old value
 - $C = 1$: Q^{int} holds its old value, but Q follows Q^{int}
 - Q doesn't change when $C=0$ or $C=1$
 - It changes when **C transitions from 0 to 1 (a *rising-edge* of C)**

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D , but Q holds its old value
 - $C = 1$: Q^{int} holds its old value, but Q follows Q^{int}
 - Q doesn't change when $C=0$ or $C=1$
 - It changes when C transitions from 0 to 1 (a *rising-edge* of C)

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D, but Q holds its old value
 - $C = 1$: Q^{int} holds its old value, but Q follows Q^{int}
 - Q doesn't change when $C=0$ or $C=1$
 - It changes when **C transitions from 0 to 1 (a *rising-edge* of C)**

D Flip-Flop

 

- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D, but Q holds its old value
 - $C = 1$: Q^{int} holds its old value, but Q follows Q^{int}
 - Q doesn't change when $C=0$ or $C=1$
 - It changes when **C transitions from 0 to 1 (a *rising-edge* of C)**

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D, but Q holds its old value
 - $C = 1$: Q^{int} holds its old value, but Q follows Q^{int}
 - Q doesn't change when $C=0$ or $C=1$
 - It changes when **C transitions from 0 to 1 (a rising-edge of C)**

What happens on a falling edge ($C: 1 \rightarrow 0$)?


D Flip-Flop

An edge-triggered storage element

 


D Flip-Flop

An edge-triggered storage element

 


D Flip-Flop

An edge-triggered storage element

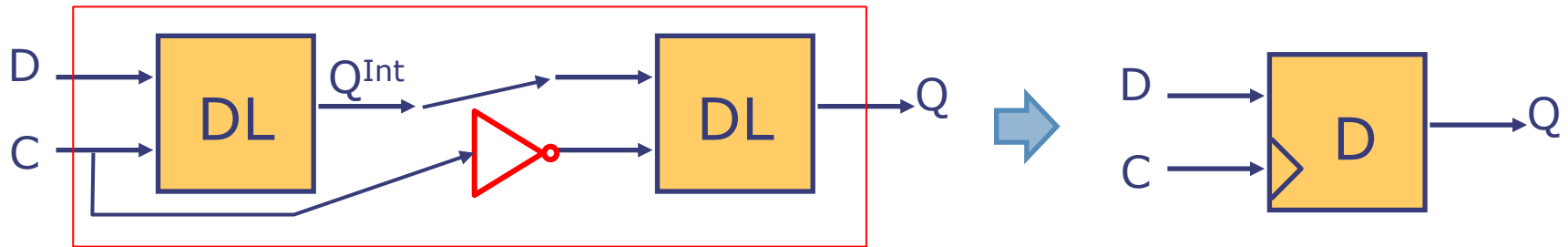


 C changes periodically (a *Clock* signal)




D Flip-Flop

An *edge-triggered* storage element

 


 C changes periodically (a *Clock* signal)




D Flip-Flop

An edge-triggered storage element

 

 
C changes periodically (a *Clock* signal)




*Data is sampled at the rising edge of the clock and must be **stable** at that time*

D Flip-Flop

An edge-triggered storage element

 

 
C changes periodically (a *Clock* signal)




*Data is sampled at the rising edge of the clock and must be **stable** at that time*

D Flip-Flop

An edge-triggered storage element

 

 
C changes periodically (a *Clock* signal)




*Data is sampled at the rising edge of the clock and must be **stable** at that time*

D Flip-Flop

An edge-triggered storage element

 

 
C changes periodically (a *Clock* signal)




*Data is sampled at the rising edge of the clock
and must be **stable** at that time*

D Flip-Flop

An edge-triggered storage element

 

 
C changes periodically (a *Clock* signal)




*Data is sampled at the rising edge of the clock and must be **stable** at that time*

D Flip-Flop

An edge-triggered storage element


 


 C changes periodically (a *Clock* signal)





*Data is sampled at the rising edge of the clock and must be **stable** at that time*

D Flip-Flop Timing

  



- Flip-flop input D should not change around the rising edge of the clock to avoid *metastability*

D Flip-Flop Timing

  



- Flip-flop input D should not change around the rising edge of the clock to avoid *metastability*
- Formally, D should be a stable and valid digital value:

D Flip-Flop Timing

  



- Flip-flop input D should not change around the rising edge of the clock to avoid *metastability*
- Formally, D should be a stable and valid digital value:
 - For at least t_{SETUP} before the rising edge of the clock

D Flip-Flop Timing

  



- Flip-flop input D should not change around the rising edge of the clock to avoid *metastability*
- Formally, D should be a stable and valid digital value:
 - For at least t_{SETUP} before the rising edge of the clock
 - For at least t_{HOLD} after the rising edge of the clock

D Flip-Flop Timing

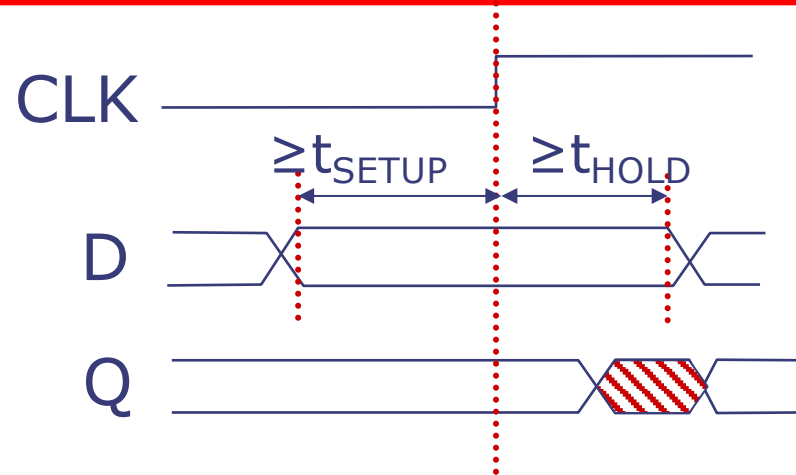 


- Flip-flop input D should not change around the rising edge of the clock to avoid *metastability*
- Formally, D should be a stable and valid digital value:
 - For at least t_{SETUP} before the rising edge of the clock
 - For at least t_{HOLD} after the rising edge of the clock

D Flip-Flop Timing

  


- Flip-flop input D should not change around the rising edge of the clock to avoid *metastability*
- Formally, D should be a stable and valid digital value:
 - For at least t_{SETUP} before the rising edge of the clock
 - For at least t_{HOLD} after the rising edge of the clock
- Flip-flop propagation delay t_{PD} is measured from **rising edge of the clock** to **valid output** (CLK→Q)


Sequential Circuits using D Flip-Flops

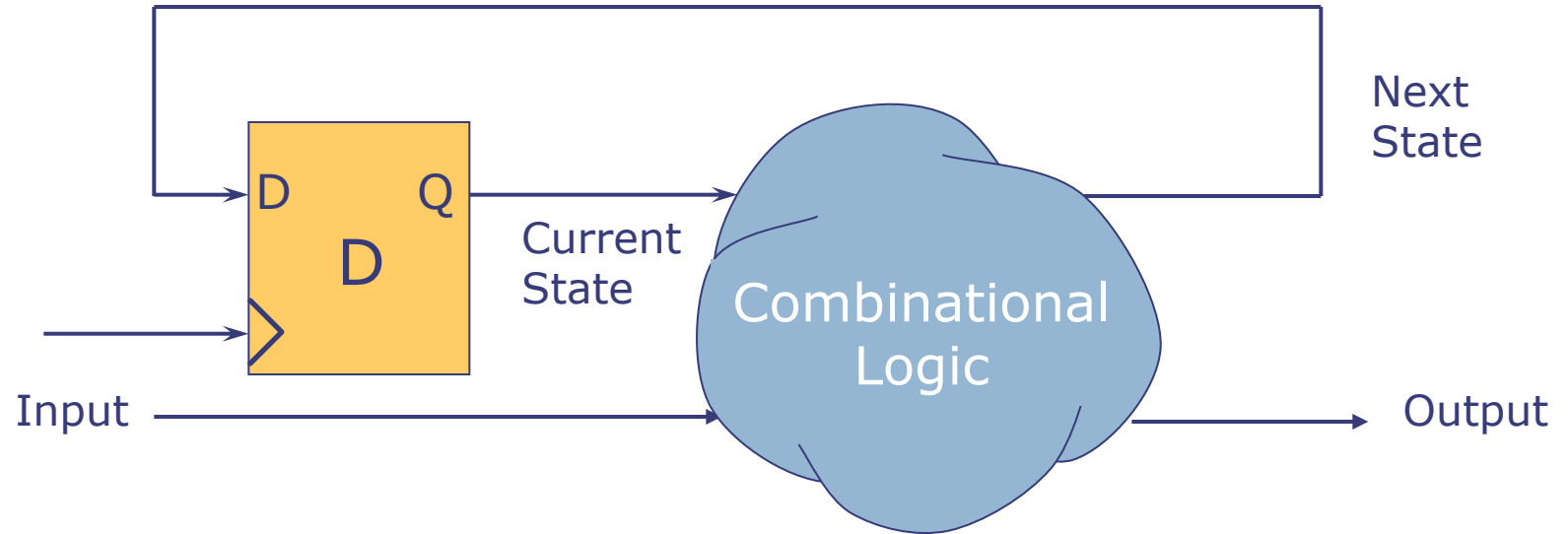

Sequential Circuits using D Flip-Flops

 


Sequential Circuits using D Flip-Flops

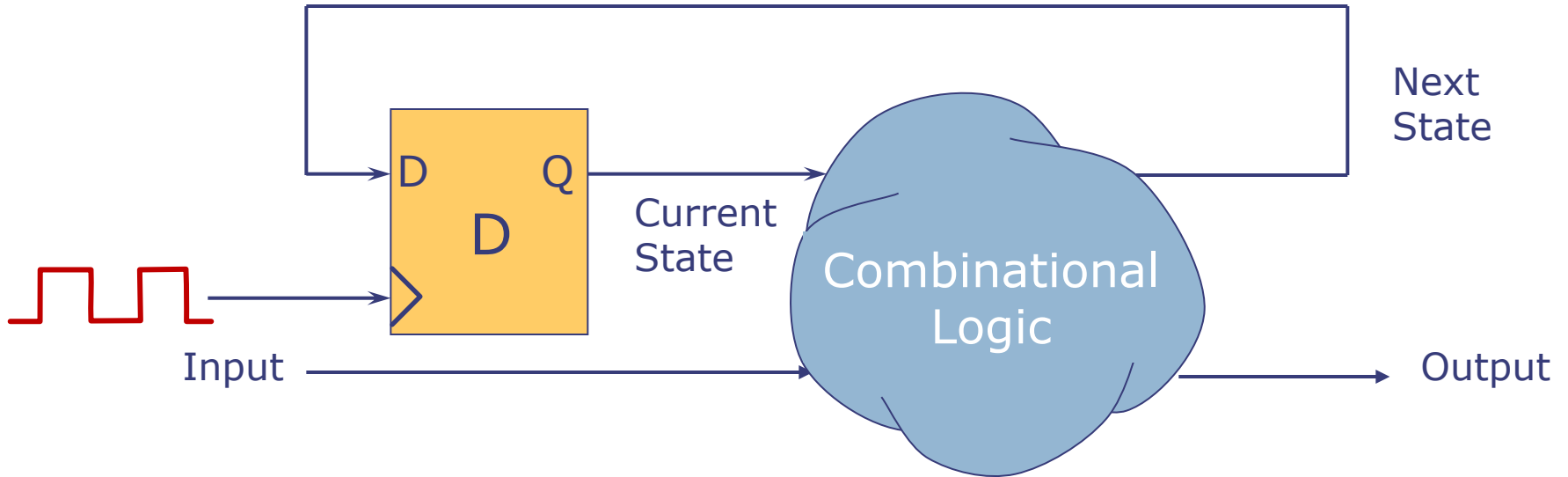



- There is never a combinational cycle between D and Q!

Sequential Circuits using D Flip-Flops

 


- There is never a combinational cycle between D and Q!
- Works correctly, as long as we meet t_{SETUP} and t_{HOLD}
 - More on this later

D Flip-Flop with Write Enable

  


Data is captured
only if EN is on

D Flip-Flop with Write Enable

 


Data is captured
only if EN is on

D Flip-Flop with Write Enable

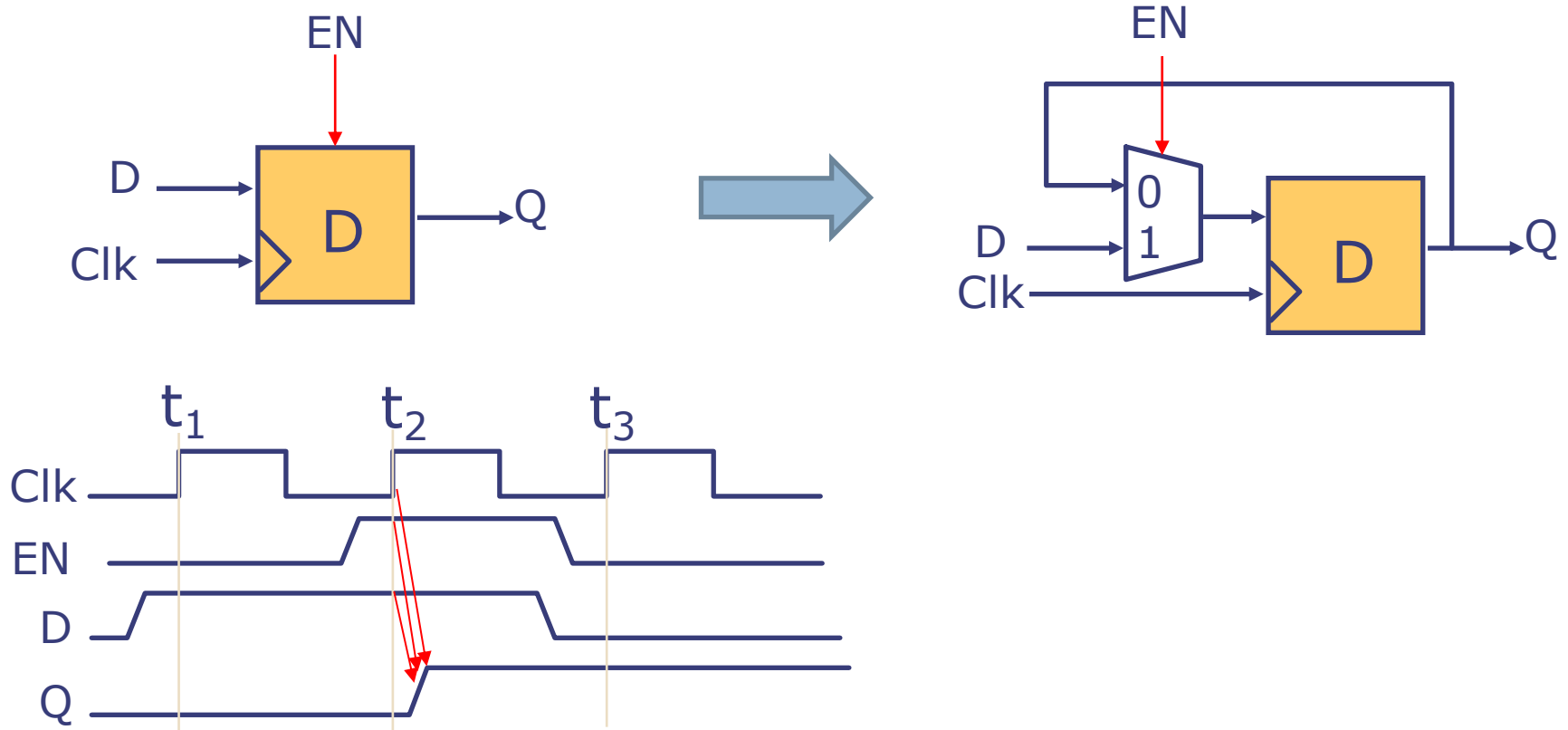


Data is captured
only if EN is on

D Flip-Flop with Write Enable

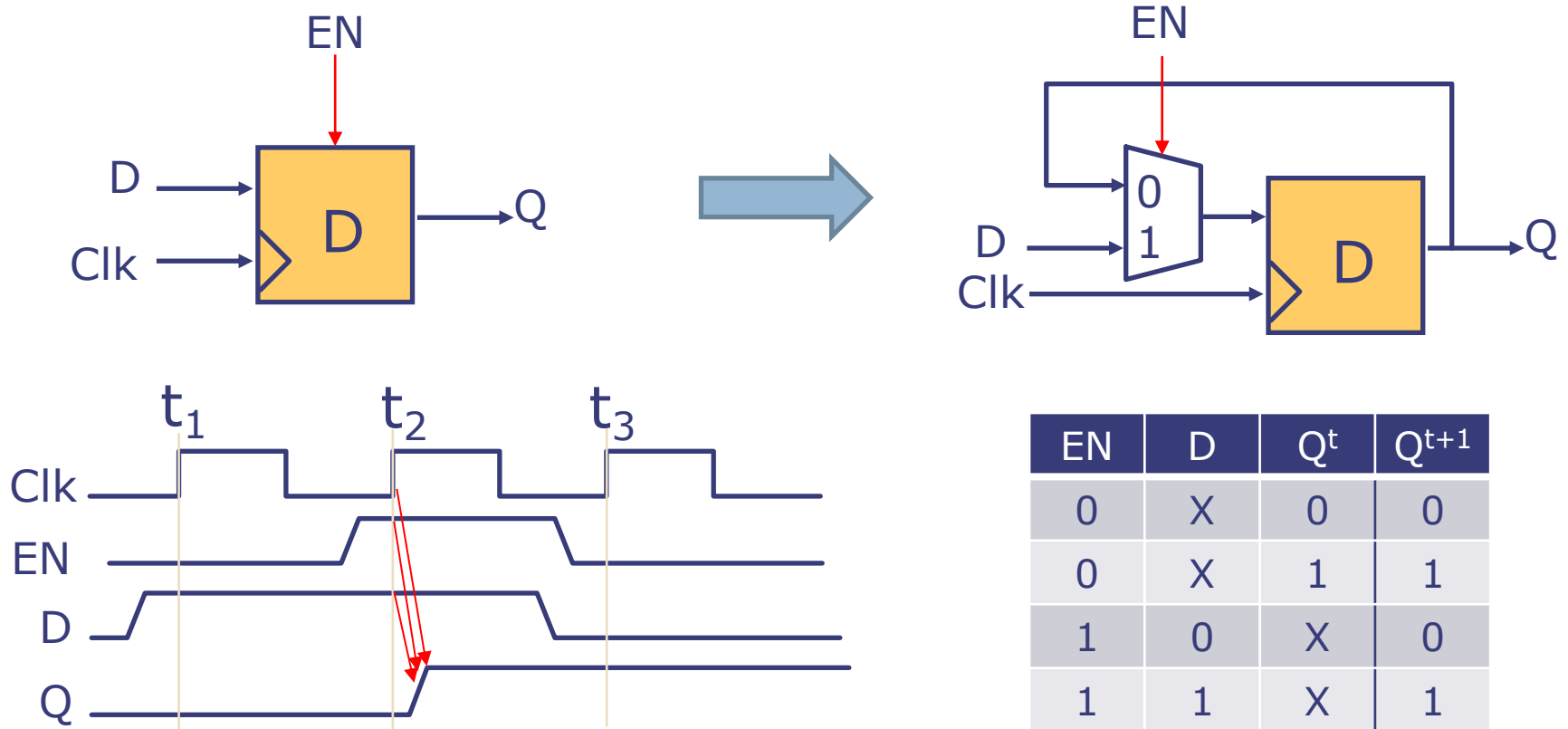

Data is captured
only if EN is on


D Flip-Flop with Write Enable

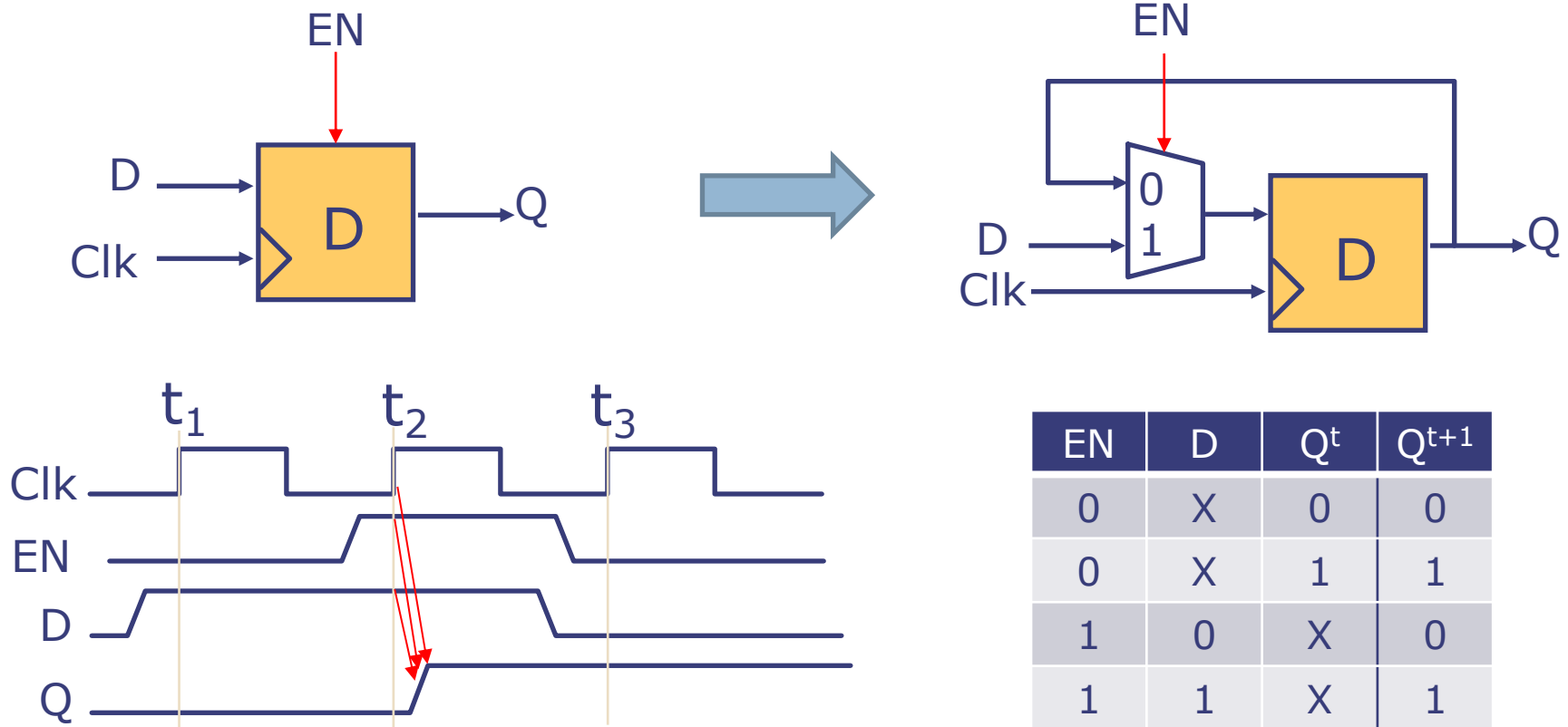

Data is captured
only if EN is on

Transitions happen at
rising edge of the clock
No need to specify the
clock explicitly




D Flip-Flop with Write Enable

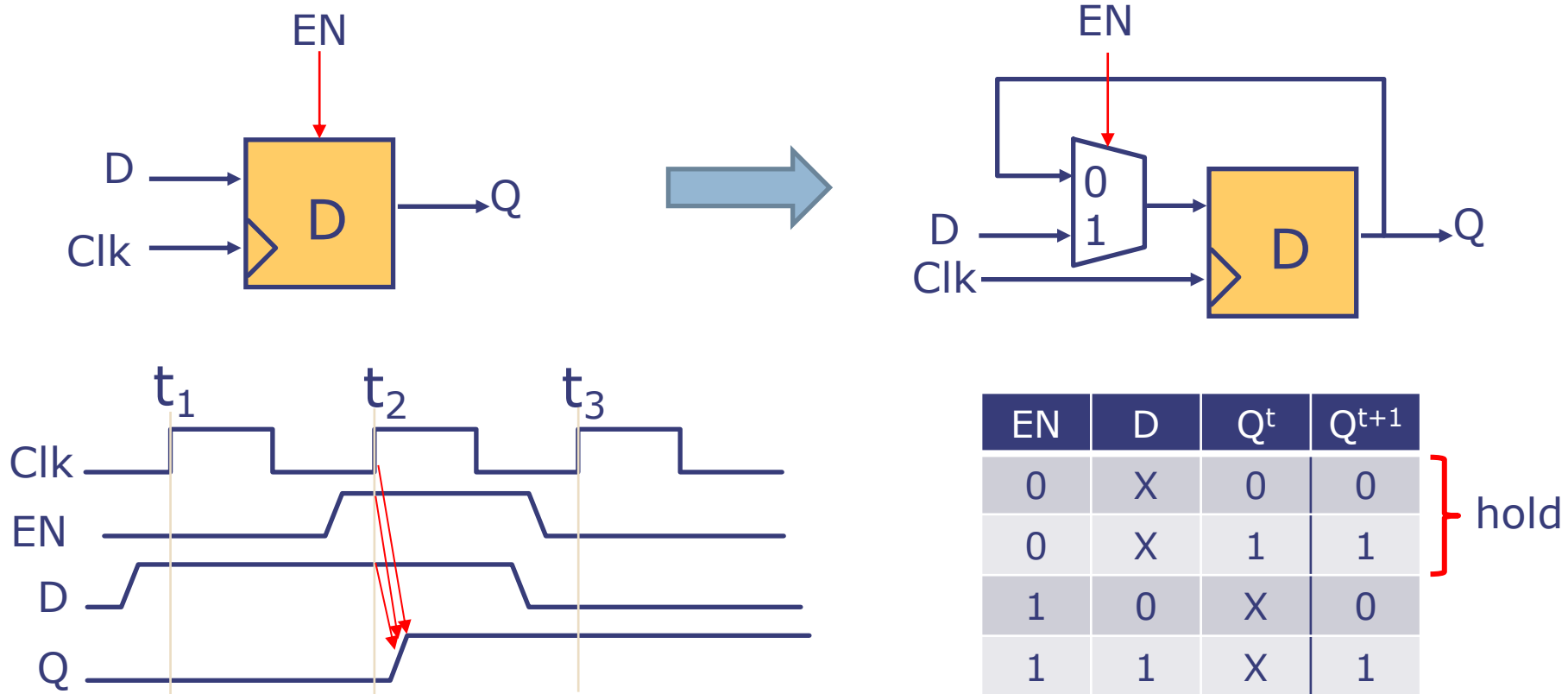

Data is captured
only if EN is on

Transitions happen at
rising edge of the clock
No need to specify the
clock explicitly

D Flip-Flop with Write Enable

   


EN	D	Q^t	Q^{t+1}	
0	X	0	0	hold
0	X	1	1	
1	0	X	0	copy input
1	1	X	1	



Data is captured
only if EN is on

Transitions happen at
rising edge of the clock
No need to specify the
clock explicitly


How Are Flip-Flops Initialized?

 

How Are Flip-Flops Initialized?

  

How Are Flip-Flops Initialized?

 


- When $\text{Reset} = 1$, flip flop is set to initial value regardless of value of EN
- When $\text{Reset} = 0$, then it behaves like a D flip-flop with enable

Using D Flip-Flops to Build Sequential Circuits



Synchronous Sequential Circuits

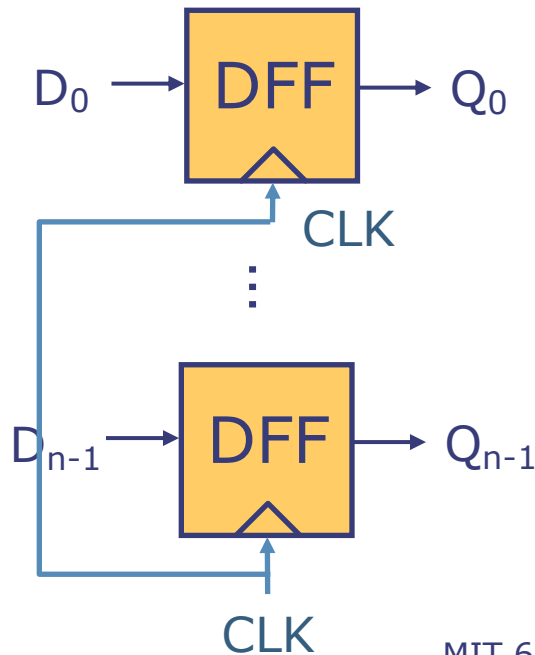- All the D Flip-Flops use the same periodic clock signal.





Synchronous Sequential Circuits

 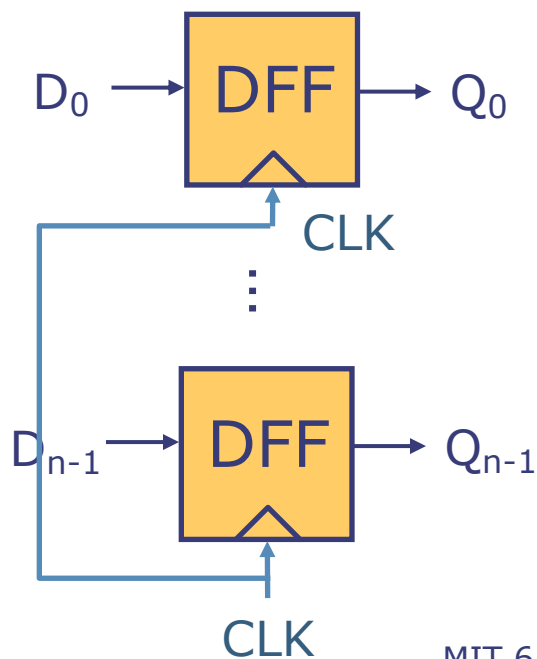- All the D Flip-Flops use the same periodic clock signal.
- Register: Group of DFFs
 - Stores multi-bit values



Synchronous Sequential Circuits

 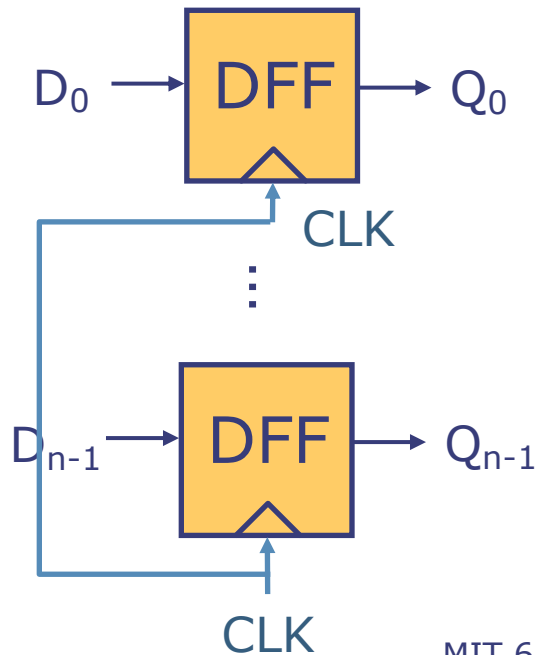- All the D Flip-Flops use the same periodic clock signal.
- Register: Group of DFFs
 - Stores multi-bit values
- Registers update their contents simultaneously, at the rising edge of the clock




Synchronous Sequential Circuits

- Synchronous sequential circuits: All state kept in registers driven by the same clock


Synchronous Sequential Circuits

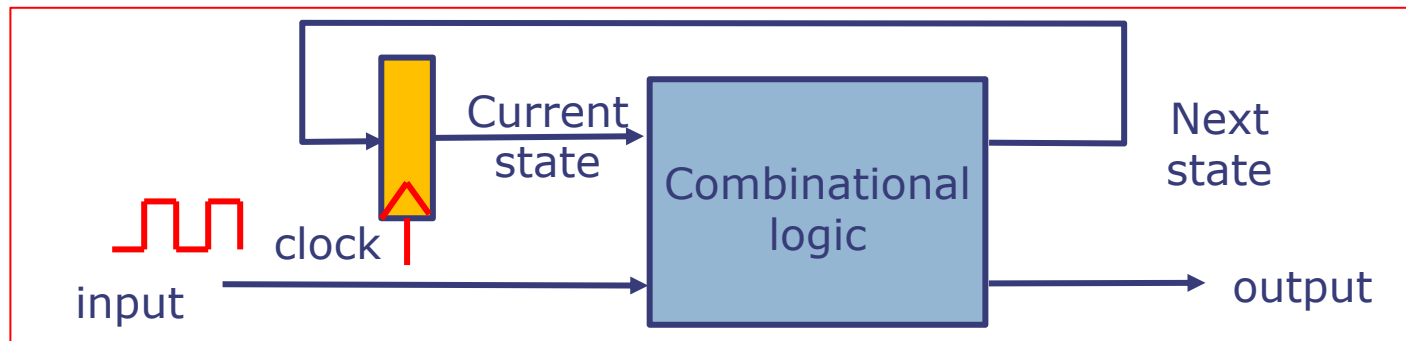- Synchronous sequential circuits: All state kept in registers driven by the same clock




Synchronous Sequential Circuits

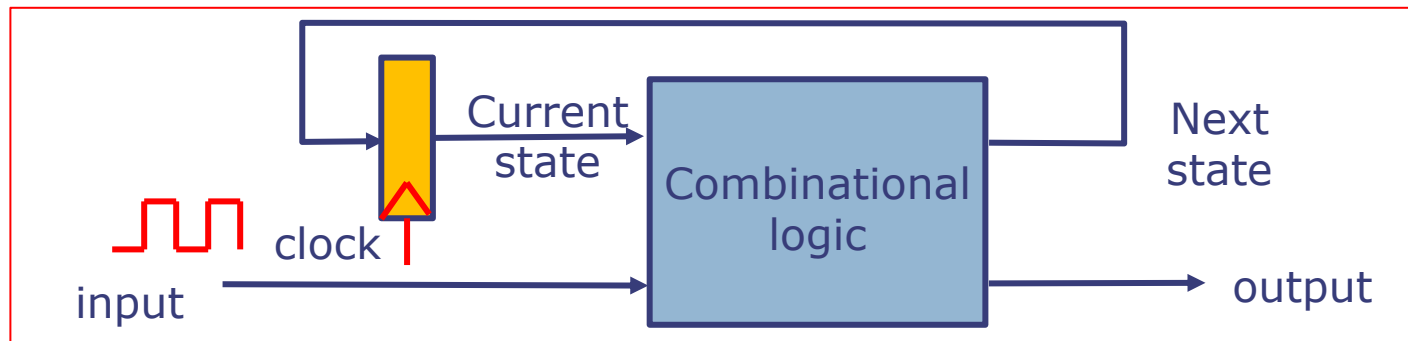- Synchronous sequential circuits: All state kept in registers driven by the same clock
- This allows discretizing time into cycles and abstracting sequential circuits as **finite state machines (FSMs)**.



Synchronous Sequential Circuits

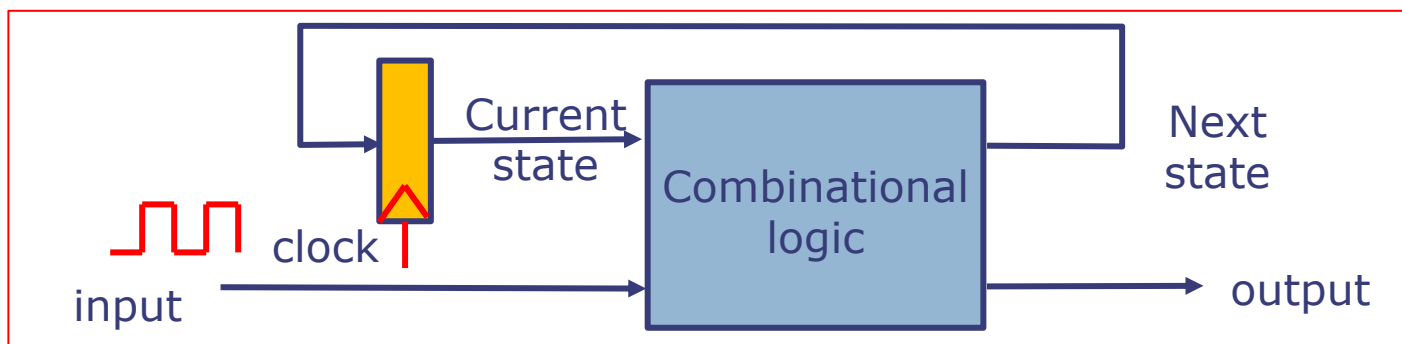- Synchronous sequential circuits: All state kept in registers driven by the same clock
- This allows discretizing time into cycles and abstracting sequential circuits as **finite state machines (FSMs)**.
- FSMs can be described with **state-transition diagrams** or truth tables



A Simple Sequential Circuit

Let's make a digital binary *Combination Lock*:




Specification:

- A 1-bit input (“0” or “1”)
- A 1-bit output (“Unlock” signal)
- UNLOCK is 1 if and only if:

Last 4 inputs were the “combination”: 0110

A Simple Sequential Circuit

 Let's make a digital binary *Combination Lock*:




Specification:

- A 1-bit input (“0” or “1”)
- A 1-bit output (“Unlock” signal)
- UNLOCK is 1 if and only if:

Last 4 inputs were the “combination”: 0110

How many states do we need?


State-Transition Diagram

 

Designing our lock


- Need an initial state; call it S0.

State-Transition Diagram

 


Designing our lock

- Need an initial state; call it S0.

 


State-Transition Diagram

 


Designing our lock

- Need an initial state; call it S0.

 


State-Transition Diagram

 


Designing our lock

 - Need an initial state; call it S0.
- Must have a separate state for each step of the proper entry sequence




State-Transition Diagram

 


Designing our lock

 - Need an initial state; call it S0.
- Must have a separate state for each step of the proper entry sequence




State-Transition Diagram

 


Designing our lock

 - Need an initial state; call it S0.
- Must have a separate state for each step of the proper entry sequence




State-Transition Diagram

 


Designing our lock

 - Need an initial state; call it S0.
- Must have a separate state for each step of the proper entry sequence
- Must handle other (erroneous) entries




State-Transition Diagram

 

Designing our lock

 - Need an initial state; call it S0.
- Must have a separate state for each step of the proper entry sequence
- Must handle other (erroneous) entries




Valid State-Transition Diagrams

- Arcs leaving a state must be:
 - (1) **mutually exclusive**
 - *For a given input value, can't have two choices*
 - (2) **collectively exhaustive**
 - *Every state must specify what happens for each possible input combination.*
 - *"Nothing happens" means arc back to itself.*

Two-Bit Counter


An Example

 

State-Transition Diagram

Two-Bit Counter

An Example

 


State-Transition Diagram

CurrentState	NextState	
	inc = 0	inc = 1
$q1^t \ q0^t$	$q1^{t+1} \ q0^{t+1}$	$q1^{t+1} \ q0^{t+1}$
0 0	0 0	0 1
0 1	0 1	1 0
1 0	1 0	1 1
1 1	1 1	0 0

Two-Bit Counter

An Example

 


State-Transition Diagram

CurrentState	NextState	
	inc = 0	inc = 1
$q1^t \ q0^t$	$q1^{t+1} \ q0^{t+1}$	$q1^{t+1} \ q0^{t+1}$
0 0	0 0	0 1
0 1	0 1	1 0
1 0	1 0	1 1
1 1	1 1	0 0

Two-Bit Counter

An Example

 


CurrentState	NextState	
	inc = 0	inc = 1
$q1^t \ q0^t$	$q1^{t+1} \ q0^{t+1}$	$q1^{t+1} \ q0^{t+1}$
0 0	0 0	0 1
0 1	0 1	1 0
1 0	1 0	1 1
1 1	1 1	0 0

State-Transition Diagram

$$q0^{t+1} = \sim inc \cdot q0^t + inc \cdot \sim q0^t$$

Two-Bit Counter

An Example

 


CurrentState	NextState	
	inc = 0	inc = 1
$q1^t \ q0^t$	$q1^{t+1} \ q0^{t+1}$	$q1^{t+1} \ q0^{t+1}$
0 0	0 0	0 1
0 1	0 1	1 0
1 0	1 0	1 1
1 1	1 1	0 0

State-Transition Diagram

$$\begin{aligned}
 q0^{t+1} &= \sim inc \cdot q0^t + inc \cdot \sim q0^t \\
 &= inc \oplus q0^t
 \end{aligned}$$

Two-Bit Counter

An Example

 

CurrentState	NextState	
	inc = 0	inc = 1
$q1^t \ q0^t$	$q1^{t+1} \ q0^{t+1}$	$q1^{t+1} \ q0^{t+1}$
0 0	0 0	0 1
0 1	0 1	1 0
1 0	1 0	1 1
1 1	1 1	0 0


State-Transition Diagram

$$\begin{aligned}
 q0^{t+1} &= \sim inc \cdot q0^t + inc \cdot \sim q0^t \\
 &= inc \oplus q0^t
 \end{aligned}$$

$$\begin{aligned}
 q1^{t+1} &= \sim inc \cdot q1^t + inc \cdot \sim q1^t \cdot q0^t + inc \cdot q1^t \cdot \sim q0^t \\
 &= \sim inc \cdot q1^t + inc \cdot (q1^t \oplus q0^t)
 \end{aligned}$$

Two-Bit Counter

An Example

 

CurrentState	NextState	
	inc = 0	inc = 1
$q1^t \ q0^t$	$q1^{t+1} \ q0^{t+1}$	$q1^{t+1} \ q0^{t+1}$
0 0	0 0	0 1
0 1	0 1	1 0
1 0	1 0	1 1
1 1	1 1	0 0

State-Transition Diagram

$$\begin{aligned}
 q0^{t+1} &= \sim inc \cdot q0^t + inc \cdot \sim q0^t \\
 &= inc \oplus q0^t
 \end{aligned}$$

$$\begin{aligned}
 q1^{t+1} &= \sim inc \cdot q1^t + inc \cdot \sim q1^t \cdot q0^t + inc \cdot q1^t \cdot \sim q0^t \\
 &= \sim inc \cdot q1^t + inc \cdot (q1^t \oplus q0^t)
 \end{aligned}$$

Output = current state = $q1q0$

Two-Bit Counter Circuit

Using D flip-flops

$$\begin{aligned}q0^{t+1} &= \sim inc \cdot q0^t + inc \cdot \sim q0^t \\q1^{t+1} &= \sim inc \cdot q1^t + inc \cdot (q1^t \oplus q0^t)\end{aligned}$$




Two-Bit Counter Circuit

Using D flip-flops

$$q0^{t+1} = \sim inc \cdot q0^t + inc \cdot \sim q0^t$$
$$q1^{t+1} = \sim inc \cdot q1^t + inc \cdot (q1^t \oplus q0^t)$$

 - Use two D flip-flops with *reset* and *enable* to store $q0$ and $q1$




Two-Bit Counter Circuit

Using D flip-flops

$$q0^{t+1} = \sim inc \cdot q0^t + inc \cdot \sim q0^t$$
$$q1^{t+1} = \sim inc \cdot q1^t + inc \cdot (q1^t \oplus q0^t)$$

 - Use two D flip-flops with *reset* and *enable* to store $q0$ and $q1$
- The state only changes when inc is 1. Let's connect inc to **EN** and simplify the equations




Two-Bit Counter Circuit

Using D flip-flops

$$q0^{t+1} = \sim inc \cdot q0^t + inc \cdot \sim q0^t$$
$$q1^{t+1} = \sim inc \cdot q1^t + inc \cdot (q1^t \oplus q0^t)$$

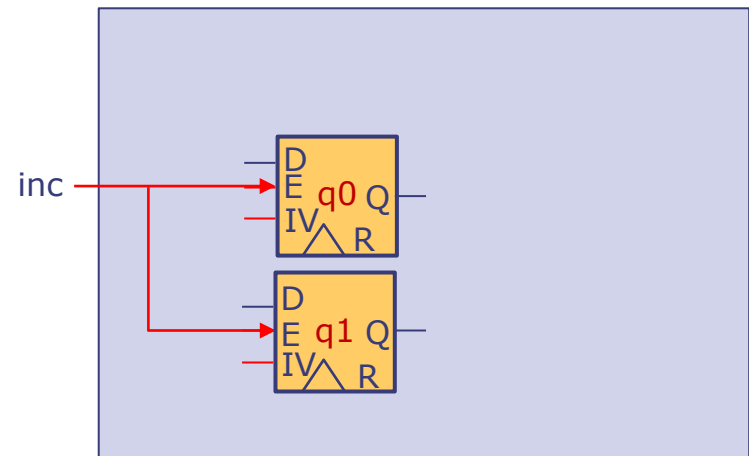- Use two D flip-flops with *reset* and *enable* to store $q0$ and $q1$
- The state only changes when inc is 1. Let's connect inc to **EN** and simplify the equations




Two-Bit Counter Circuit

Using D flip-flops

$$q0^{t+1} = \sim inc \cdot q0^t + inc \cdot \sim q0^t$$
$$q1^{t+1} = \sim inc \cdot q1^t + inc \cdot (q1^t \oplus q0^t)$$

- Use two D flip-flops with *reset* and *enable* to store $q0$ and $q1$
- The state only changes when inc is 1. Let's connect inc to **EN** and simplify the equations
 
$$\left. \begin{aligned} q0^{t+1} &= \sim q0^t \\ q1^{t+1} &= q1^t \oplus q0^t \end{aligned} \right\} inc=1$$




Two-Bit Counter Circuit

Using D flip-flops

$$q0^{t+1} = \sim inc \cdot q0^t + inc \cdot \sim q0^t$$
$$q1^{t+1} = \sim inc \cdot q1^t + inc \cdot (q1^t \oplus q0^t)$$

- Use two D flip-flops with *reset* and *enable* to store $q0$ and $q1$
- The state only changes when inc is 1. Let's connect inc to **EN** and simplify the equations
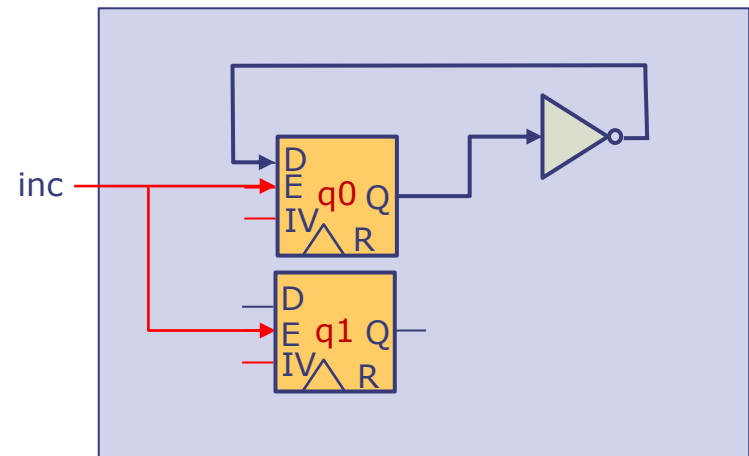
$$\left. \begin{aligned} q0^{t+1} &= \sim q0^t \\ q1^{t+1} &= q1^t \oplus q0^t \end{aligned} \right\} inc=1$$




Two-Bit Counter Circuit

Using D flip-flops

$$q0^{t+1} = \sim inc \cdot q0^t + inc \cdot \sim q0^t$$
$$q1^{t+1} = \sim inc \cdot q1^t + inc \cdot (q1^t \oplus q0^t)$$

- Use two D flip-flops with *reset* and *enable* to store $q0$ and $q1$
- The state only changes when inc is 1. Let's connect inc to **EN** and simplify the equations
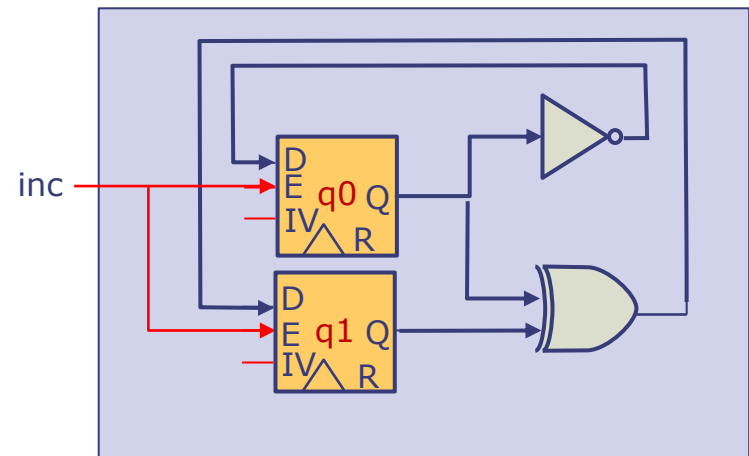
$$\left. \begin{aligned} q0^{t+1} &= \sim q0^t \\ q1^{t+1} &= q1^t \oplus q0^t \end{aligned} \right\} inc=1$$




Two-Bit Counter Circuit

Using D flip-flops

$$q0^{t+1} = \sim inc \cdot q0^t + inc \cdot \sim q0^t$$
$$q1^{t+1} = \sim inc \cdot q1^t + inc \cdot (q1^t \oplus q0^t)$$

- Use two D flip-flops with *reset* and *enable* to store $q0$ and $q1$
- The state only changes when inc is 1. Let's connect inc to **EN** and simplify the equations
- Output is $q1q0$
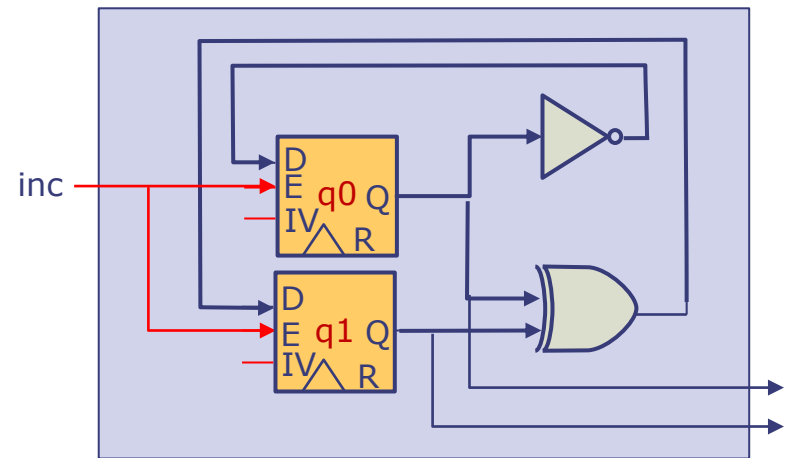
$$\left. \begin{aligned} q0^{t+1} &= \sim q0^t \\ q1^{t+1} &= q1^t \oplus q0^t \end{aligned} \right\} inc=1$$




Two-Bit Counter Circuit

Using D flip-flops

$$q0^{t+1} = \sim inc \cdot q0^t + inc \cdot \sim q0^t$$
$$q1^{t+1} = \sim inc \cdot q1^t + inc \cdot (q1^t \oplus q0^t)$$



- Use two D flip-flops with *reset* and *enable* to store $q0$ and $q1$
- The state only changes when inc is 1. Let's connect inc to **EN** and simplify the equations
- Output is $q1q0$
- Set Initial Value of both flip-flops to 0 (initial state: 00)
 - Loaded when Reset = 1
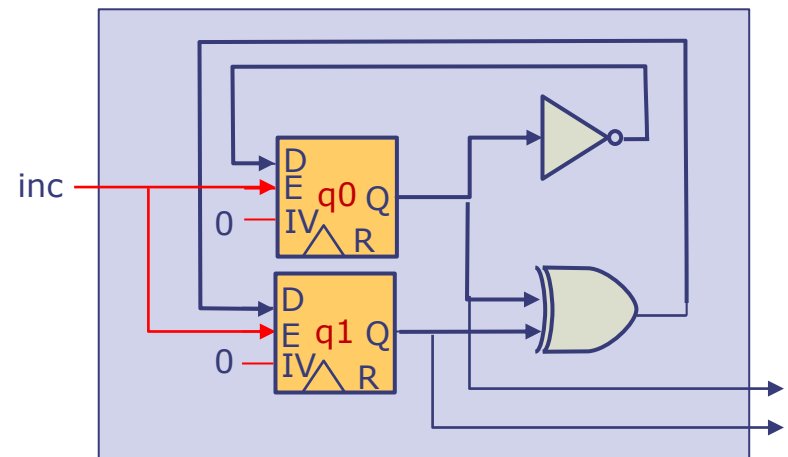
$$\left. \begin{aligned} q0^{t+1} &= \sim q0^t \\ q1^{t+1} &= q1^t \oplus q0^t \end{aligned} \right\} inc=1$$




Timing Constraints in Sequential Circuits

Recap: D Flip-Flop Timing

 
 


- Flip-flop input D should not change around the rising edge of the clock to avoid *metastability*
- Formally, D should be a stable and valid digital value:
 - For at least t_{SETUP} before the rising edge of the clock
 - For at least t_{HOLD} after the rising edge of the clock
- Flip-flop propagation delay t_{PD} is measured from rising edge of the clock to valid output (CLK \rightarrow Q)



Single-clock Synchronous Circuits

 



Single-clock Synchronous Circuits

  

Single-clock Synchronous Circuits

 
 


Single-clock Synchronous Circuits

 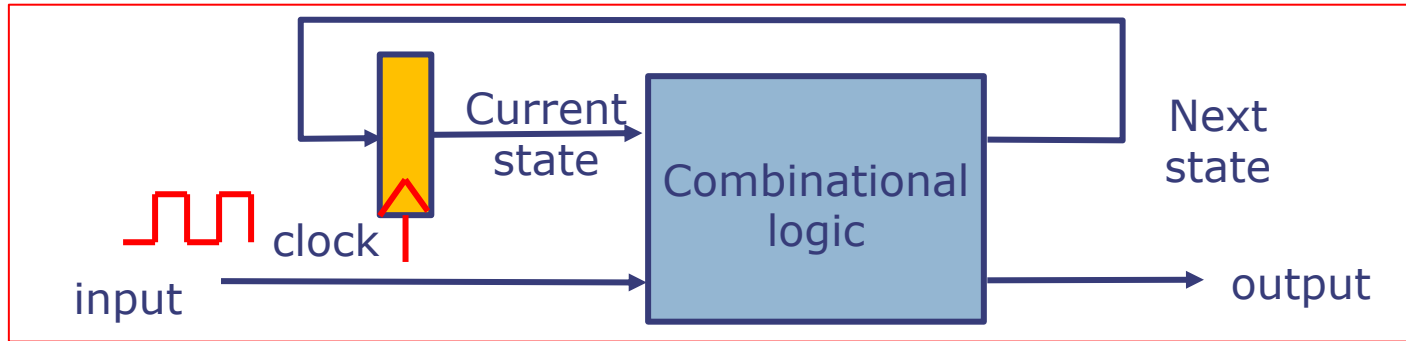


Need to analyze
the timing of each
register-to-register path


Meeting the Setup-Time Constraint

  



Meeting the Setup-Time Constraint

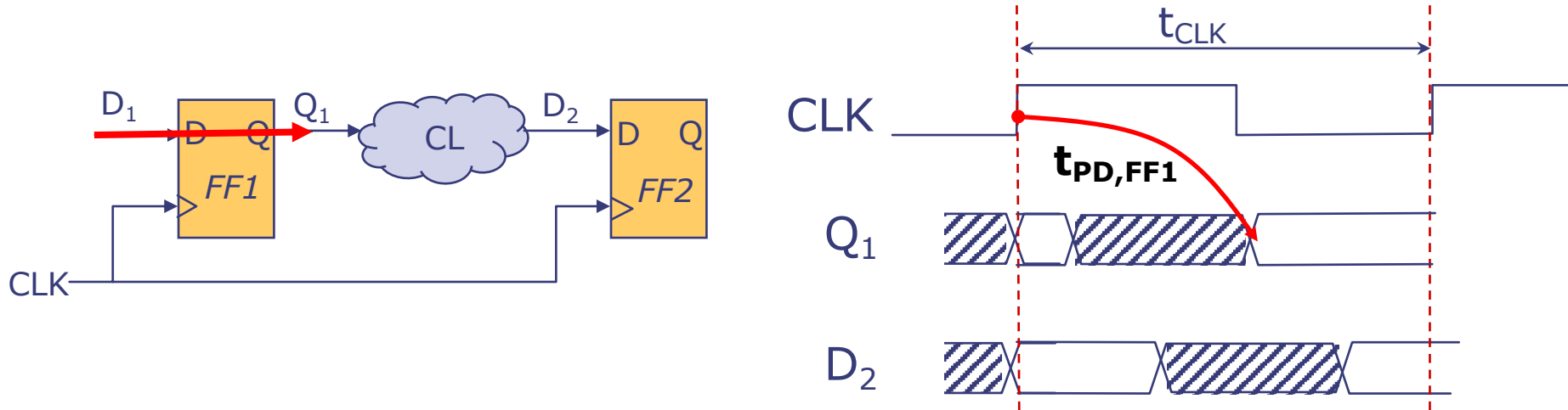

Meeting the Setup-Time Constraint

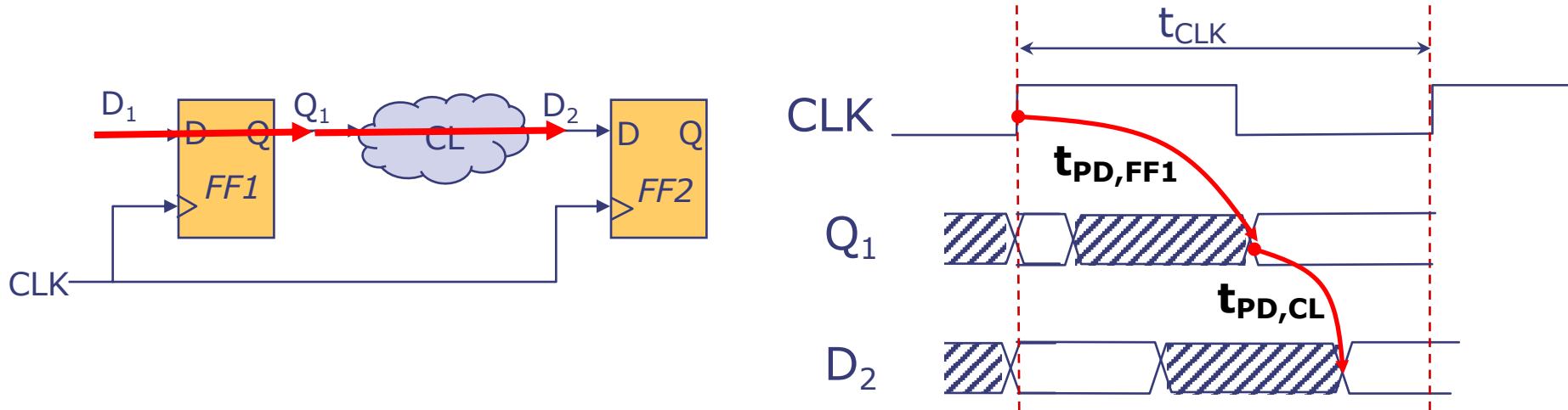


Meeting the Setup-Time Constraint

  


- To meet FF2's setup time,


Meeting the Setup-Time Constraint

 

- To meet FF2's setup time,

 


Meeting the Setup-Time Constraint

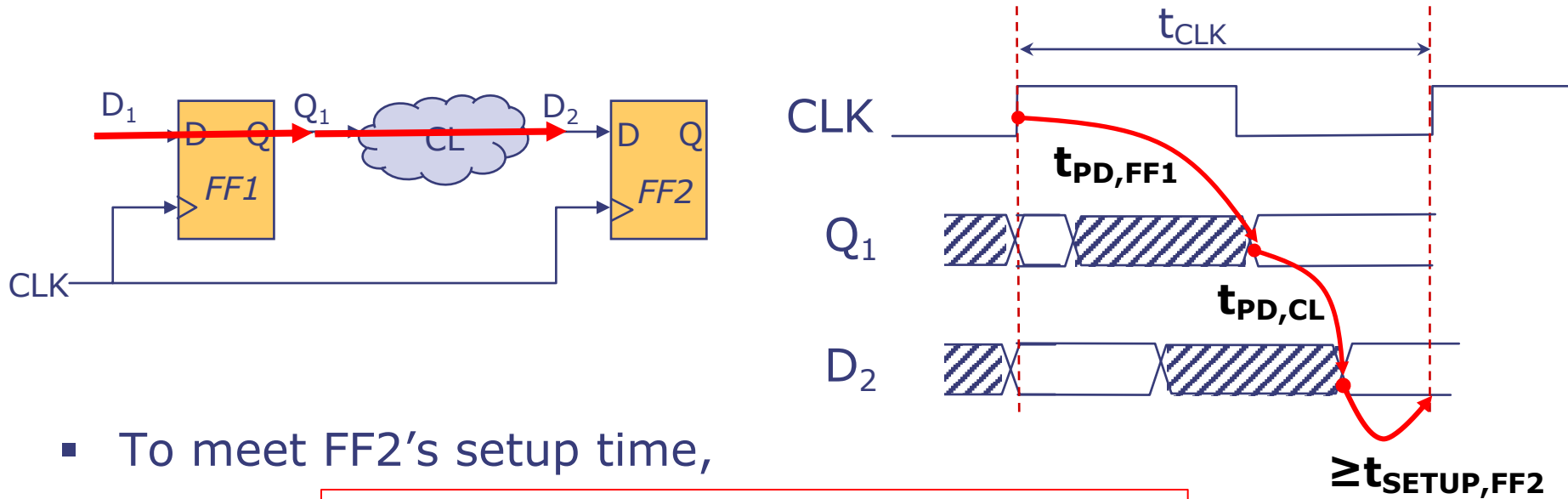

- To meet FF2's setup time,

$$t_{CLK} \geq t_{PD,FF1} + t_{PD,CL} + t_{SETUP,FF2}$$

Meeting the Setup-Time Constraint

 


- To meet FF2's setup time,

$$t_{CLK} \geq t_{PD,FF1} + t_{PD,CL} + t_{SETUP,FF2}$$

- The **slowest** register-to-register path in the system determines the clock;

Meeting the Setup-Time Constraint


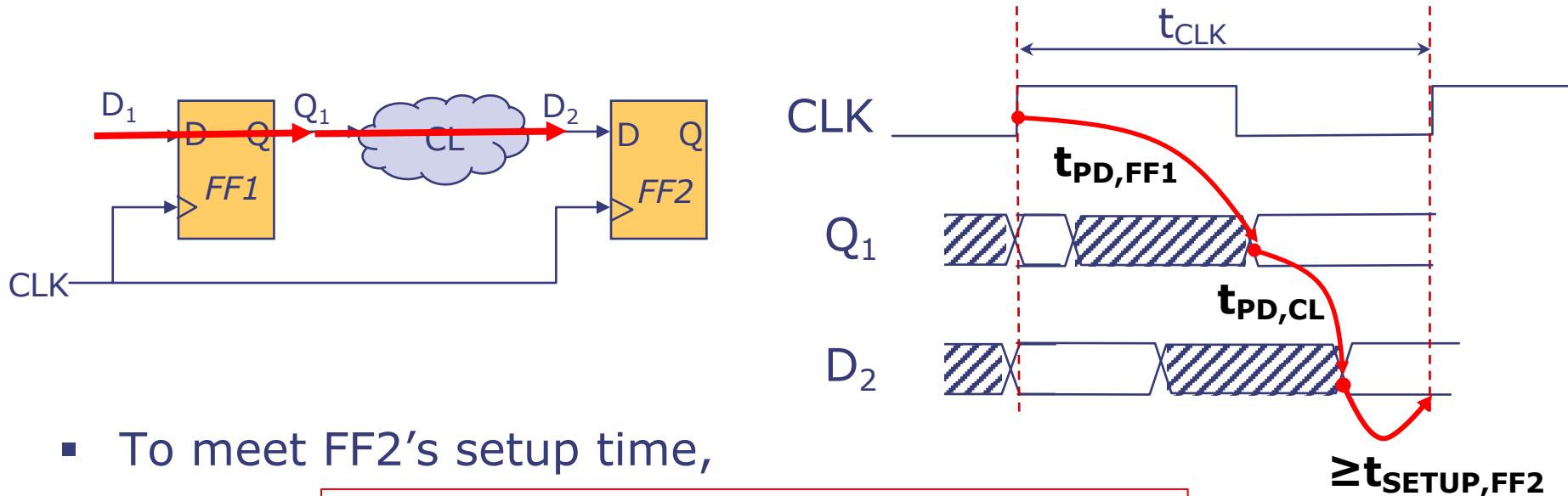


- To meet FF2's setup time,

$$t_{CLK} \geq t_{PD,FF1} + t_{PD,CL} + t_{SETUP,FF2}$$



- The **slowest** register-to-register path in the system determines the clock;
- Equivalently, a given register technology and clock limit the amount of combinational logic between registers

Meeting the Hold-Time Constraint

  


- Hold time (t_{HOLD}) constraint of FF2 may be violated if D₂ changes too quickly

Meeting the Hold-Time Constraint

  


- Hold time (t_{HOLD}) constraint of FF2 may be violated if D₂ changes too quickly

Meeting the Hold-Time Constraint

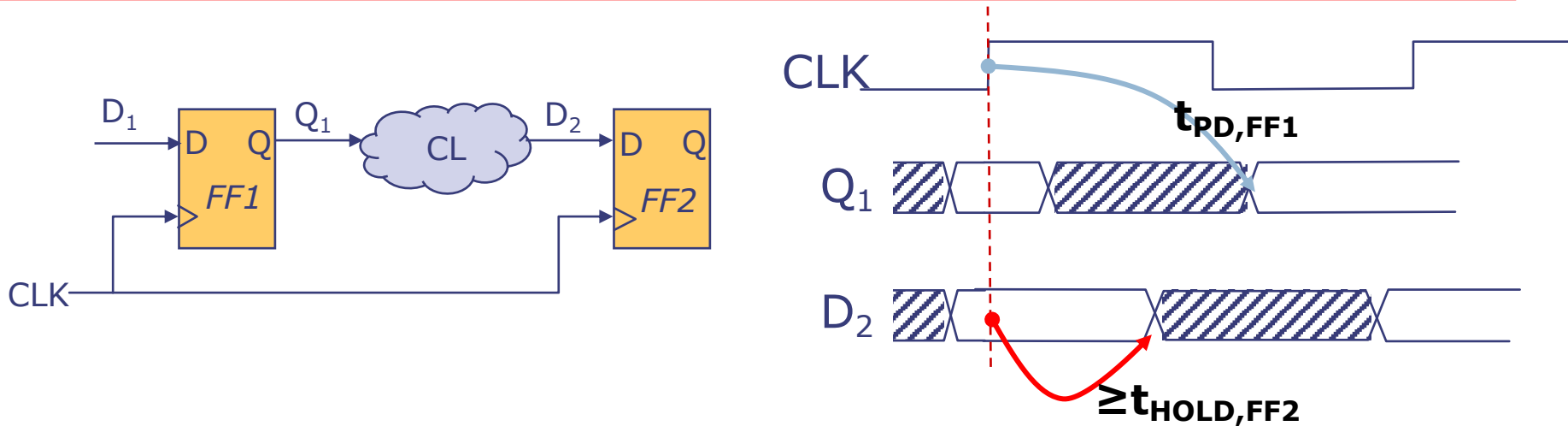


- Hold time (t_{HOLD}) constraint of FF2 may be violated if D_2 changes too quickly
- Propagation delay (t_{PD}), the upper bound on time from valid inputs to valid outputs, does not help us analyze hold time!

Meeting the Hold-Time Constraint

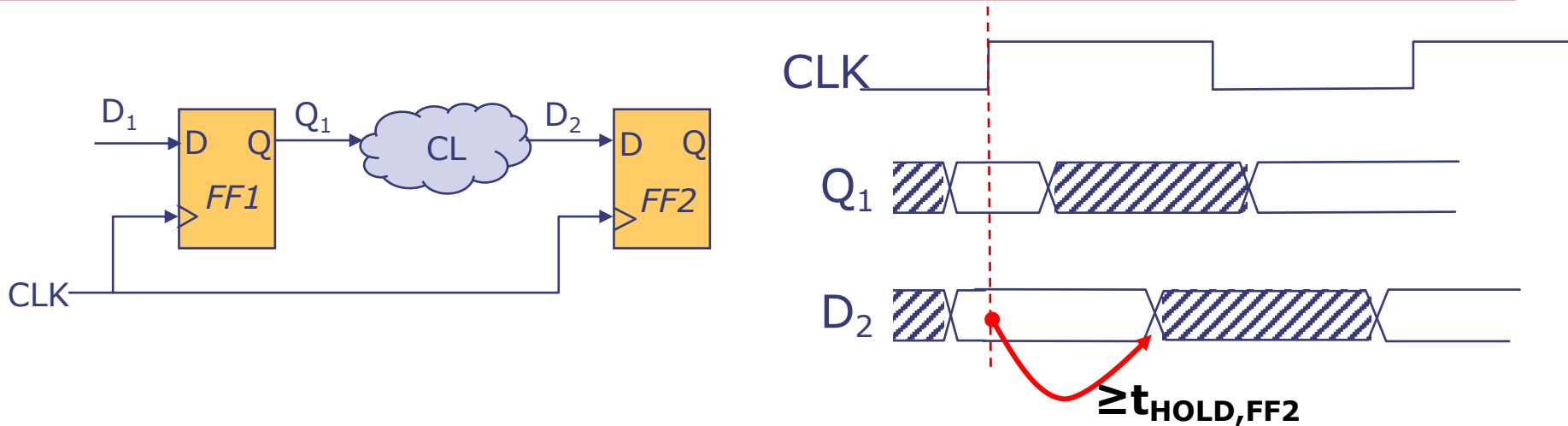


- Hold time (t_{HOLD}) constraint of FF2 may be violated if D_2 changes too quickly
- Propagation delay (t_{PD}), the upper bound on time from valid inputs to valid outputs, does not help us analyze hold time!

Meeting the Hold-Time Constraint

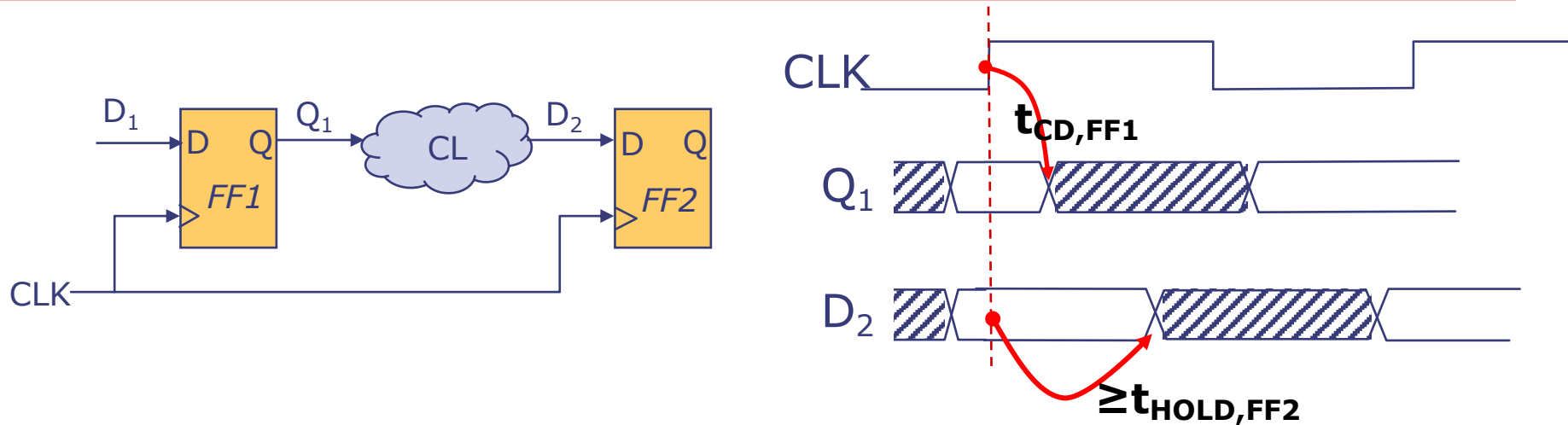


- Hold time (t_{HOLD}) constraint of FF2 may be violated if D_2 changes too quickly
- Propagation delay (t_{PD}), the upper bound on time from valid inputs to valid outputs, does not help us analyze hold time!
- *Contamination delay* (t_{CD}) is the lower bound on time from input-to-output transition (invalid input to invalid output)

Meeting the Hold-Time Constraint

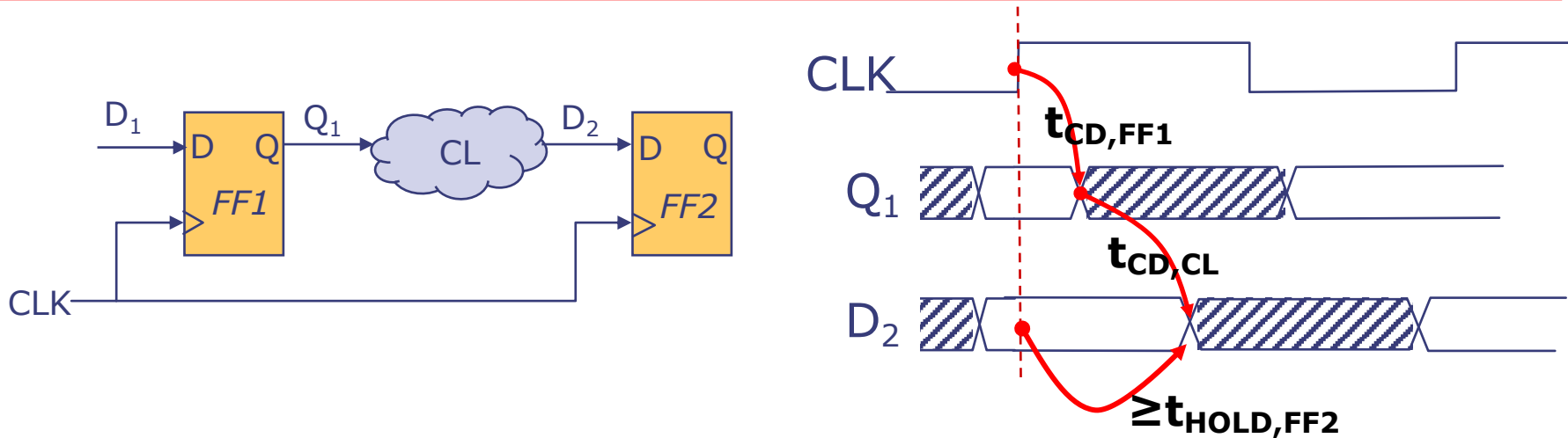

- Hold time (t_{HOLD}) constraint of FF2 may be violated if D_2 changes too quickly
- Propagation delay (t_{PD}), the upper bound on time from valid inputs to valid outputs, does not help us analyze hold time!
- *Contamination delay* (t_{CD}) is the lower bound on time from input-to-output transition (invalid input to invalid output)


Meeting the Hold-Time Constraint

 

- Hold time (t_{HOLD}) constraint of FF2 may be violated if D_2 changes too quickly
- Propagation delay (t_{PD}), the upper bound on time from valid inputs to valid outputs, does not help us analyze hold time!
- *Contamination delay* (t_{CD}) is the lower bound on time from input-to-output transition (invalid input to invalid output)
- To meet FF2's hold-time constraint

$$t_{CD,FF1} + t_{CD,CL} \geq t_{HOLD,FF2}$$

Meeting the Hold-Time Constraint

 

- Hold time (t_{HOLD}) constraint of FF2 may be violated if D_2 changes too quickly
- Propagation delay (t_{PD}), the upper bound on time from valid inputs to valid outputs, does not help us analyze hold time!
- *Contamination delay* (t_{CD}) is the lower bound on time from input-to-output transition (invalid input to invalid output)
- To meet FF2's hold-time constraint


$$t_{CD,FF1} + t_{CD,CL} \geq t_{HOLD,FF2}$$

Tools may need to add logic to fast paths to meet t_{HOLD}


Timing Summary

- For a sequential circuit to work properly, we must guarantee that the **setup time** and **hold time** constraints of every register will always be satisfied.
- The **setup time** constraint is affected by both the logic in the circuit *and* the clock period. To fix violations, either:
 - Change the logic to be faster (lower t_{PD})
 - Change the clock to be slower (higher t_{CLK})
- The **hold time** constraint is affected *only* by the logic in the circuit.
 - Changing the clock period will not fix violations.
 - Sum of contamination delays must be greater than the register hold time, otherwise the circuit won't work.
- If hold time is satisfied, then the fastest clock period can be set as the **maximum sum of the propagation delays plus setup time** across all register-to-register paths.


Sequential Circuit Timing Example

 


Sequential Circuit Timing Example

 

Sequential Circuit Timing Example

 


Sequential Circuit Timing Example

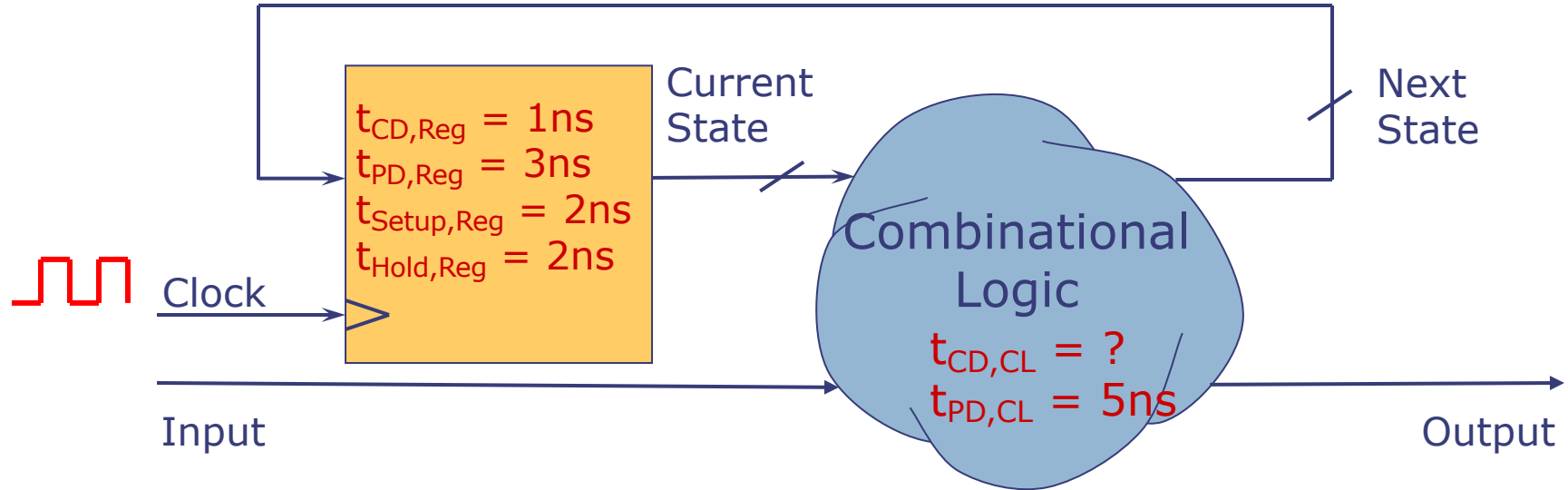

Questions:

- Constraints on t_{CD} for the logic?
- Minimum clock period?

Sequential Circuit Timing Example

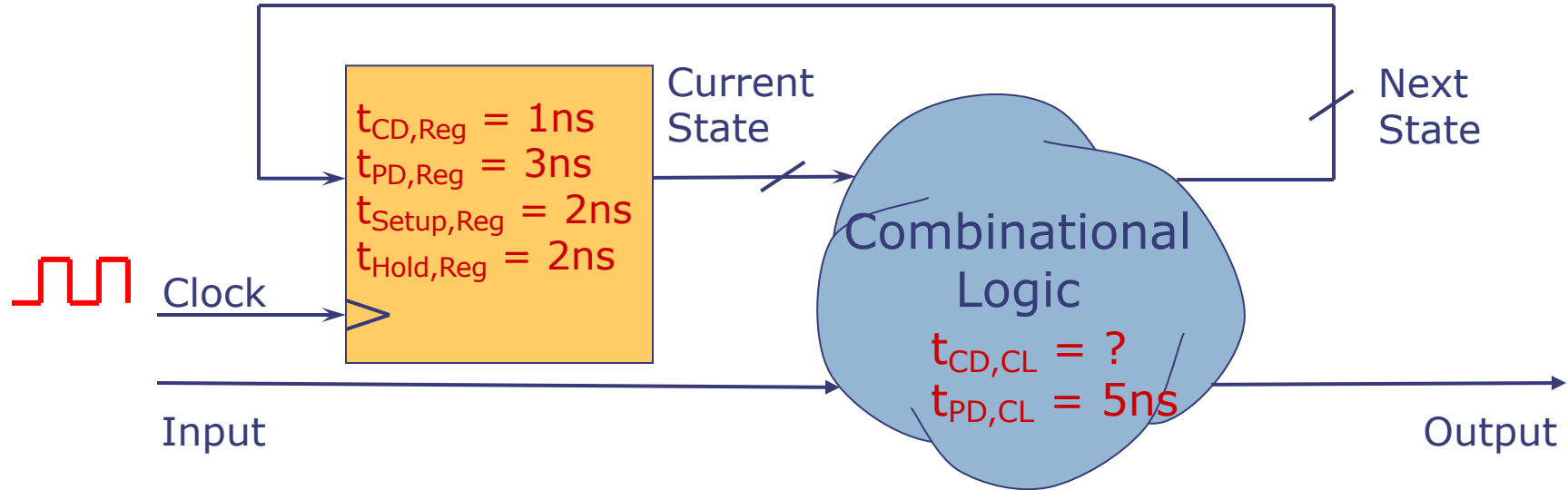


Questions:

- Constraints on t_{CD} for the logic?

$$t_{CD,Reg} (1 ns) + t_{CD,CL}(?) \geq t_{Hold,Reg}(2 ns)$$

- Minimum clock period?

Sequential Circuit Timing Example

 

Questions:


- Constraints on t_{CD} for the logic?

$$t_{CD,Reg} (1 ns) + t_{CD,CL}(?) \geq t_{Hold,Reg}(2 ns)$$

$$t_{CD,CL} \geq 1 ns$$

- Minimum clock period?

Sequential Circuit Timing Example

 

Questions:

- Constraints on t_{CD} for the logic?

$$t_{CD,Reg} (1 ns) + t_{CD,CL}(?) \geq t_{Hold,Reg}(2 ns)$$

$$t_{CD,CL} \geq 1 ns$$

- Minimum clock period?

$$t_{CLK} \geq t_{PD,Reg} + t_{PD,CL} + t_{Setup,Reg} = 10ns$$

Thank you!

Next lecture:
Sequential logic in Minispec