


## 6.004 Worksheet Questions

### L11 – Sequential Circuits in Minispec

**Note:** A subset of problems are marked with a red star (★). We especially encourage you to try these out before recitation.
 
#### Problem 1. ★

Implement the combination lock finite-state machine (FSM) from Lecture 10 as a Minispec module. The lock FSM should unlock only when the last four input bits have been 0110. The diagram below shows the FSM's state-transition diagram.



- (A) Implement this state-transition diagram by filling in the code skeleton below. Use the State enum to ensure state values can only be S0-S4.

```

typedef enum { S0, S1, S2, S3, S4 } State;

module Lock;
    Reg#(State) state(S0);

    input Bit#(1) in;

    rule tick;
        state <= case (state)
            S0: _____;
            S1: _____;
            S2: _____;
            S3: _____;
            S4: _____;
        endcase;
    endrule

    method Bool unlock = _____;
endmodule
  
```

(B) How many flip-flops does this lock FSM require to encode all possible states?

(C) Consider an alternative implementation of the Lock module that stores the last four input bits. Fill in the skeleton code below to complete this implementation.

```
module Lock;
  Reg#(Bit#(4)) lastFourBits(4'b1111);

  input Bit#(1) in;

  rule tick;
    lastFourBits <= _____;
  endrule

  method Bool unlock = _____;
endmodule
```

## Problem 2.

Below is an implementation of a 4-bit lock, `Lock4`, that matches against an arbitrary pattern, given as a *module argument*. Use `Lock4` to implement `Lock8`, a lock module that unlocks with an 8-bit combination.

```
module Lock4(Bit#(4) combo);
    // Storing the most significant bit, inverted will ensure
    // that we will not unlock in less than four cycles
    Reg#(Bit#(4)) lastFourBits(signExtend(~combo[3]));

    input Bit#(1) in;
    rule tick;
        lastFourBits <= {lastFourBits[2:0], in};
    endrule

    method Bool unlock = (lastFourBits == combo);
endmodule

module Lock8(Bit#(8) combo);

    Lock4 upper(_____);
    Lock4 lower(_____);

    _____; // Hint: You need some extra state
                // to make both locks operate in
sync
    input Bit#(1) in;
    rule tick;
        _____;
        _____;
        _____;
        _____;

    endrule

    method Bool unlock =
        _____;
endmodule
```

### Problem 3.

★ (A) Composing two 4-bit Lock modules to make an 8-bit Lock module is kludgy. Instead, we can make a parametric module, `Lock#(n)`, that unlocks on an  $n$ -bit combination sequence (given as a module argument). Implement `Lock#(n)` by filling out the code skeleton below.

```
module Lock#(Integer n)(_____);

    Reg#(____)lastBits(_____);

    input Bit#(1) in;

    rule tick;

    _____;

endrule

    method Bool unlock = _____;

endmodule
```

(B) Test your `Lock#(n)` module by completing the testbench module below, called `LockTest`. Ideally, your testbench should test all possible 8-bit input sequences; at a minimum, it should check a few incorrect sequences as well as the correct sequence. Your testbench should print PASS if all tests are correct, and FAIL otherwise. You can add additional registers or submodules, though they aren't needed.

```
module LockTest;
    Bit#(8) combo = 8'b01100111;
    Lock#(8) lock(combo);
    Reg#(Bit#(16)) cycle(0);

    rule test;

        cycle <= cycle + 1;
    endrule
endmodule
```


#### Problem 4. ★

In this problem, we construct a sequential circuit to compute the  $N^{\text{th}}$  Fibonacci number denoted by  $F_N$ . The following recurrence relation defines the Fibonacci sequence.

$$F_0 = 0, F_1 = 1, F_N = F_{N-1} + F_{N-2} \quad \forall \quad N \geq 2$$

There are two registers  $x$  and  $y$  that store the Fibonacci values for two consecutive integers. In addition, a counter register  $i$  is initialized to  $N-1$  and decremented each cycle. The computation stops when register  $i$  goes down to 0 and the result ( $F_N$ ) is available in register  $x$ .

 - (A) What are the initial values for registers  $x$  and  $y$ ?
- (B) Derive the next state computation equations for the three registers.
- (C) Derive the logic for the enable signal that determines when the registers are updated using the next state logic. Note that all three registers are controlled by a single enable signal.
- (D) Implement the sequential circuit using the next state and enable logic derived above.



Implement the Fibonacci FSM by filling in the code skeleton below.

```
// Use 32-bit values
typedef Bit#(32) Word;

module Fibonacci;
    Reg#(Word) x(0);
    Reg#(Word) y(0);
    Reg#(Word) i(0);

    input Maybe#(Word) in default = Invalid;

    rule tick;

    endrule

    method Maybe#(Word) result = _____;
endmodule
```

### Problem 5.

Implement a sequential circuit to compute the factorial of a 16-bit number.

- (A) Design the circuit as a sequential Minispec module by filling in the skeleton code below. The circuit should start a new factorial computation when a Valid input is given. Register **x** should be initialized to the input argument, and register **f** should eventually hold the output. When the computation is finished, the result method should return a Valid result; while the computation is ongoing, result should return Invalid.

You can use the multiplication operator (\*). \* performs unsigned multiplication of Bit#(n) inputs. Assume inputs and results are unsigned. Though we have not yet seen how to multiply two numbers, lab 5 includes the design of a multiplier from scratch.

```
module Factorial;
  Reg#(Bit#(16)) x(0);
  Reg#(Bit#(16)) f(0);

  input Maybe#(Bit#(16)) in default = Invalid;

  rule factorialStep;

  endrule

  method Maybe#(Bit#(16)) result =
    _____;
endmodule
```

- (B) Manually synthesize your Factorial module into a sequential circuit with registers and combinational logic blocks (similar to how Lecture 11 does this with GCD). No need to draw the implementation of all basic signals (e.g., you can give formulas, like for the sel signal in Lecture 11).



## Problem 6. From Past Quizzes (Fall 2019)

You join a startup building hardware to mine Dogecoins. In this cryptocurrency, mining coins requires repeatedly evaluating a function with two arguments,  $sc(x, y)$ .  $x$  is given to you, and mining requires trying different values of  $y$  until you find a  $y$  for which  $sc(x, y)$  is below a threshold value. Finding such a  $y$  value yields several Dogecoins as a reward, which you can then exchange for cold hard cash.

Because the  $sc$  function is expensive, it is implemented as a multi-cycle sequential module, called  $SC$ .  $SC$  is given to you. Its implementation is irrelevant, and its interface, shown below, is the usual interface for multi-cycle modules:  $SC$  has a single input,  $in$ , and a single method,  $getResult()$ . To start a new computation, the module user sets  $in$  to a **Valid** **Args** struct containing arguments  $x$  and  $y$ . Some cycles later,  $SC$  produces the result as a **Valid** output of its  $getResult()$  method. While  $SC$  is processing an input, the  $getResult()$  method returns **Invalid** and  $in$  should stay **Invalid**.


```

module SC;
    input Maybe#(Args) in default = Invalid;
    method Maybe#(Bit#(32)) getResult();
        // unknown implementation
    endmethod

    // unknown rules
endmodule

// input struct to SC
typedef struct {
    Bit#(32) x;
    Bit#(32) y;
} Args;
    
```

You are asked to design the **ArgFeeder** module, which accepts an input  $x$ , and feeds a sequence of inputs  $(x, 0)$ ,  $(x, 1)$ ,  $(x, 2)$ , ...,  $(x, y-1)$ ,  $(x, y)$  to the  $SC$  module. **ArgFeeder** keeps feeding values to  $SC$  until  $SC$ 's result is less than **threshold** (a parameter to your module). At that point, **ArgFeeder** should return the  $y$  such that  $(x, y)$  meets this condition through its  $getResult()$  method. The diagram below sketches the implementation of **ArgFeeder**. Like  $SC$ , **ArgFeeder** follows the usual interface for a multi-cycle module.

 

Implement the **ArgFeeder** module by completing the implementation of the  $getResult()$  method and the **tick** rule. The rule considers three cases:

- (i) a new input is provided to **ArgFeeder**,
- (ii)  $SC$  returns a **Valid** result, and it is *less* than the threshold value, and
- (iii)  $SC$  returns a **Valid** result, but it is *not less* than the threshold value.

**You may use any Minispec operator, including arithmetic (+, -, \*, /). You will not need additional registers to complete this problem. Do not add additional rules, methods, or functions.**

```

module ArgFeeder#(Integer threshold);
  SC sc;

  Reg#(Maybe#(Bit#(32))) out(Invalid);
  RegU#(Bit#(32)) x;
  RegU#(Bit#(32)) y;

  input Maybe#(Bit#(32)) in_x default = Invalid;

  method Maybe#(Bit#(32)) getResult();
    // implement the getResult() method
    return 

|  |
|--|
|  |
|--|

;
  endmethod

  rule tick;
    if (isValid(in_x)) begin
      // case (i): received a new input; start a new sequence of (x, y) pairs
      sc.in = Valid(Args{x: 

|  |
|--|
|  |
|--|

, y: 

|  |
|--|
|  |
|--|

});
      out <= 

|  |
|--|
|  |
|--|

;
      x <= 

|  |
|--|
|  |
|--|

;
      y <= 

|  |
|--|
|  |
|--|

;

      end else if (isValid(sc.getResult())) begin
        if (fromMaybe(?, sc.getResult()) < threshold) begin
          // case (ii): result satisfies threshold
          out <= 

|  |
|--|
|  |
|--|

;

          end else begin
            // case (iii): result does not yet satisfy threshold
            // send next (x, y) pair to SC
            sc.in = Valid(Args{x: 

|  |
|--|
|  |
|--|

, y: 

|  |
|--|
|  |
|--|

});
            y <= 

|  |
|--|
|  |
|--|

;

          end
        end
      endrule
    endmodule

```

### Problem 7. From Past Quizzes (Spring 2020) ★

The incomplete Minispec module, `FindLongestBitRun`, below counts the length of the longest string of 1's in a 32-bit word. The algorithm works by repeatedly performing a bitwise AND of the word with a version of itself that has been left-shifted by one. This repeats until the word is 0. The number of iterations required is the longest string of 1's in the word. This works because each iteration converts the last 1 in any string of 1's into a 0. The word will not equal zero until its longest string of 1's has all been converted into 0's.

The circuit should start a new computation when a Valid input is given and `bitString` is 0. The `bitString` register should be initialized to the input argument, and register `n` should hold the output. When the computation is finished, the `result` method should return a Valid result; while the computation is ongoing, `result` should return Invalid.

```
typedef Bit#(32) Word;

module FindLongestBitRun;
  Reg#(Bool) initialized(False);
  Reg#(Bit#(6)) n(0);
  Reg#(Word) bitString(0);

  input Maybe#(Word) in default = Invalid;

  method Maybe#(Bit#(6)) result;
    return (initialized && bitString == 0) ? [Part A1] : [Part A1];
  endmethod

  rule tick;
    if (isValid(in) && bitString == 0) begin
      n <= 0;
      bitString <= [Part A2];
      initialized <= True;
    end else if (initialized && (bitString != 0)) begin
      n <= n + 1;
      bitString <= [Part A3];
    end
  endrule
endmodule
```

(A) There are blanks in the code above labeled [Part A#]. #]. **Fill in the missing code, by copying each of the lines below and filling in the blanks corresponding to parts A1, A2, and A3.**

You may use any Minispec operators, built-in functions, and literals. You will not need additional registers to complete this problem. Do not add other rules, methods, or functions.

**A1:** `return` (initialized && bitString == 0) ? \_\_\_\_\_ : \_\_\_\_\_;

**A2:** `bitString` <= \_\_\_\_\_;

**A3:** `bitString` <= \_\_\_\_\_;

(B) At cycle 0, the input is set to `Valid(32'b0111)`. **Copy and fill in the table below to indicate the values at the output of the `result()` method, the value in register `n`, and the value in the `bitString` register.** Write “Invalid” if a value is invalid, “?” if a value is unknown, and just a number to indicate a valid value (i.e. you do not need to write “Valid(5)”; just write “5”). “0b” indicates that the number after it is a binary value.


**Copy and fill in the table below**

Cycle	0	1	2	3	4	5	6
Input	0b0111	Invalid	0b1111	Invalid	0b0001	Invalid	Invalid
result() output							
value in register n							
value in bitString							
 
### Problem 8. From Past Quizzes (Fall 2020)

Suppose we want to create a system that decides if the concatenation of its **previous** 2 single-bit inputs is a power of 2 (where the MSB is the input from 2 cycles ago and the LSB is from 1 cycle ago). If the previous 2 bits (prior to the current input) are a power-of-two the system outputs a 1, otherwise it outputs 0. Before any input is sent, assume the initial previous 2 bits are 2'b00.

A partial FSM diagram of this circuit is shown below:



*Before receiving any inputs the FSM is in state A.*

(A) For this FSM to provide the correct answer, to what existing states must D transition to (A, B, C, or D), and what output does D give (0 or 1)?

Current State = D, Input = 0, Next State = \_\_\_\_\_

Current State = D, Input = 1, Next State = \_\_\_\_\_

Current State = D, Output = \_\_\_\_\_

(B) Using the partial FSM, fill out the truth table below.

State	Input	Next State	Output
A	0	A	0
A	1		
B	0	D	
B	1		
C	0	D	0
C	1	C	
D	0	<u>Part_A</u>	<u>Part_A</u>
D	1	<u>Part_A</u>	

(C) We now want to implement a different version of this is-power-of-2 sequential circuit in minispec. In this version, if the **previous 5 bits** are a power of 2 the module's `getOutput` method will **return  $\log_2(\text{previous 5 bits})$ , otherwise it will return -1.**

To determine is-power-of-2, we will use the following identity **for integers  $X \geq 0$  and  $N > 0$ :**

$$X = 0 \text{ or } X = 2^N \rightarrow X \& (X - 1) = 0$$

The module has 2 registers:

**prevBits:** contains the 5 bits to check for is-power-of-2 in the current cycle.

**newOneIndex:** contains the index of the most recent "1" bit in **prevBits**. Hint: how does this relate to  $\log_2(\text{prevBits})$ ? (Note: this value is stored as a 4-bit 2's complement value to support initializing it to -1).

**Fill in the minispec implementation of the described module:**

**(label 4C)**

```
module PowTwo;
  Reg#(Bit#(5)) prevBits(0);
  Reg#(Bit#(4)) newOneIndex(-1);

  input Bit#(1) in;

  rule tick;

    prevBits <= _____;

    if (in == 1) newOneIndex <= _____;

    else if (_____) newOneIndex <= _____;

    else if (_____) newOneIndex <= _____;

  endrule

  method Bit#(4) getOutput();
    // fill in missing code for this method

  endmethod
endmodule
```