

Combinational Logic and Introduction to Minispec

Combinational Logic and Introduction to Minispec

Reminders:

Quiz 1 review tonight 7:30-9:30pm

Quiz 1 on Thursday 7:30-9:30pm

Lecture Goals


- Learn how to design large combinational circuits through three useful examples:
 - Adder
 - Multiplexers
 - Shifter

Lecture Goals

- Learn how to design large combinational circuits through three useful examples:
 - Adder
 - Multiplexers
 - Shifter
- Learn how to implement combinational circuits in the Minispec hardware description language (HDL)
 - Design each combinational circuit as a **function**, which can be simulated or synthesized into gates


Building a Combinational Addder

 - Goal: Build a circuit that takes two n -bit inputs a and b and produces $(n+1)$ -bit output $s=a+b$




Building a Combinational Adder

 - Goal: Build a circuit that takes two n -bit inputs a and b and produces $(n+1)$ -bit output $s = a + b$



Building a Combinational Adder

 - Goal: Build a circuit that takes two n -bit inputs a and b and produces $(n+1)$ -bit output $s = a + b$




- Approach: Implement the binary addition algorithm we have seen (called the standard algorithm)

$$\begin{array}{r} 1110 \text{ — carry} \\ 1110 \\ + 0111 \\ \hline 10101 \end{array}$$

Formalizing the Standard Algorithm

carry —
 
$$\begin{array}{r} 1110 \\ 1110 \\ + 0111 \\ \hline 10101 \end{array}$$



$$\begin{array}{r} c_4 c_3 c_2 c_1 0 \\ a_3 a_2 a_1 a_0 \\ + b_3 b_2 b_1 b_0 \\ \hline s_4 s_3 s_2 s_1 s_0 \end{array}$$

Formalizing the Standard Algorithm

$$\begin{array}{r} \text{carry} \text{ --- } 1110 \\ 1110 \\ + 0111 \\ \hline 10101 \end{array} \quad \rightarrow \quad \begin{array}{r} c_4 c_3 c_2 c_1 \theta \\ a_3 a_2 a_1 a_0 \\ + b_3 b_2 b_1 b_0 \\ \hline s_4 s_3 s_2 s_1 s_0 \end{array}$$

- The i^{th} step of each addition

Formalizing the Standard Algorithm

carry — 1110

$$\begin{array}{r} 1110 \\ 1110 \\ + 0111 \\ \hline 10101 \end{array}$$

→

$$\begin{array}{r} c_4 c_3 c_2 c_1 0 \\ a_3 a_2 a_1 a_0 \\ + b_3 b_2 b_1 b_0 \\ \hline s_4 s_3 s_2 s_1 s_0 \end{array}$$

- The i^{th} step of each addition
 - Takes three 1-bit inputs: a_i , b_i , c_i (carry-in)

Formalizing the Standard Algorithm

carry —

$$\begin{array}{r} 1110 \\ 1110 \\ + 0111 \\ \hline 10101 \end{array} \quad \rightarrow \quad \begin{array}{r} c_4 c_3 c_2 c_1 0 \\ a_3 a_2 a_1 a_0 \\ + b_3 b_2 b_1 b_0 \\ \hline s_4 s_3 s_2 s_1 s_0 \end{array}$$

- The i^{th} step of each addition
 - Takes three 1-bit inputs: a_i , b_i , c_i (carry-in)
 - Produces two 1-bit outputs: s_i , c_{i+1} (carry-out)
 - The 2-bit output $c_{i+1}s_i$ is the binary sum of the three inputs

Formalizing the Standard Algorithm

carry —


$$\begin{array}{r} 1110 \\ 1110 \\ + 0111 \\ \hline 10101 \end{array} \quad \rightarrow \quad \begin{array}{r} c_4 c_3 c_2 c_1 0 \\ a_3 a_2 a_1 a_0 \\ + b_3 b_2 b_1 b_0 \\ \hline s_4 s_3 s_2 s_1 s_0 \end{array}$$

- The i^{th} step of each addition
 - Takes three 1-bit inputs: a_i , b_i , c_i (carry-in)
 - Produces two 1-bit outputs: s_i , c_{i+1} (carry-out)
 - The 2-bit output $c_{i+1}s_i$ is the binary sum of the three inputs

Can you build a circuit that performs a single step with what you've learned so far?

Combinational Logic for an Adder

 
- First, build a full adder (FA), which
 - Adds three one-bit numbers:
 a , b , and carry-in
 - Produces a sum bit and a carry-out bit




Combinational Logic for an Adder

- First, build a full adder (FA), which

 - Adds three one-bit numbers:
 a , b , and carry-in
- Produces a sum bit and a carry-out bit




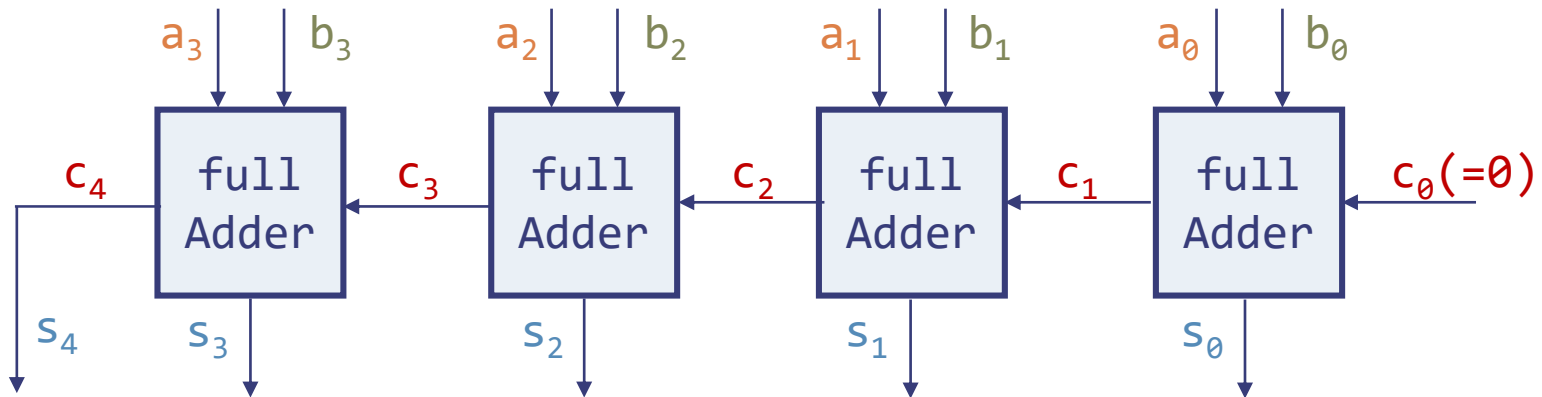- Then, cascade FAs to perform binary addition




Combinational Logic for an Adder

 - First, build a full adder (FA), which
 - Adds three one-bit numbers:
 a , b , and carry-in
 - Produces a sum bit and a carry-out bit



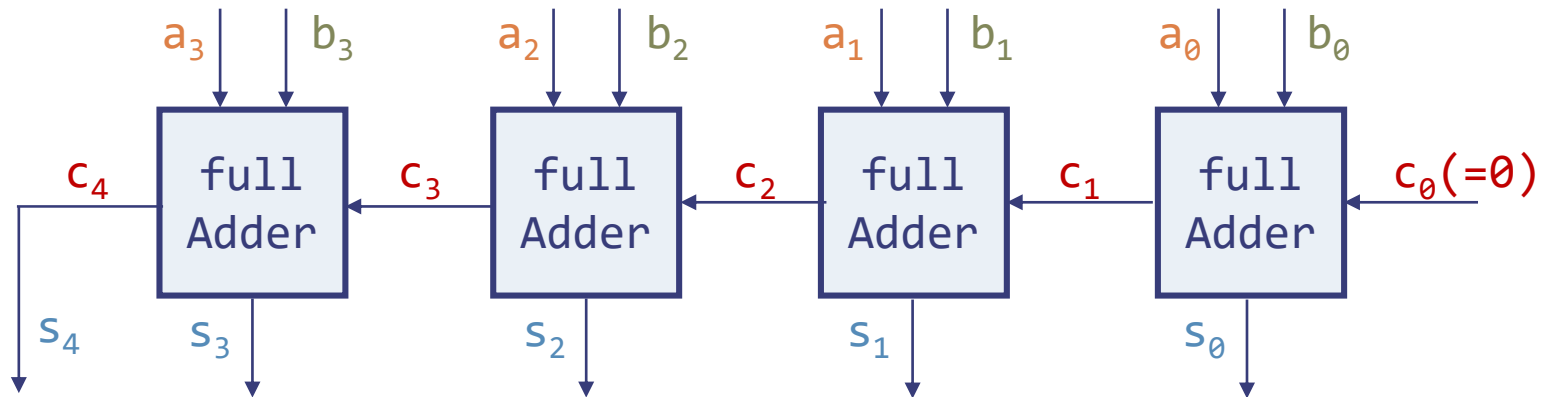- Then, cascade FAs to perform binary addition



- Result: A ripple-carry adder (simple but slow)

Deriving the Full Adder


Truth table

a	b	c _{in}	c _{out}	s
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Boolean expressions

$S =$

$C_{out} =$

 

Deriving the Full Adder


Truth table

a	b	c _{in}	c _{out}	s
0	0	0	0	0
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Boolean expressions

$S =$

$C_{out} =$

 

Deriving the Full Adder


Truth table

a	b	c _{in}	c _{out}	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1		
1	0	0	0	1
1	0	1		
1	1	0		
1	1	1		

Boolean expressions

$S =$

$C_{out} =$

 

Deriving the Full Adder


Truth table

a	b	c _{in}	c _{out}	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1		

Boolean expressions

$S =$

$C_{out} =$

 

Deriving the Full Adder


Truth table

a	b	c _{in}	c _{out}	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Boolean expressions

$S =$

$C_{out} =$

 

Deriving the Full Adder


Truth table

a	b	c _{in}	c _{out}	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Boolean expressions

$$s = a \oplus b \oplus c_{in}$$


$$c_{out} =$$

 

Deriving the Full Adder

Truth table

a	b	c _{in}	c _{out}	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Boolean expressions


$$s = a \oplus b \oplus c_{in}$$

$$c_{out} = a \cdot b + a \cdot c_{in} + b \cdot c_{in}$$

Deriving the Full Adder

Truth table

a	b	c _{in}	c _{out}	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Boolean expressions

$$s = a \oplus b \oplus c_{in}$$

$$c_{out} = a \cdot b + a \cdot c_{in} + b \cdot c_{in}$$

Describing a 32-bit Adder alternatives

- Truth table with 2^{64} rows and 33 columns

Describing a 32-bit Adder alternatives

- Truth table with 2^{64} rows and 33 columns
- 32 sets of Boolean equations, where each set describes a FA

Describing a 32-bit Adder

alternatives

- Truth table with 2^{64} rows and 33 columns
- 32 sets of Boolean equations, where each set describes a FA
- Use some ad-hoc notation to describe recurrences
 - $s_k = a_k \oplus b_k \oplus c_k$
 - $c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k$

$$\left. \begin{array}{l} s_k = a_k \oplus b_k \oplus c_k \\ c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k \end{array} \right\} 0 \leq k \leq 31$$

Describing a 32-bit Adder

alternatives

- Truth table with 2^{64} rows and 33 columns
- 32 sets of Boolean equations, where each set describes a FA
- Use some ad-hoc notation to describe recurrences
 - $s_k = a_k \oplus b_k \oplus c_k$
 - $c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k$
- Circuit diagrams: tedious to draw, error-prone

$$\left. \begin{array}{l} s_k = a_k \oplus b_k \oplus c_k \\ c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k \end{array} \right\} 0 \leq k \leq 31$$

Describing a 32-bit Adder alternatives

- Truth table with 2^{64} rows and 33 columns
- 32 sets of Boolean equations, where each set describes a FA
- Use some ad-hoc notation to describe recurrences
 - $s_k = a_k \oplus b_k \oplus c_k$
 - $c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k$
- Circuit diagrams: tedious to draw, error-prone

$$\left. \begin{array}{l} s_k = a_k \oplus b_k \oplus c_k \\ c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k \end{array} \right\} 0 \leq k \leq 31$$



Describing a 32-bit Adder alternatives

- Truth table with 2^{64} rows and 33 columns
- 32 sets of Boolean equations, where each set describes a FA
- Use some ad-hoc notation to describe recurrences
 - $s_k = a_k \oplus b_k \oplus c_k$
 - $c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k$ $\left. \vphantom{\begin{matrix} s_k = a_k \oplus b_k \oplus c_k \\ c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k \end{matrix}} \right\} 0 \leq k \leq 31$
- Circuit diagrams: tedious to draw, error-prone
- A hardware description language (HDL), *i.e.*, a programming language specialized to describe hardware




Describing a 32-bit Adder alternatives


- Truth table with 2^{64} rows and 33 columns
- 32 sets of Boolean equations, where each set describes a FA
- Use some ad-hoc notation to describe recurrences
 - $s_k = a_k \oplus b_k \oplus c_k$
 - $c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k$ $\left. \vphantom{\begin{matrix} s_k \\ c_{k+1} \end{matrix}} \right\} 0 \leq k \leq 31$
- Circuit diagrams: tedious to draw, error-prone
- A hardware description language (HDL), *i.e.*, a programming language specialized to describe hardware
 - Precisely specify the structure and behavior of digital circuits




Describing a 32-bit Adder alternatives

- Truth table with 2^{64} rows and 33 columns
 - 32 sets of Boolean equations, where each set describes a FA
 - Use some ad-hoc notation to describe recurrences
 - $s_k = a_k \oplus b_k \oplus c_k$
 - $c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k$ $\left. \vphantom{\begin{matrix} s_k \\ c_{k+1} \end{matrix}} \right\} 0 \leq k \leq 31$
 - Circuit diagrams: tedious to draw, error-prone
- 
- A hardware description language (HDL), *i.e.*, a programming language specialized to describe hardware
 - Precisely specify the structure and behavior of digital circuits
 - Designs can be automatically simulated or synthesized to hardware


Describing a 32-bit Adder alternatives

- Truth table with 2^{64} rows and 33 columns
 - 32 sets of Boolean equations, where each set describes a FA
 - Use some ad-hoc notation to describe recurrences
 - $s_k = a_k \oplus b_k \oplus c_k$
 - $c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k$ $\left. \vphantom{\begin{matrix} s_k = a_k \oplus b_k \oplus c_k \\ c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k \end{matrix}} \right\} 0 \leq k \leq 31$
 - Circuit diagrams: tedious to draw, error-prone
- 
- A hardware description language (HDL), *i.e.*, a programming language specialized to describe hardware
 - Precisely specify the structure and behavior of digital circuits
 - Designs can be automatically simulated or synthesized to hardware
 - Enables building hardware with same principles used to build software (write and compose simple, reusable building blocks)

Describing a 32-bit Adder alternatives

- Truth table with 2^{64} rows and 33 columns
- 32 sets of Boolean equations, where each set describes a FA
- Use some ad-hoc notation to describe recurrences
 - $s_k = a_k \oplus b_k \oplus c_k$
 - $c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k$
- Circuit diagrams: tedious to draw, error-prone
- A hardware description language (HDL), *i.e.*, a programming language specialized to describe hardware
 - Precisely specify the structure and behavior of digital circuits
 - Designs can be automatically simulated or synthesized to hardware
 - Enables building hardware with same principles used to build software (write and compose simple, reusable building blocks)
 - Uses a familiar syntax (functions, variables, control-flow statements, etc.)

Describing a 32-bit Adder alternatives

- Truth table with 2^{64} rows and 33 columns
- 32 sets of Boolean equations, where each set describes a FA
- Use some ad-hoc notation to describe recurrences
 - $s_k = a_k \oplus b_k \oplus c_k$
 - $c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k$

$\} \quad 0 \leq k \leq 31$
- Circuit diagrams: tedious to draw, error-prone
- A hardware description language (HDL), *i.e.*, a programming language specialized to describe hardware
 - Precisely specify the structure and behavior of digital circuits
 - Designs can be automatically simulated or synthesized to hardware
 - Enables building hardware with same principles used to build software (write and compose simple, reusable building blocks)
 - Uses a familiar syntax (functions, variables, control-flow statements, etc.)

But be aware of the differences!

Introduction to Minispec

A simple HDL based on Bluespec

Combinational Logic as Functions

- In Minispec, combinational circuits are described using functions

```
function Bool inv(Bool x);  
    Bool result = !x;  
    return result;  
endfunction
```

Combinational Logic as Functions

- In Minispec, combinational circuits are described using functions

Function name


```
function Bool inv(Bool x);  
    Bool result = !x;  
    return result;  
endfunction
```

Combinational Logic as Functions

- In Minispec, combinational circuits are described using functions

Return type Function name
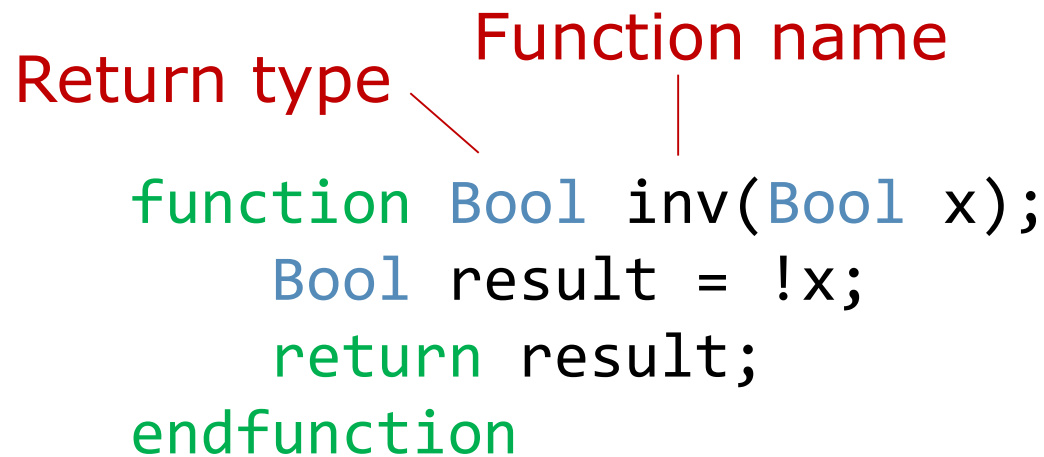
```
function Bool inv(Bool x);  
    Bool result = !x;  
    return result;  
endfunction
```



Combinational Logic as Functions

- In Minispec, combinational circuits are described using functions

Return type Function name Input arguments

```
function Bool inv(Bool x);  
    Bool result = !x;  
    return result;  
endfunction
```

Combinational Logic as Functions

- In Minispec, combinational circuits are described using functions

Return type Function name Input arguments

```
function Bool inv(Bool x);  
    Bool result = !x;  
    return result;  
endfunction
```

Statement(s),
including a return
statement

Combinational Logic as Functions

- In Minispec, combinational circuits are described using functions

Return type Function name Input arguments

```
function Bool inv(Bool x);  
    Bool result = !x;  
    return result;  
endfunction
```

Statement(s),
including a return
statement

- All values have a fixed type, which is known statically (e.g., result is of type Bool)

Combinational Logic as Functions

- In Minispec, combinational circuits are described using functions

Return type Function name Input arguments

```
function Bool inv(Bool x);  
    Bool result = !x;  
    return result;  
endfunction
```

Statement(s),
including a return
statement

- All values have a fixed type, which is known statically (e.g., result is of type Bool)
- Note: Types Start With An Uppercase Letter, variable and function names are lowercase

Bool Type and Operations

- Values of type `Bool` can be `True` or `False`
- `Bool` supports Boolean and comparison operations:

```
Bool a = True;
```

```
Bool b = False;
```

```
Bool x = !a;      // False since a == True
```

```
Bool y = a && b;   // False since b == False
```

```
Bool z = a || b;  // True since a == True
```

```
Bool n = a != b;  // True; equivalent to XOR
```

```
Bool e = a == b;  // False; equivalent to XNOR
```

Bool Type and Operations

- Values of type `Bool` can be `True` or `False`
- `Bool` supports Boolean and comparison operations:

```
Bool a = True;  
Bool b = False;
```

```
Bool x = !a;      // False since a == True  
Bool y = a && b;   // False since b == False  
Bool z = a || b;  // True since a == True
```

```
Bool n = a != b;  // True; equivalent to XOR  
Bool e = a == b;  // False; equivalent to XNOR
```

- `Bool` is the simplest type, but working with many single-bit values is tedious
 - Need a type that represents multi-bit values!

Bit#(n) Type and Operations

- Bit#(n) represents an n-bit value
- Bit#(n) supports the following basic operations:
 - Bitwise logical: \sim (negation), $\&$ (AND), $|$ (OR), \wedge (XOR)

```
Bit#(4) a = 4'b0011; // 4-bit binary 3
Bit#(4) b = 4'b0101; // 4-bit binary 5
Bit#(4) x = ~a;      // 4'b1100
Bit#(4) y = a & b;   // 4'b0001
Bit#(4) z = a ^ b;   // 4'b0110
```

Bit#(n) Type and Operations

- Bit#(n) represents an n-bit value
- Bit#(n) supports the following basic operations:
 - Bitwise logical: \sim (negation), $\&$ (AND), $|$ (OR), \wedge (XOR)

```
Bit#(4) a = 4'b0011; // 4-bit binary 3
```

```
Bit#(4) b = 4'b0101; // 4-bit binary 5
```

```
Bit#(4) x = ~a; // 4'b1100
```

```
Bit#(4) y = a & b; // 4'b0001
```

```
Bit#(4) z = a ^ b; // 4'b0110
```

- Bit selection

```
Bit#(1) l = a[0]; // 1'b1 (least significant)
```

```
Bit#(3) m = a[3:1]; // 3'b001
```

Bit#(n) Type and Operations

- Bit#(n) represents an n-bit value
- Bit#(n) supports the following basic operations:
 - Bitwise logical: \sim (negation), $\&$ (AND), $|$ (OR), \wedge (XOR)

```
Bit#(4) a = 4'b0011; // 4-bit binary 3
```

```
Bit#(4) b = 4'b0101; // 4-bit binary 5
```

```
Bit#(4) x = ~a; // 4'b1100
```

```
Bit#(4) y = a & b; // 4'b0001
```

```
Bit#(4) z = a ^ b; // 4'b0110
```

- Bit selection


```
Bit#(1) l = a[0]; // 1'b1 (least significant)
```

```
Bit#(3) m = a[3:1]; // 3'b001
```

- Concatenation

```
Bit#(8) c = {a, b}; // 8'b00110101
```


Full Adder in Minispec

 

$$s = a \oplus b \oplus c_{in}$$
$$c_{out} = a \cdot b + a \cdot c_{in} + b \cdot c_{in}$$

```
function Bit#(2) fullAdder(Bit#(1) a, Bit#(1) b, Bit#(1) cin);  
  
endfunction
```



Full Adder in Minispec

  

$$s = a \oplus b \oplus c_{in}$$
$$c_{out} = a \cdot b + a \cdot c_{in} + b \cdot c_{in}$$

```
function Bit#(2) fullAdder(Bit#(1) a, Bit#(1) b, Bit#(1) cin);  
    Bit#(1) s = a ^ b ^ cin;  
  
endfunction
```


Full Adder in Minispec



$$s = a \oplus b \oplus c_{in}$$
$$c_{out} = a \cdot b + a \cdot c_{in} + b \cdot c_{in}$$

```
function Bit#(2) fullAdder(Bit#(1) a, Bit#(1) b, Bit#(1) cin);  
  Bit#(1) s = a ^ b ^ cin;  
  Bit#(1) cout = (a & b) | (a & cin) | (b & cin);  
  
endfunction
```


Full Adder in Minispec

 


$$s = a \oplus b \oplus c_{in}$$
$$c_{out} = a \cdot b + a \cdot c_{in} + b \cdot c_{in}$$

```
function Bit#(2) fullAdder(Bit#(1) a, Bit#(1) b, Bit#(1) cin);  
  Bit#(1) s = a ^ b ^ cin;  
  Bit#(1) cout = (a & b) | (a & cin) | (b & cin);  
  return {cout, s};  
endfunction
```

2-bit Ripple-Carry Adder

 


2-bit Ripple-Carry Adder

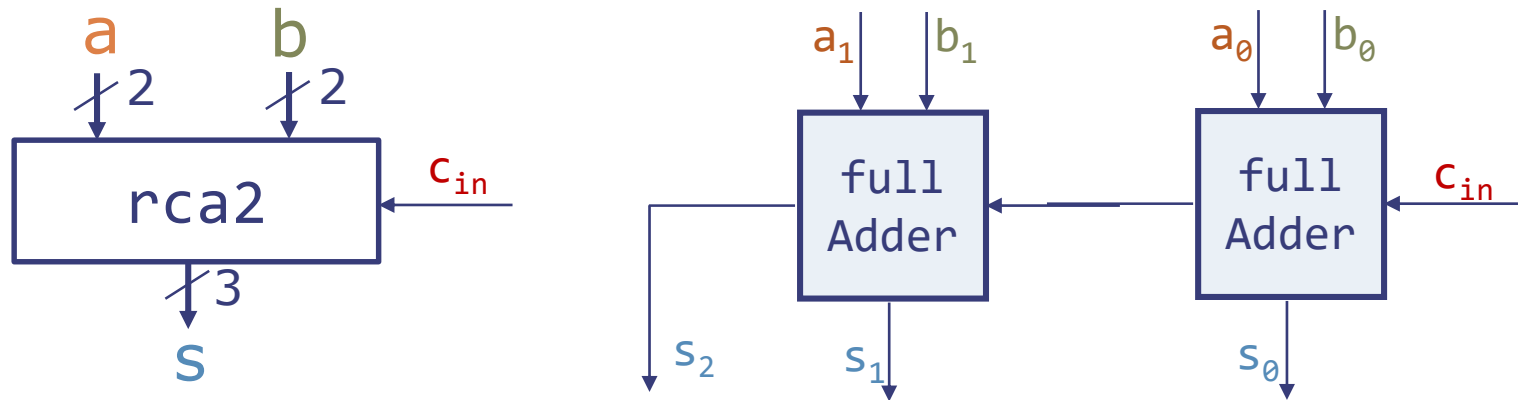

```
function Bit#(3) rca2(Bit#(2) a, Bit#(2) b, Bit#(1) cin);
```


```
endfunction
```

2-bit Ripple-Carry Adder

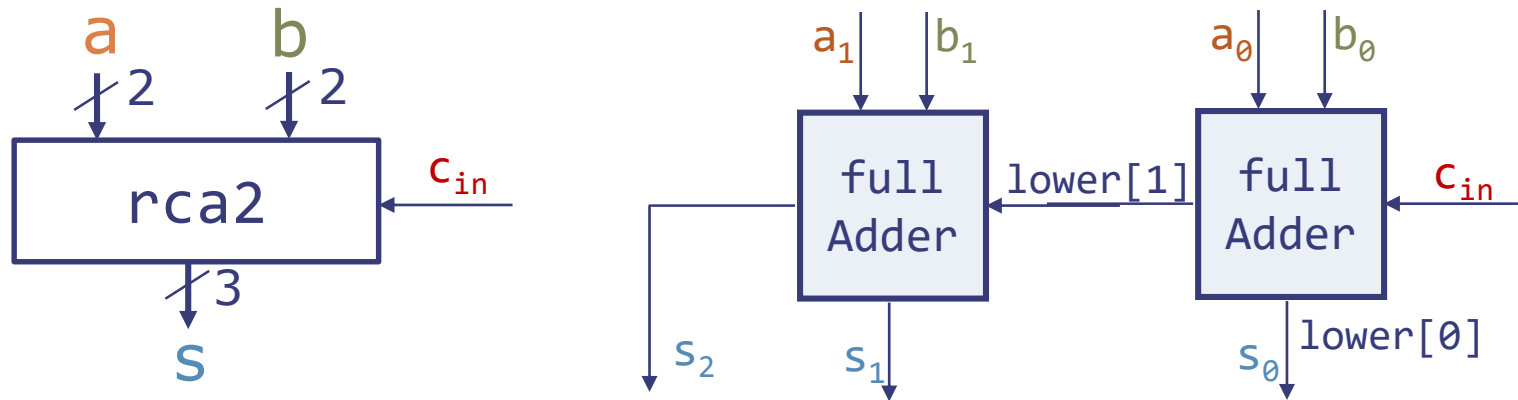


```
function Bit#(3) rca2(Bit#(2) a, Bit#(2) b, Bit#(1) cin);  
    Bit#(2) lower = fullAdder(a[0], b[0], cin);  
  
endfunction
```

2-bit Ripple-Carry Adder

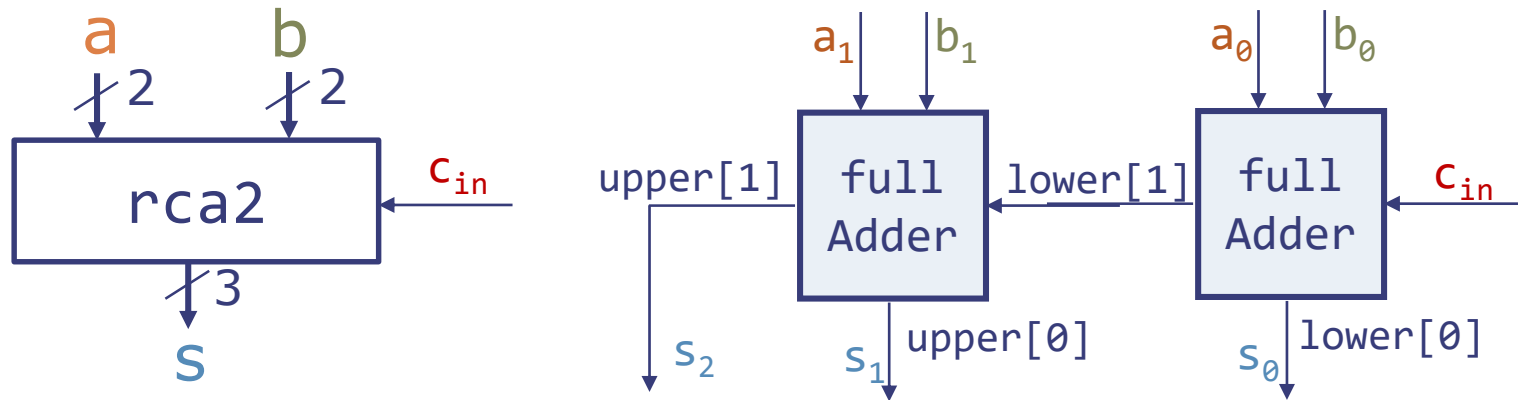


```
function Bit#(3) rca2(Bit#(2) a, Bit#(2) b, Bit#(1) cin);  
    Bit#(2) lower = fullAdder(a[0], b[0], cin);  
    Bit#(2) upper = fullAdder(a[1], b[1], lower[1]);  
  
endfunction
```

2-bit Ripple-Carry Adder

 

```
function Bit#(3) rca2(Bit#(2) a, Bit#(2) b, Bit#(1) cin);  
    Bit#(2) lower = fullAdder(a[0], b[0], cin);  
    Bit#(2) upper = fullAdder(a[1], b[1], lower[1]);  
    return {upper, lower[0]};  
endfunction
```



2-bit Ripple-Carry Adder

 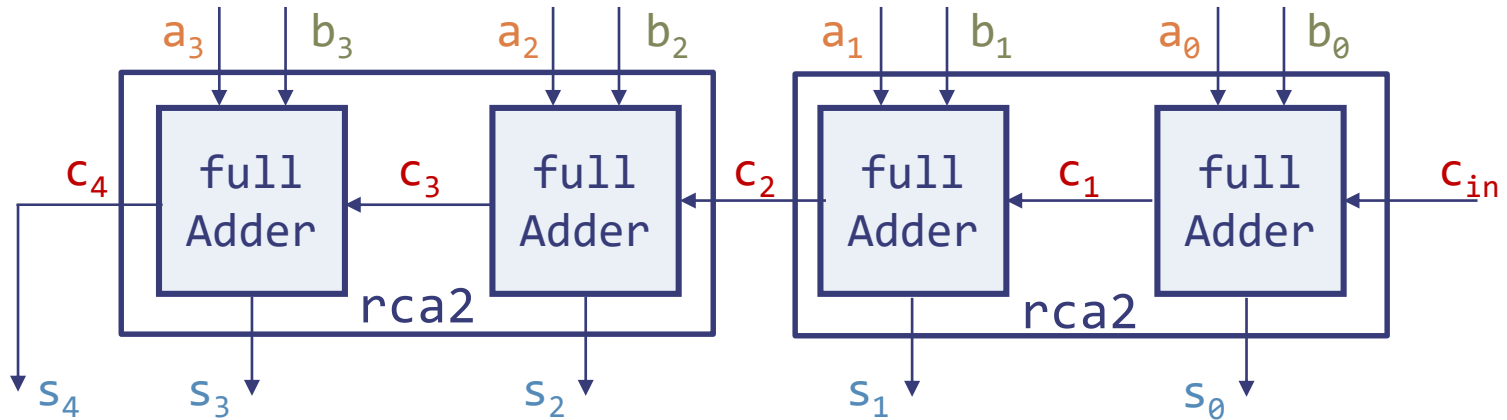

```
function Bit#(3) rca2(Bit#(2) a, Bit#(2) b, Bit#(1) cin);  
    Bit#(2) lower = fullAdder(a[0], b[0], cin);  
    Bit#(2) upper = fullAdder(a[1], b[1], lower[1]);  
    return {upper, lower[0]};  
endfunction
```


- Functions are **inlined**: Each function call creates a new instance (copy) of the called circuit
 - Allows composing simple circuits to build larger ones

4-bit Ripple-Carry Adder



```
function Bit#(5) rca4(Bit#(4) a, Bit#(4) b, Bit#(1) cin);  
    Bit#(3) lower = rca2(a[1:0], b[1:0], cin);  
    Bit#(3) upper = rca2(a[3:2], b[3:2], lower[2]);  
    return {upper, lower[1:0]};  
endfunction
```

4-bit Ripple-Carry Adder

 


```
function Bit#(5) rca4(Bit#(4) a, Bit#(4) b, Bit#(1) cin);  
  Bit#(3) lower = rca2(a[1:0], b[1:0], cin);  
  Bit#(3) upper = rca2(a[3:2], b[3:2], lower[2]);  
  return {upper, lower[1:0]};  
endfunction
```

- Composing functions lets us build larger circuits, but writing very large circuits this way is tedious
 - Next lecture: Writing an n-bit adder in a single function

Multiplexers


2-way Multiplexer

 - A 2-way multiplexer or mux selects between two inputs a and b based on a single-bit input s (select input)




2-way Multiplexer

 - A 2-way multiplexer or mux selects between two inputs a and b based on a single-bit input s (select input)




- Gate-level implementation:

 


2-way Multiplexer with n -bit inputs

 - If a and b are n -bit wide, the 2-way multiplexer can be implemented with n one-bit 2-way multiplexers in parallel
 - s is the same input for all the replicated structures




2-way Multiplexer with n -bit inputs

 - If a and b are n -bit wide, the 2-way multiplexer can be implemented with n one-bit 2-way multiplexers in parallel
 - s is the same input for all the replicated structures





4-way Multiplexer

 - A 4-way multiplexer selects between four inputs based on the value of a 2-bit input s




4-way Multiplexer

  - A 4-way multiplexer selects between four inputs based on the value of a 2-bit input s
- Typically implemented using 2-way multiplexers




k -way Multiplexer

 - A k -way multiplexer can be implemented with a tree of $k-1$ 2-way multiplexers



k -way Multiplexer

 
- A k -way multiplexer can be implemented with a tree of $k-1$ 2-way multiplexers
 - Example: 8-way multiplexer



k -way Multiplexer

- A k -way multiplexer can be implemented with a tree of $k-1$ 2-way multiplexers
 - Example: 8-way multiplexer

 How many 2-way one-bit muxes needed to implement a k -way n -bit mux?




k -way Multiplexer

- A k -way multiplexer can be implemented with a tree of $k-1$ 2-way multiplexers
 - Example: 8-way multiplexer


How many 2-way one-bit muxes needed to implement a k -way n -bit mux?

$$(k-1)*n$$

 


Multiplexers in Minispec

 - 2-way mux \rightarrow Conditional operator



Multiplexers in Minispec

- 2-way mux → Conditional operator

 


Minispec

`s? b : a`

Multiplexers in Minispec

- 2-way mux → Conditional operator

 


Minispec

`s? b : a`

s has type **Bool**; True is treated as 1 and False as 0

Multiplexers in Minispec

- 2-way mux → Conditional operator

 

Minispec

`s? b : a`


Python

`b if s else a`

s has type **Bool**; True is treated as 1 and False as 0

Multiplexers in Minispec

- 2-way mux → Conditional operator

 

Minispec


```
s? b : a
```

Python

```
b if s else a
```


s has type **Bool**; True is treated as 1 and False as 0

- k -way mux → Case expression

 

Multiplexers in Minispec

- 2-way mux → Conditional operator

 

Minispec


```
s? b : a
```

Python

```
b if s else a
```

s has type **Bool**; True is treated as 1 and False as 0

- k*-way mux → Case expression

 


Minispec

```
case (s)
  0 : a;
  1 : b;
  2 : c;
  3 : d;
endcase
```

Multiplexers in Minispec

- 2-way mux → Conditional operator

 

Minispec


```
s? b : a
```

Python

```
b if s else a
```

s has type **Bool**; True is treated as 1 and False as 0

- k-way mux → Case expression

 

Minispec

```
case (s)
  0 : a;
  1 : b;
  2 : c;
  3 : d;
endcase
```

s has type **Bit#(2)**

Aside: No Conditional Execution!

- Given this conditional statement...

$s? \text{ foo}(x) : \text{ bar}(y)$

Aside: No Conditional Execution!

- Given this conditional statement...

$s? \text{foo}(x) : \text{bar}(y)$

- In software, the program would first evaluate s , then run **either $\text{foo}(x)$ or $\text{bar}(y)$**

Aside: No Conditional Execution!

- Given this conditional statement...

$s? \text{foo}(x) : \text{bar}(y)$


- In software, the program would first evaluate s , then run **either $\text{foo}(x)$ or $\text{bar}(y)$**
- But in hardware, this statement instantiates and evaluates **both $\text{foo}(x)$ and $\text{bar}(y)$** , in parallel!

Aside: No Conditional Execution!

- Given this conditional statement...

$s? \text{foo}(x) : \text{bar}(y)$

 
- In software, the program would first evaluate s , then run **either $\text{foo}(x)$ or $\text{bar}(y)$**
- But in hardware, this statement instantiates and evaluates **both $\text{foo}(x)$ and $\text{bar}(y)$** , in parallel!



Selecting a Wire: $x[i]$

assume x is 4 bits wide



- Constant selector: e.g., $x[2]$

 

Selecting a Wire: $x[i]$

assume x is 4 bits wide



- Constant selector: e.g., $x[2]$

  

Selecting a Wire: $x[i]$

assume x is 4 bits wide

- Constant selector: e.g., $x[2]$

 
 


no hardware;
 $x[2]$ is just
the name of
a wire

Selecting a Wire: $x[i]$


assume x is 4 bits wide

- Constant selector: e.g., $x[2]$

  

no hardware;
 $x[2]$ is just
the name of
a wire



- Dynamic selector: $x[i]$

 

Selecting a Wire: $x[i]$



assume x is 4 bits wide

- Constant selector: e.g., $x[2]$

  

no hardware;
 $x[2]$ is just
the name of
a wire


- Dynamic selector: $x[i]$

  

4-way
mux



Shift operators

Fixed-Size Shifts

 


- Fixed-size shift operation is cheap in hardware
 - Just wire the circuit appropriately

Fixed-Size Shifts

  


- Fixed-size shift operation is cheap in hardware
 - Just wire the circuit appropriately

Fixed-Size Shifts

 


- Fixed-size shift operation is cheap in hardware
 - Just wire the circuit appropriately




Fixed-Size Shifts

 

 - Fixed-size shift operation is cheap in hardware
 - Just wire the circuit appropriately
- Arithmetic shifts are similar




Fixed-Size Shifts

   


- Fixed-size shift operation is cheap in hardware
 - Just wire the circuit appropriately
- Arithmetic shifts are similar

 Arithmetic right shift by n divides integer in two's complement representation by 2^n




Fixed-Size Shifts

 

- Fixed-size shift operation is cheap in hardware
 - Just wire the circuit appropriately
- Arithmetic shifts are similar

 Arithmetic right shift
by n divides integer
in two's complement
representation by 2^n



Logical Right Shift by s


- Suppose we want a shifter that right-shifts an N -bit input x by s , where $N=32$ and $0 \leq s \leq 31$

Logical Right Shift by s

- Suppose we want a shifter that right-shifts an N -bit input x by s , where $N=32$ and $0 \leq s \leq 31$
- Naïve approach: Create 32 different fixed-size shifters and select using a mux


Logical Right Shift by s

 - Suppose we want a shifter that right-shifts an N -bit input x by s , where $N=32$ and $0 \leq s \leq 31$
- Naïve approach: Create 32 different fixed-size shifters and select using a mux



Logical Right Shift by s

 
- Suppose we want a shifter that right-shifts an N -bit input x by s , where $N=32$ and $0 \leq s \leq 31$
- Naïve approach: Create 32 different fixed-size shifters and select using a mux



How many 2-way 1-bit muxes are needed to implement this 32-way 32-bit mux?

Logical Right Shift by s

 - Suppose we want a shifter that right-shifts an N -bit input x by s , where $N=32$ and $0 \leq s \leq 31$
- Naïve approach: Create 32 different fixed-size shifters and select using a mux




How many 2-way 1-bit muxes are needed to implement this 32-way 32-bit mux?

 (32-1)

Logical Right Shift by s

- Suppose we want a shifter that right-shifts an N -bit input x by s , where $N=32$ and $0 \leq s \leq 31$
- Naïve approach: Create 32 different fixed-size shifters and select using a mux




How many 2-way 1-bit muxes are needed to implement this 32-way 32-bit mux?

$$(32-1) * 32 = 992$$

Logical Right Shift by s

 - Suppose we want a shifter that right-shifts an N -bit input x by s , where $N=32$ and $0 \leq s \leq 31$
- Naïve approach: Create 32 different fixed-size shifters and select using a mux




How many 2-way 1-bit muxes are needed to implement this 32-way 32-bit mux?

$$\begin{aligned}(32-1) * 32 &= 992 \\ &= \sim 4k \text{ gates}\end{aligned}$$

Logical Right Shift by s

 - Suppose we want a shifter that right-shifts an N -bit input x by s , where $N=32$ and $0 \leq s \leq 31$
- Naïve approach: Create 32 different fixed-size shifters and select using a mux



How many 2-way 1-bit muxes are needed to implement this 32-way 32-bit mux?

$$(32-1) * 32 = 992 \\ = \sim 4k \text{ gates}$$

We can do better!

Barrel Shifter

An efficient circuit to perform variable-size shifts

- A barrel shifter performs shift by s using a series of fixed-size power-of-2 shifts

Barrel Shifter

An efficient circuit to perform variable-size shifts

- A barrel shifter performs shift by s using a series of fixed-size power-of-2 shifts
 - For example, shift by 5 ($=4+1$) can be done with shifts of sizes 4 and 1

Barrel Shifter


An efficient circuit to perform variable-size shifts

- A barrel shifter performs shift by s using a series of fixed-size power-of-2 shifts
 - For example, shift by 5 ($=4+1$) can be done with shifts of sizes 4 and 1
 - The bit encoding of s tells us which shifts are needed: if the i^{th} bit of n is 1, then we need to shift by 2^i
 - Ex: $5 = 0b00101$

Barrel Shifter

An efficient circuit to perform variable-size shifts

- A barrel shifter performs shift by s using a series of fixed-size power-of-2 shifts
 - For example, shift by 5 ($=4+1$) can be done with shifts of sizes 4 and 1
 - The bit encoding of s tells us which shifts are needed: if the i^{th} bit of n is 1, then we need to shift by 2^i
 - Ex: $5 = 0b00101$
 - Implementation: A cascade of $\log_2 N$ muxes that choose between shifting by 2^i and not shifting

 


Barrel Shifter

An efficient circuit to perform variable-size shifts

- A barrel shifter performs shift by s using a series of fixed-size power-of-2 shifts
 - For example, shift by 5 ($=4+1$) can be done with shifts of sizes 4 and 1
 - The bit encoding of s tells us which shifts are needed: if the i^{th} bit of n is 1, then we need to shift by 2^i
 - Ex: $5 = 0b00101$
 - Implementation: A cascade of $\log_2 N$ muxes that choose between shifting by 2^i and not shifting

How many 2-way 1-bit muxes?

 


Barrel Shifter

An efficient circuit to perform variable-size shifts

- A barrel shifter performs shift by s using a series of fixed-size power-of-2 shifts
 - For example, shift by 5 ($=4+1$) can be done with shifts of sizes 4 and 1
 - The bit encoding of s tells us which shifts are needed: if the i^{th} bit of n is 1, then we need to shift by 2^i
 - Ex: $5 = 0b00101$
 - Implementation: A cascade of $\log_2 N$ muxes that choose between shifting by 2^i and not shifting


How many 2-way 1-bit muxes?

$$N * \log_2 N = 32 * 5 = 160$$

 


Barrel Shifter Implementation

 - Example in Minispec for N=4
 - Only need 2 bits for s, why?



Barrel Shifter Implementation

 - Example in Minispec for N=4
 - Only need 2 bits for s, why?




```
function Bit#(4) barrelShifter(Bit#(4) x, Bit#(2) s);
```

```
endfunction
```

Barrel Shifter Implementation

 - Example in Minispec for N=4
 - Only need 2 bits for s, why?
- Use conditional operator for 2-way muxes




```
function Bit#(4) barrelShifter(Bit#(4) x, Bit#(2) s);
```

```
endfunction
```

Barrel Shifter Implementation

 - Example in Minispec for N=4
 - Only need 2 bits for s, why?
- Use conditional operator for 2-way muxes
- Use concatenation and bit selection for fixed shifts




```
function Bit#(4) barrelShifter(Bit#(4) x, Bit#(2) s);
```

```
endfunction
```

Barrel Shifter Implementation

 - Example in Minispec for N=4
 - Only need 2 bits for s, why?
- Use conditional operator for 2-way muxes
- Use concatenation and bit selection for fixed shifts




```
function Bit#(4) barrelShifter(Bit#(4) x, Bit#(2) s);  
    Bit#(4) r1 = (s[1] == 0) ? x : {2'b00, x[3:2]};
```

```
endfunction
```


Barrel Shifter Implementation

 
- Example in Minispec for N=4
 - Only need 2 bits for s, why?
- Use conditional operator for 2-way muxes
- Use concatenation and bit selection for fixed shifts



```
function Bit#(4) barrelShifter(Bit#(4) x, Bit#(2) s);  
    Bit#(4) r1 = (s[1] == 0) ? x : {2'b00, x[3:2]};  
    Bit#(4) r0 = (s[0] == 0) ? r1 : {1'b0, r1[3:1]};  
  
endfunction
```

Barrel Shifter Implementation

 - Example in Minispec for N=4
 - Only need 2 bits for s, why?
- Use conditional operator for 2-way muxes
- Use concatenation and bit selection for fixed shifts



```
function Bit#(4) barrelShifter(Bit#(4) x, Bit#(2) s);  
    Bit#(4) r1 = (s[1] == 0) ? x : {2'b00, x[3:2]};  
    Bit#(4) r0 = (s[0] == 0) ? r1 : {1'b0, r1[3:1]};  
    return r0;  
endfunction
```

Thank you!

Next lecture:
Complex combinational circuits
and advanced Minispec