

Complex Combinational Logic: Implementation and Design Tradeoffs


Lecture Goals

- Learn some advanced Minispec features that enable implementing large circuits succinctly
 - Parametric functions
 - Type inference and user-defined types
 - Loops and control-flow statements


Lecture Goals

- Learn some advanced Minispec features that enable implementing large circuits succinctly
 - Parametric functions
 - Type inference and user-defined types
 - Loops and control-flow statements
- Study design tradeoffs in combinational logic by analyzing different adder implementations

Reminder: 4-bit Ripple-Carry Adder

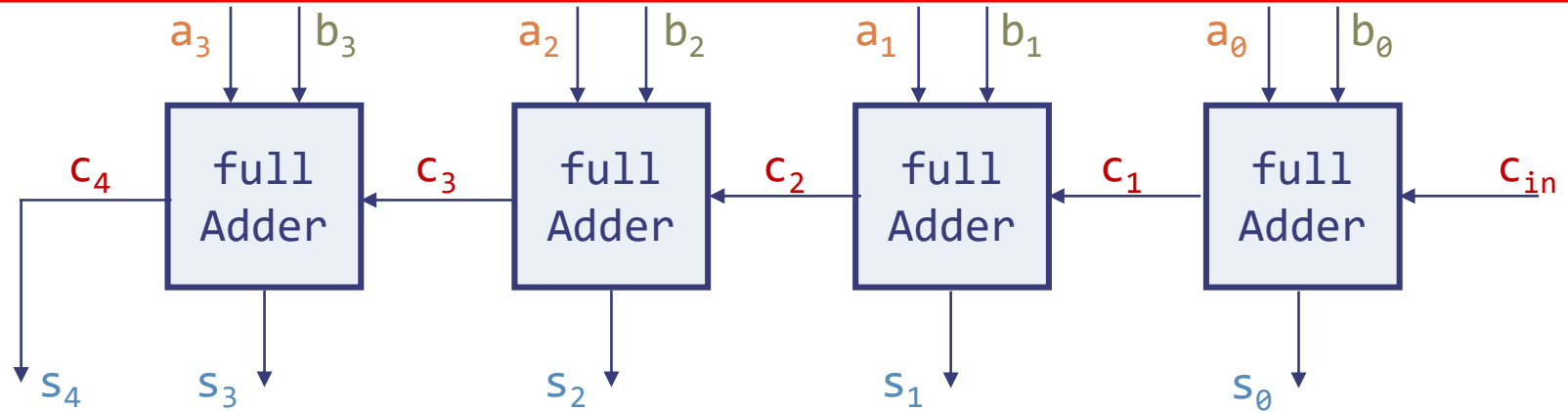


Reminder: 4-bit Ripple-Carry Adder

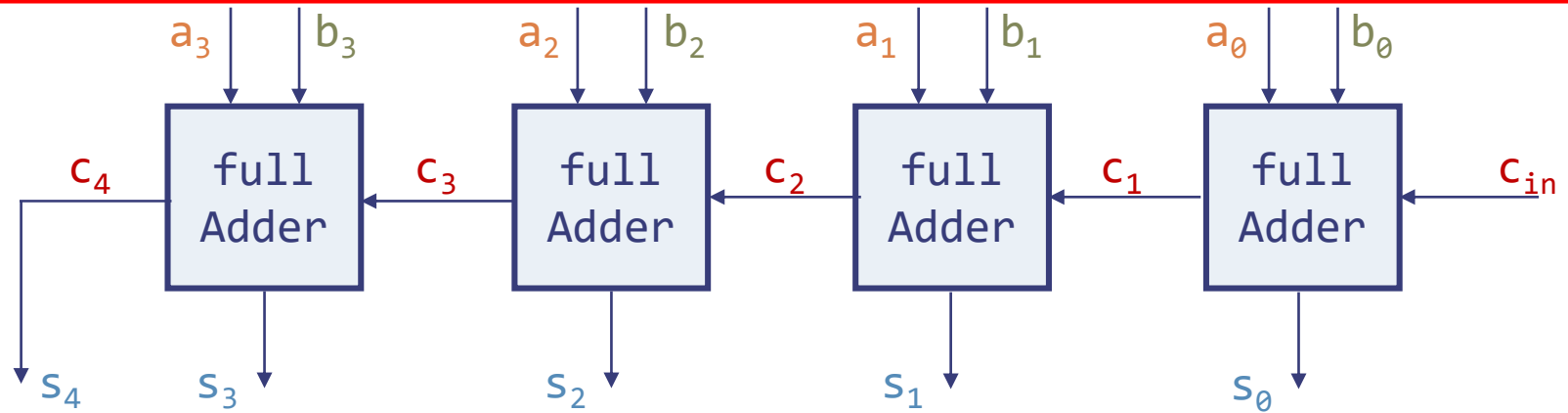


```
function Bit#(2) fullAdder(Bit#(1) a, Bit#(1) b, Bit#(1) cin);  
    Bit#(1) s = a ^ b ^ cin;  
    Bit#(1) cout = (a & b) | (a & cin) | (b & cin);  
    return {cout, s};  
endfunction
```

Reminder: 4-bit Ripple-Carry Adder

 

```
function Bit#(2) fullAdder(Bit#(1) a, Bit#(1) b, Bit#(1) cin);  
    Bit#(1) s = a ^ b ^ cin;  
    Bit#(1) cout = (a & b) | (a & cin) | (b & cin);  
    return {cout, s};  
endfunction
```


Reminder: 4-bit Ripple-Carry Adder

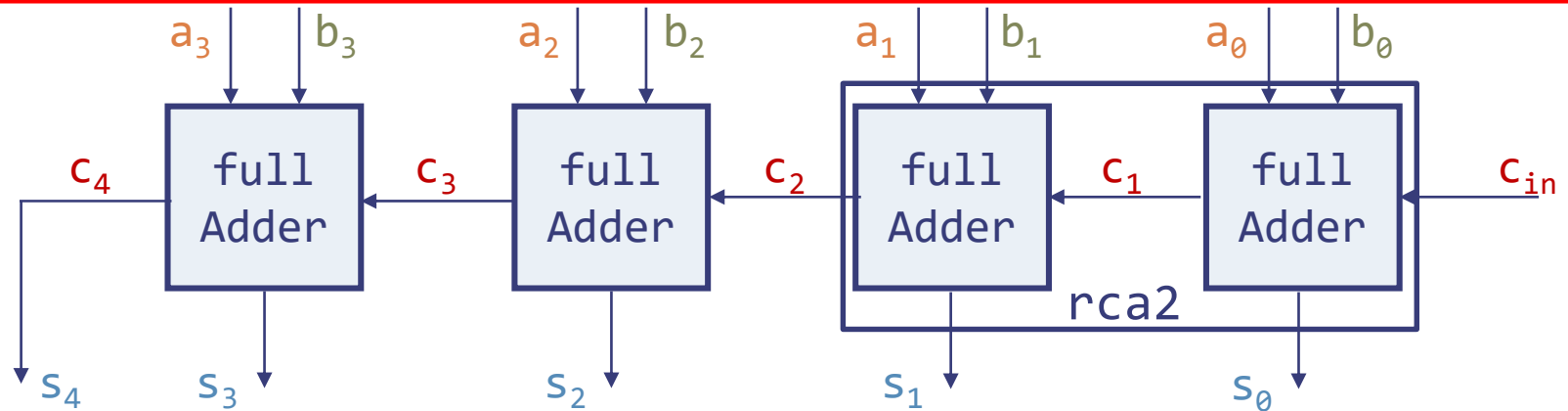

```
function Bit#(2) fullAdder(Bit#(1) a, Bit#(1) b, Bit#(1) cin);
    Bit#(1) s = a ^ b ^ cin;
    Bit#(1) cout = (a & b) | (a & cin) | (b & cin);
    return {cout, s};
endfunction

function Bit#(3) rca2(Bit#(2) a, Bit#(2) b, Bit#(1) cin);
    Bit#(2) lower = fullAdder(a[0], b[0], cin);
    Bit#(2) upper = fullAdder(a[1], b[1], lower[1]);
    return {upper, lower[0]};
endfunction
```


Reminder: 4-bit Ripple-Carry Adder

 

```
function Bit#(2) fullAdder(Bit#(1) a, Bit#(1) b, Bit#(1) cin);
    Bit#(1) s = a ^ b ^ cin;
    Bit#(1) cout = (a & b) | (a & cin) | (b & cin);
    return {cout, s};
endfunction


function Bit#(3) rca2(Bit#(2) a, Bit#(2) b, Bit#(1) cin);
    Bit#(2) lower = fullAdder(a[0], b[0], cin);
    Bit#(2) upper = fullAdder(a[1], b[1], lower[1]);
    return {upper, lower[0]};
endfunction
```


Reminder: 4-bit Ripple-Carry Adder

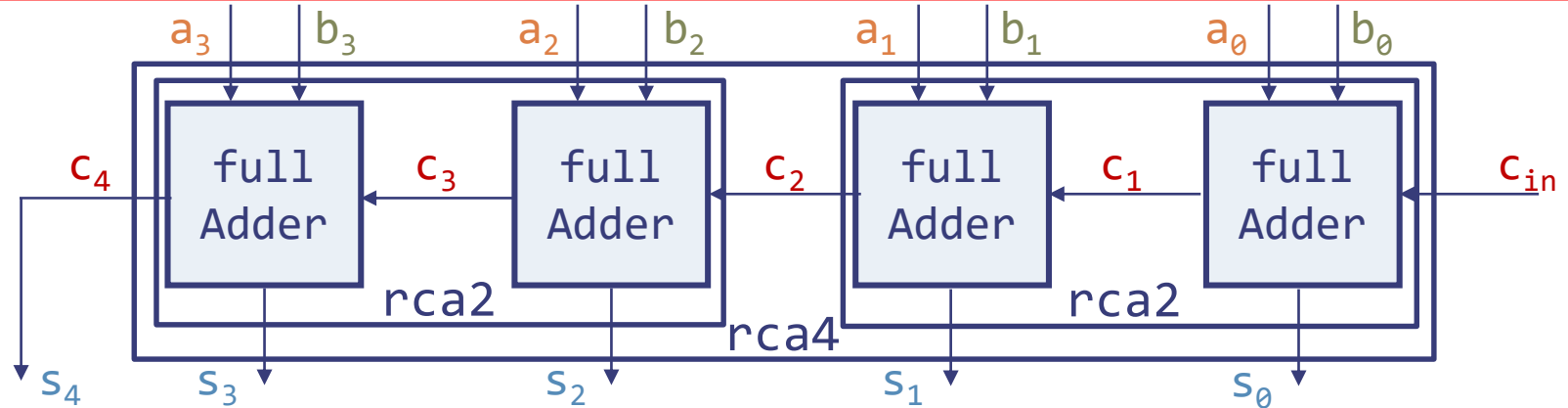

```
function Bit#(2) fullAdder(Bit#(1) a, Bit#(1) b, Bit#(1) cin);  
    Bit#(1) s = a ^ b ^ cin;  
    Bit#(1) cout = (a & b) | (a & cin) | (b & cin);  
    return {cout, s};  
endfunction  
  
function Bit#(3) rca2(Bit#(2) a, Bit#(2) b, Bit#(1) cin);  
    Bit#(2) lower = fullAdder(a[0], b[0], cin);  
    Bit#(2) upper = fullAdder(a[1], b[1], lower[1]);  
    return {upper, lower[0]};  
endfunction
```

Reminder: 4-bit Ripple-Carry Adder

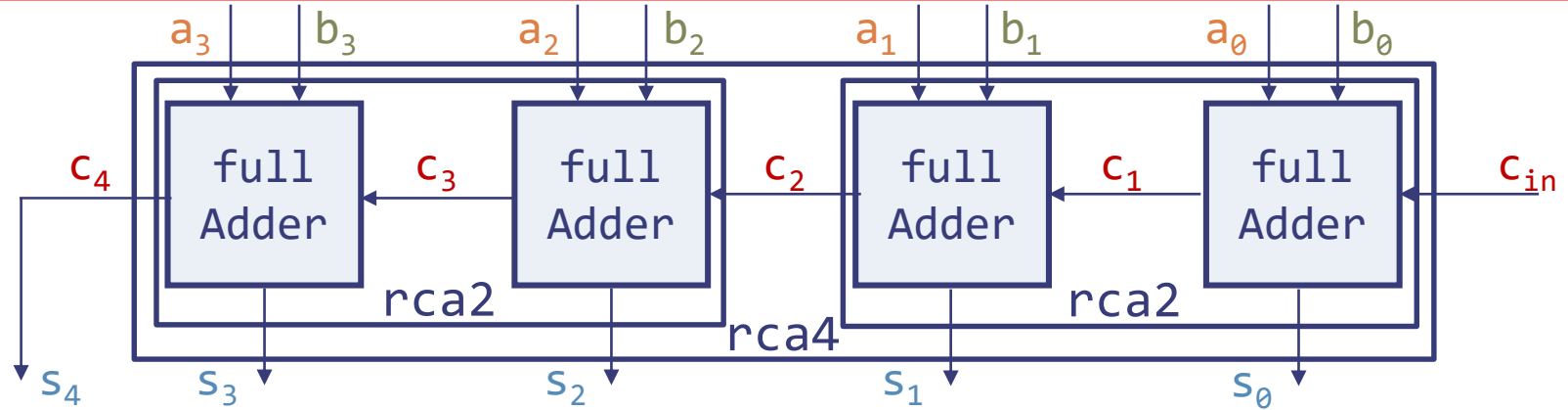


```
function Bit#(2) fullAdder(Bit#(1) a, Bit#(1) b, Bit#(1) cin);
    Bit#(1) s = a ^ b ^ cin;
    Bit#(1) cout = (a & b) | (a & cin) | (b & cin);
    return {cout, s};
endfunction

function Bit#(3) rca2(Bit#(2) a, Bit#(2) b, Bit#(1) cin);
    Bit#(2) lower = fullAdder(a[0], b[0], cin);
    Bit#(2) upper = fullAdder(a[1], b[1], lower[1]);
    return {upper, lower[0]};
endfunction

function Bit#(5) rca4(Bit#(4) a, Bit#(4) b, Bit#(1) cin);
    Bit#(3) lower = rca2(a[1:0], b[1:0], cin);
    Bit#(3) upper = rca2(a[3:2], b[3:2], lower[2]);
    return {upper, lower[1:0]};
endfunction
```

Reminder: 4-bit Ripple-Carry Adder

 

```
function Bit#(2) fullAdder(Bit#(1) a, Bit#(1) b, Bit#(1) cin);
```

```
    Bit#(1) s = a ^ b ^ cin;
```

```
    Bit#(1) cout = (a & b) | (a & cin) | (b & cin);
```

```
    return {cout, s};
```

```
endfunction
```

```
function Bit#(3) rca2(Bit#(2) a, Bit#(2) b, Bit#(1) cin);
```

```
    Bit#(2) lower = fullAdder(a[0], b[0], cin);
```

```
    Bit#(2) upper = fullAdder(a[1], b[1], lower[1]);
```

```
    return {upper, lower[0]};
```

```
endfunction
```

```
function Bit#(5) rca4(Bit#(4) a, Bit#(4) b, Bit#(1) cin);
```

```
    Bit#(3) lower = rca2(a[1:0], b[1:0], cin);
```


```
    Bit#(3) upper = rca2(a[3:2], b[3:2], lower[2]);
```

```
    return {upper, lower[1:0]};
```

```
endfunction
```

- Problem 1: Have to write a function for every bit width

Reminder: 4-bit Ripple-Carry Adder

 

```
function Bit#(2) fullAdder(Bit#(1) a, Bit#(1) b, Bit#(1) cin);  
    Bit#(1) s = a ^ b ^ cin;  
    Bit#(1) cout = (a & b) | (a & cin) | (b & cin);  
    return {cout, s};  
endfunction  
  
function Bit#(3) rca2(Bit#(2) a, Bit#(2) b, Bit#(1) cin);  
    Bit#(2) lower = fullAdder(a[0], b[0], cin);  
    Bit#(2) upper = fullAdder(a[1], b[1], lower[1]);  
    return {upper, lower[0]};  
endfunction  
  
function Bit#(5) rca4(Bit#(4) a, Bit#(4) b, Bit#(1) cin);  
    Bit#(3) lower = rca2(a[1:0], b[1:0], cin);  
    Bit#(3) upper = rca2(a[3:2], b[3:2], lower[2]);  
    return {upper, lower[1:0]};  
endfunction
```

- Problem 1: Have to write a function for every bit width
- Problem 2: If we build large functions from smaller ones, have to write many functions!

Parametric Types

- $\text{Bit\#}(n)$, an n -bit value, is a **parametric type**
 - n is the **parameter** (an Integer value)
 - Using $\text{Bit\#}(n)$ requires specifying a fixed n (e.g., $\text{Bit\#}(4)$ is a 4-bit value)

Parametric Types

- $\text{Bit\#}(n)$, an n -bit value, is a **parametric type**
 - n is the **parameter** (an Integer value)
 - Using $\text{Bit\#}(n)$ requires specifying a fixed n (e.g., $\text{Bit\#}(4)$ is a 4-bit value)
- Minispec provides other parametric types, and lets you define your own

Parametric Types

- $\text{Bit\#}(n)$, an n -bit value, is a **parametric type**
 - n is the **parameter** (an Integer value)
 - Using $\text{Bit\#}(n)$ requires specifying a fixed n (e.g., $\text{Bit\#}(4)$ is a 4-bit value)
- Minispec provides other parametric types, and lets you define your own
 - Parametric types are *generic*
 - They take one or more parameters
 - Parameters must be known at compile-time
 - Specifying the parameters yields a *concrete* type

Parametric Types

- $\text{Bit}\#(n)$, an n -bit value, is a **parametric type**
 - n is the **parameter** (an Integer value)
 - Using $\text{Bit}\#(n)$ requires specifying a fixed n (e.g., $\text{Bit}\#(4)$ is a 4-bit value)
- Minispec provides other parametric types, and lets you define your own
 - Parametric types are *generic*
 - They take one or more parameters
 - Parameters must be known at compile-time
 - Specifying the parameters yields a *concrete* type
- Parameters can be Integers or types
 - Example: $\text{Vector}\#(n, T)$ is an n -element vector of T 's (e.g., $\text{Vector}\#(4, \text{Bit}\#(8))$ = 4-elem vector of 8-bit values)

Parametric Functions

- Functions have fixed argument and return types
 - Problem 1: Have to write a function for every bit width
 - Problem 2: If we build large functions from smaller ones, have to write many functions! (e.g., $\text{rca2} \rightarrow \text{rca4} \rightarrow \text{rca8} \dots$)

Parametric Functions

- Functions have fixed argument and return types
 - Problem 1: Have to write a function for every bit width
 - Problem 2: If we build large functions from smaller ones, have to write many functions! (e.g., $\text{rca2} \rightarrow \text{rca4} \rightarrow \text{rca8} \dots$)
- Parametric functions solve these problems: We can write one *generic* function that covers every case
 - Example: $\text{rca\#}(n)$, an n -bit ripple-carry adder

Parametric Functions

- Functions have fixed argument and return types
 - Problem 1: Have to write a function for every bit width
 - Problem 2: If we build large functions from smaller ones, have to write many functions! (e.g., $\text{rca2} \rightarrow \text{rca4} \rightarrow \text{rca8} \dots$)
- Parametric functions solve these problems: We can write one *generic* function that covers every case
 - Example: $\text{rca\#}(n)$, an n -bit ripple-carry adder
- A parametric function must be invoked with fixed parameters, which instantiates a *concrete* function
 - Example: Calling $\text{rca\#}(32)$ instantiates a 32-bit adder

Example: Parametric Parity

Example: Parametric Parity

```
function Bit#(1) parity#(Integer n)(Bit#(n) x);  
    return (n == 1)? x : x[n-1] ^ parity#(n-1)(x[n-2:0]);  
endfunction
```

Example: Parametric Parity

```
function Bit#(1) parity#(Integer n)(Bit#(n) x);  
    return (n == 1)? x : x[n-1] ^ parity#(n-1)(x[n-2:0]);  
endfunction
```

- The parameter `n` is used as a variable in the function

Example: Parametric Parity

```
function Bit#(1) parity#(Integer n)(Bit#(n) x);  
    return (n == 1)? x : x[n-1] ^ parity#(n-1)(x[n-2:0]);  
endfunction
```

- The parameter `n` is used as a variable in the function
- Large circuits implemented by composing smaller ones:
`parity#(n)` invokes `parity#(n-1)`!

Example: Parametric Parity

```
function Bit#(1) parity#(Integer n)(Bit#(n) x);  
    return (n == 1)? x : x[n-1] ^ parity#(n-1)(x[n-2:0]);  
endfunction
```

- The parameter `n` is used as a variable in the function
- Large circuits implemented by composing smaller ones: `parity#(n)` invokes `parity#(n-1)`!
- If another function calls `parity#(3)`, compiler produces:

Example: Parametric Parity

```
function Bit#(1) parity#(Integer n)(Bit#(n) x);  
    return (n == 1)? x : x[n-1] ^ parity#(n-1)(x[n-2:0]);  
endfunction
```

- The parameter `n` is used as a variable in the function
- Large circuits implemented by composing smaller ones: `parity#(n)` invokes `parity#(n-1)`!
- If another function calls `parity#(3)`, compiler produces:

```
function Bit#(1) parity#(3)(Bit#(3) x);  
    return x[2] ^ parity#(2)(x[1:0]);  
endfunction
```

Example: Parametric Parity

```
function Bit#(1) parity#(Integer n)(Bit#(n) x);  
    return (n == 1)? x : x[n-1] ^ parity#(n-1)(x[n-2:0]);  
endfunction
```

- The parameter `n` is used as a variable in the function
- Large circuits implemented by composing smaller ones: `parity#(n)` invokes `parity#(n-1)`!
- If another function calls `parity#(3)`, compiler produces:

```
function Bit#(1) parity#(3)(Bit#(3) x);  
    return x[2] ^ parity#(2)(x[1:0]);  
endfunction  
function Bit#(1) parity#(2)(Bit#(2) x);  
    return x[1] ^ parity#(1)(x[0:0]);  
endfunction
```

Example: Parametric Parity

```
function Bit#(1) parity#(Integer n)(Bit#(n) x);  
    return (n == 1)? x : x[n-1] ^ parity#(n-1)(x[n-2:0]);  
endfunction
```

- The parameter `n` is used as a variable in the function
- Large circuits implemented by composing smaller ones: `parity#(n)` invokes `parity#(n-1)`!
- If another function calls `parity#(3)`, compiler produces:


```
function Bit#(1) parity#(3)(Bit#(3) x);  
    return x[2] ^ parity#(2)(x[1:0]);  
endfunction  
function Bit#(1) parity#(2)(Bit#(2) x);  
    return x[1] ^ parity#(1)(x[0:0]);  
endfunction  
function Bit#(1) parity#(1)(Bit#(1) x);  
    return x;  
endfunction
```

Example: Parametric Parity

```
function Bit#(1) parity#(Integer n)(Bit#(n) x);  
    return (n == 1)? x : x[n-1] ^ parity#(n-1)(x[n-2:0]);  
endfunction
```

- The parameter **n** is used as a variable in the function
- Large circuits implemented by composing smaller ones: parity#(n) invokes parity#(n-1)!
- If another function calls parity#(3), compiler produces:
 
```
function Bit#(1) parity#(3)(Bit#(3) x);  
    return x[2] ^ parity#(2)(x[1:0]);  
endfunction  
function Bit#(1) parity#(2)(Bit#(2) x);  
    return x[1] ^ parity#(1)(x[0:0]);  
endfunction  
function Bit#(1) parity#(1)(Bit#(1) x);  
    return x;  
endfunction
```




Example: Parametric Parity

```
function Bit#(1) parity#(Integer n)(Bit#(n) x);  
    return (n == 1)? x : x[n-1] ^ parity#(n-1)(x[n-2:0]);  
endfunction
```

- The parameter **n** is used as a variable in the function
- Large circuits implemented by composing smaller ones: `parity#(n)` invokes `parity#(n-1)`!
- If another function calls `parity#(3)`, compiler produces:
 
```
function Bit#(1) parity#(3)(Bit#(3) x);  
    return x[2] ^ parity#(2)(x[1:0]);  
endfunction  
function Bit#(1) parity#(2)(Bit#(2) x);  
    return x[1] ^ parity#(1)(x[0:0]);  
endfunction  
function Bit#(1) parity#(1)(Bit#(1) x);  
    return x;  
endfunction
```




Example: Parametric Parity

```
function Bit#(1) parity#(Integer n)(Bit#(n) x);  
    return (n == 1)? x : x[n-1] ^ parity#(n-1)(x[n-2:0]);  
endfunction
```

- The parameter **n** is used as a variable in the function
- Large circuits implemented by composing smaller ones: parity#(n) invokes parity#(n-1)!
- If another function calls parity#(3), compiler produces:
 
```
function Bit#(1) parity#(3)(Bit#(3) x);  
    return x[2] ^ parity#(2)(x[1:0]);  
endfunction  
function Bit#(1) parity#(2)(Bit#(2) x);  
    return x[1] ^ parity#(1)(x[0:0]);  
endfunction  
function Bit#(1) parity#(1)(Bit#(1) x);  
    return x;  
endfunction
```



Integer is a Special Type

Always evaluated by the compiler

- Integer values are (positive or negative) numbers with an **unbounded number of bits**
 - Unbounded bits → Cannot be synthesized to hardware

Integer is a Special Type

Always evaluated by the compiler


- Integer values are (positive or negative) numbers with an **unbounded number of bits**
 - Unbounded bits → Cannot be synthesized to hardware
- Integers are guaranteed to be evaluated at compile time, i.e., turned into fixed numbers
 - If the compiler cannot evaluate an Integer expression, it throws an error

Integer is a Special Type


Always evaluated by the compiler

- Integer values are (positive or negative) numbers with an **unbounded number of bits**
 - Unbounded bits → Cannot be synthesized to hardware
- Integers are guaranteed to be evaluated at compile time, i.e., turned into fixed numbers
 - If the compiler cannot evaluate an Integer expression, it throws an error
- Integer supports the same operations as Bit#(n), (arithmetic, logical, comparisons, etc.)
 - But evaluated by compiler → operations on Integers never produce any hardware

N-bit Ripple-Carry Adder

 


N-bit Ripple-Carry Adder

 

```
function Bit#(n+1) rca#(Integer n)(Bit#(n) a, Bit#(n) b, Bit#(1) cin);
```

```
endfunction
```


N-bit Ripple-Carry Adder

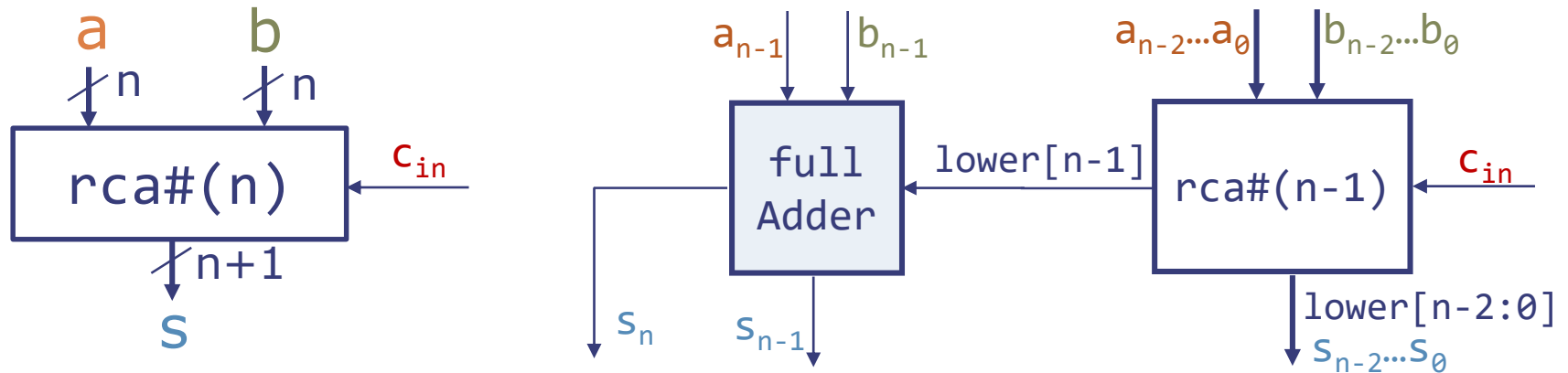

```
function Bit#(n+1) rca#(Integer n)(Bit#(n) a, Bit#(n) b, Bit#(1) cin);
    Bit#(n) lower = rca#(n-1)(a[n-2:0], b[n-2:0], cin);
```


```
endfunction
```

N-bit Ripple-Carry Adder

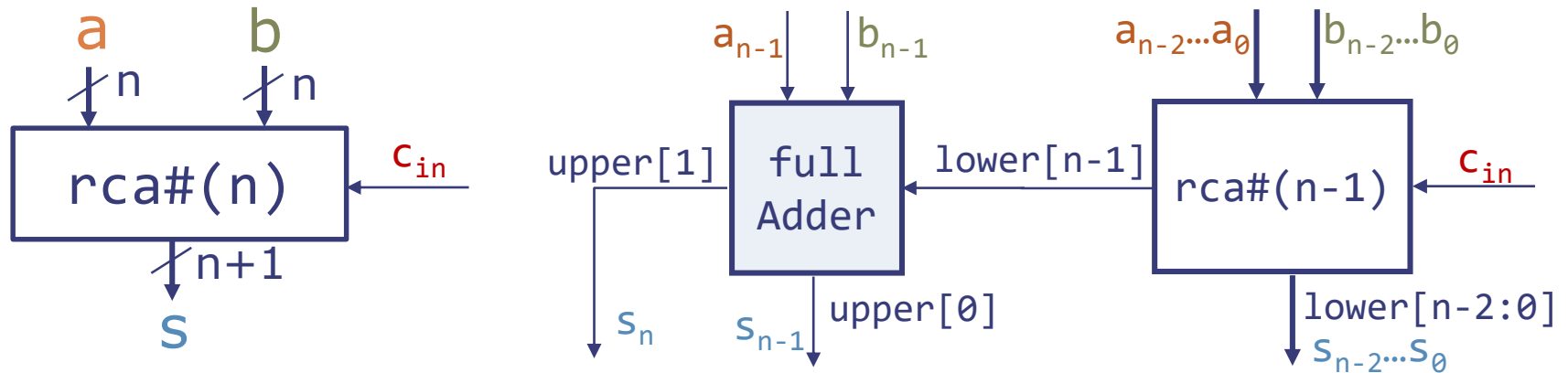


```
function Bit#(n+1) rca#(Integer n)(Bit#(n) a, Bit#(n) b, Bit#(1) cin);
    Bit#(n) lower = rca#(n-1)(a[n-2:0], b[n-2:0], cin);
    Bit#(2) upper = fullAdder(a[n-1], b[n-1], lower[n-1]);
endfunction
```

N-bit Ripple-Carry Adder

 

```
function Bit#(n+1) rca#(Integer n)(Bit#(n) a, Bit#(n) b, Bit#(1) cin);
    Bit#(n) lower = rca#(n-1)(a[n-2:0], b[n-2:0], cin);
    Bit#(2) upper = fullAdder(a[n-1], b[n-1], lower[n-1]);
    return {upper, lower[n-2:0]};
endfunction
```

N-bit Ripple-Carry Adder

 

```
function Bit#(n+1) rca#(Integer n)(Bit#(n) a, Bit#(n) b, Bit#(1) cin);
    Bit#(n) lower = rca#(n-1)(a[n-2:0], b[n-2:0], cin);
    Bit#(2) upper = fullAdder(a[n-1], b[n-1], lower[n-1]);
    return {upper, lower[n-2:0]};
endfunction
```

// Base case

```
function Bit#(2) rca#(1)(Bit#(1) a, Bit#(1) b, Bit#(1) cin);
    return fullAdder(a, b, cin);
endfunction
```

Type Inference

- You can omit the type of a variable by declaring it with the `let` keyword
- The compiler infers the variable's type from the type of the expression assigned to the variable

```
Bit#(4) x = 4'b0011;  
let y = x;           // y has type Bit#(4)  
let z = {x, x};       // z has type Bit#(8)  
let w = 2'b11;        // w has type Bit#(2)  
let n = 42;           // n has type Integer
```


User-Defined Types

- **Type synonyms** allow giving a different name to a type

```
typedef Bit#(8) Byte;
```

User-Defined Types

- **Type synonyms** allow giving a different name to a type
- **Structs** represent a group of member values with different types

```
typedef Bit#(8) Byte;
```

```
typedef struct {  
    Byte red;  
    Byte green;  
    Byte blue;  
} Pixel;
```

```
Pixel p;  
p.red = 255;
```

User-Defined Types

- **Type synonyms** allow giving a different name to a type
- **Structs** represent a group of member values with different types
- **Enums** represent a set of symbolic constants

```
typedef Bit#(8) Byte;
```

```
typedef struct {  
    Byte red;  
    Byte green;  
    Byte blue;  
} Pixel;
```

```
Pixel p;  
p.red = 255;
```

```
typedef enum {  
    Ready, Busy, Error  
} State;
```

```
State state = Ready;
```

User-Defined Types

- **Type synonyms** allow giving a different name to a type
- **Structs** represent a group of member values with different types
- **Enums** represent a set of symbolic constants
- Structs and enums are much clearer than using raw bits!
 - e.g., `Bit#(24) pixel; pixel[15:8]` versus `Pixel pixel; pixel.green`

```
typedef Bit#(8) Byte;
```

```
typedef struct {  
    Byte red;  
    Byte green;  
    Byte blue;  
} Pixel;
```

```
Pixel p;  
p.red = 255;
```

```
typedef enum {  
    Ready, Busy, Error  
} State;
```

```
State state = Ready;
```

For Loops



- For loop statements allow compactly expressing a sequence of similar statements

```
Bit#(6) w = 0;  
for (Integer i = 0; i < 6; i = i + 1)  
    w[i] = z[i / 2];
```

For Loops



- For loop statements allow compactly expressing a sequence of similar statements

```
Bit#(6) w = 0;  
for (Integer i = 0; i < 6; i = i + 1)  
    w[i] = z[i / 2];
```

- For loops are not like loops in software programming languages!
 - **Fixed number of iterations**
(Integer induction variable!)
 - **Unrolled** at compile time

For Loops



- For loop statements allow compactly expressing a sequence of similar statements

```
Bit#(6) w = 0;  
for (Integer i = 0; i < 6; i = i + 1)  
    w[i] = z[i / 2];
```


- For loops are not like loops in software programming languages!

- Fixed number of iterations**
(Integer induction variable!)
- Unrolled** at compile time

- Example: The loop above is translated into this sequence:

```
w[0] = z[0];  
w[1] = z[0];  
w[2] = z[1];  
w[3] = z[1];  
w[4] = z[2];  
w[5] = z[2];
```

N-bit Ripple-Carry Adder with Loop

 

```
function Bit#(n+1) rca#(Integer n)(Bit#(n) a, Bit#(n) b, Bit#(1) cin);
    Bit#(n) s = 0;
    Bit#(n+1) c = {0, cin};
    for (Integer i = 0; i < n; i = i + 1) begin
        let x = fullAdder(a[i], b[i], c[i]);
        s[i] = x[0];
        c[i+1] = x[1];
    end
    return {c[n], s};
endfunction
```


Conditional Statements



- If statements have a syntax similar to software:

```
function Bit#(4) max(Bit#(4) a,  
                    Bit#(4) b);  
    Bit#(4) result = b;  
    if (a > b) result = a;  
    return result;  
endfunction
```

Conditional Statements



- If statements have a syntax similar to software:

```
function Bit#(4) max(Bit#(4) a,  
                    Bit#(4) b);  
    Bit#(4) result = b;  
    if (a > b) result = a;  
    return result;  
endfunction
```

```
function Bit#(4) max(Bit#(4) a,  
                    Bit#(4) b);  
    Bit#(4) result;  
    if (a > b) result = a;  
    else result = b;  
    return result;  
endfunction
```

Conditional Statements



- If statements have a syntax similar to software:

```
function Bit#(4) max(Bit#(4) a,      function Bit#(4) max(Bit#(4) a,
                                Bit#(4) b);                                Bit#(4) b);
    Bit#(4) result = b;
    if (a > b) result = a;
    return result;
endfunction

    Bit#(4) result;
    if (a > b) result = a;
    else result = b;
    return result;
endfunction
```

- But they are **implemented very differently** from software programming languages!
 - Translated to muxes, like conditional expressions
 - Each variable assigned within an if statement uses a mux to select the right value (the one assigned in the if branch, else branch, or the previous value)

Conditional Statements



- If statements have a syntax similar to software:

```
function Bit#(4) max(Bit#(4) a,      function Bit#(4) max(Bit#(4) a,
                                Bit#(4) b);                                Bit#(4) b);
    Bit#(4) result = b;
    if (a > b) result = a;
    return result;
endfunction
                                Bit#(4) result;
                                if (a > b) result = a;
                                else result = b;
                                return result;
                                endfunction
```

- But they are **implemented very differently** from software programming languages!
 - Translated to muxes, like conditional expressions
 - Each variable assigned within an if statement uses a mux to select the right value (the one assigned in the if branch, else branch, or the previous value)
- Minispec also has case statements (see tutorial)

Minispec Takeaways

- Minispec lets you build circuits with constructs similar to those of software programming languages

Minispec Takeaways

- Minispec lets you build circuits with constructs similar to those of software programming languages
- But keep in mind that the implementation of these features is often very different from software!
 - Parametric functions and types are **instantiated**
 - Functions are **inlined**
 - Conditionals (`?:`, if-else, case) are translated to **multiplexers**, and all their branches are evaluated
 - Loops are **unrolled**
 - What remains is an acyclic graph of gates

Minispec Takeaways

- Minispec lets you build circuits with constructs similar to those of software programming languages
- But keep in mind that the implementation of these features is often very different from software!
 - Parametric functions and types are **instantiated**
 - Functions are **inlined**
 - Conditionals (`?:`, if-else, case) are translated to **multiplexers**, and all their branches are evaluated
 - Loops are **unrolled**
 - What remains is an acyclic graph of gates

Never forget that you're designing hardware


Design Tradeoffs in Combinational Circuits

Algorithmic Tradeoffs in Hardware Design

- Each function often allows many implementations with widely different delay, area, and power


Algorithmic Tradeoffs in Hardware Design

 - Each function often allows many implementations with widely different delay, area, and power




Algorithmic Tradeoffs in Hardware Design

 - Each function often allows many implementations with widely different delay, area, and power
- Choosing the right **algorithms** is key to optimizing your design
 - Tools cannot compensate for an inefficient algorithm (in most cases)




Algorithmic Tradeoffs in Hardware Design

 - Each function often allows many implementations with widely different delay, area, and power
- Choosing the right **algorithms** is key to optimizing your design
 - Tools cannot compensate for an inefficient algorithm (in most cases)
 - Just like programming software




Algorithmic Tradeoffs in Hardware Design

 
- Each function often allows many implementations with widely different delay, area, and power
- Choosing the right **algorithms** is key to optimizing your design
 - Tools cannot compensate for an inefficient algorithm (in most cases)
 - Just like programming software
- Case study: Building a better adder



Ripple-Carry Adder: Simple but Slow

 


Ripple-Carry Adder: Simple but Slow

 


- Worst-case path: Carry propagation from LSB to MSB, e.g., when adding $11\dots111$ to $00\dots001$

Ripple-Carry Adder: Simple but Slow

 

- Worst-case path: Carry propagation from LSB to MSB, e.g., when adding $11\dots111$ to $00\dots001$


Ripple-Carry Adder: Simple but Slow

 

- Worst-case path: Carry propagation from LSB to MSB, e.g., when adding 11...111 to 00...001

$$t_{PD} = n * t_{PD,FA}$$


Ripple-Carry Adder: Simple but Slow

 

- Worst-case path: Carry propagation from LSB to MSB, e.g., when adding 11...111 to 00...001

$$t_{PD} = n * t_{PD,FA} \approx \Theta(n)$$

Ripple-Carry Adder: Simple but Slow

 

- Worst-case path: Carry propagation from LSB to MSB, e.g., when adding 11...111 to 00...001

$$t_{PD} = n * t_{PD,FA} \approx \Theta(n)$$

- $\Theta(n)$ is read "order n" and tells us that the latency of our adder grows **linearly** with the number of bits of the operands

Asymptotic Analysis

- Formally, $g(n) = \Theta(f(n))$ iff there exist $C_2 \geq C_1 > 0$ such that for all but *finitely many* integers $n \geq 0$,

$$C_2 \cdot f(n) \geq g(n) \geq C_1 \cdot f(n)$$

Asymptotic Analysis

- Formally, $g(n) = \Theta(f(n))$ iff there exist $C_2 \geq C_1 > 0$ such that for all but *finitely many* integers $n \geq 0$,

$$\underbrace{C_2 \cdot f(n) \geq g(n) \geq C_1 \cdot f(n)}$$

$g(n) = O(f(n))$

$\Theta(\dots)$ implies both inequalities;
 $O(\dots)$ implies only the first.

Asymptotic Analysis

- Formally, $g(n) = \Theta(f(n))$ iff there exist $C_2 \geq C_1 > 0$ such that for all but *finitely many* integers $n \geq 0$,

$$\underbrace{C_2 \cdot f(n) \geq g(n) \geq C_1 \cdot f(n)}$$

$g(n) = O(f(n))$

$\Theta(\dots)$ implies both inequalities;
 $O(\dots)$ implies only the first.

- Example: $n^2 + 2n + 3 = \Theta(n^2)$ (read “is of order n^2 ”)

Asymptotic Analysis

- Formally, $g(n) = \Theta(f(n))$ iff there exist $C_2 \geq C_1 > 0$ such that for all but *finitely many* integers $n \geq 0$,


$$\underbrace{C_2 \cdot f(n) \geq g(n) \geq C_1 \cdot f(n)}$$

$g(n) = O(f(n))$

$\Theta(\dots)$ implies both inequalities;
 $O(\dots)$ implies only the first.


- Example: $n^2 + 2n + 3 = \Theta(n^2)$ (read “is of order n^2 ”) since $2n^2 > n^2 + 2n + 3 > n^2$ except for a few small integers

Carry-Select Adder Trades Area for Speed

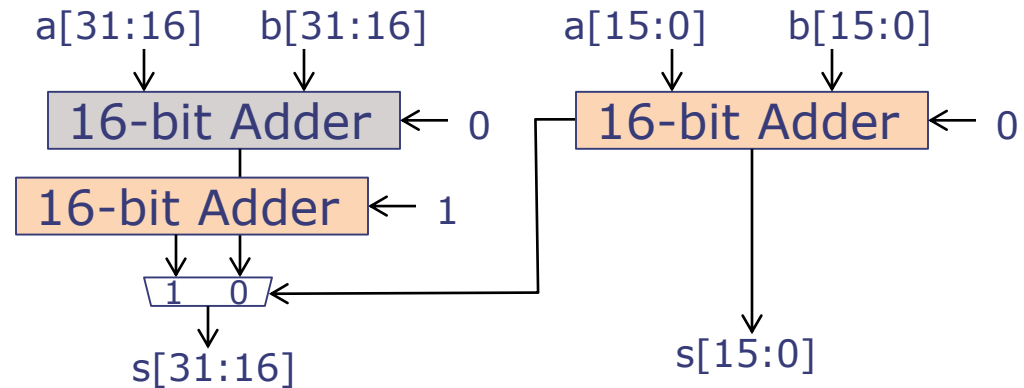


Carry-Select Adder Trades Area for Speed

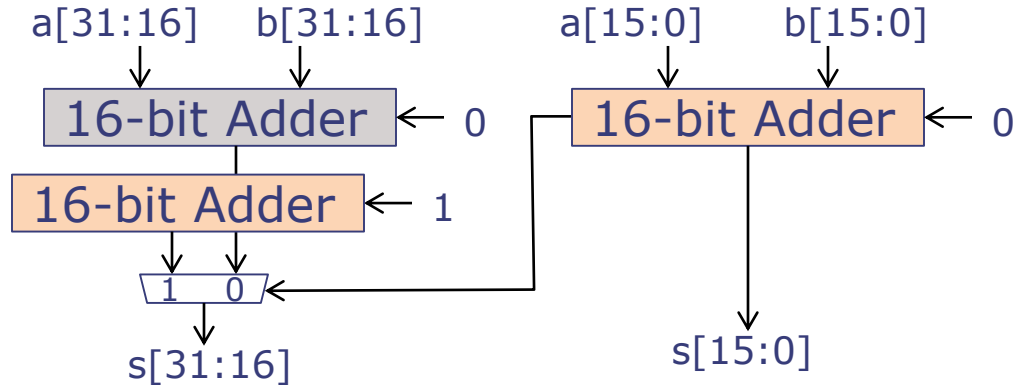Two copies of the high half of the adder: one assumes carry-in of "0", the other carry-in of "1"



Carry-Select Adder Trades Area for Speed

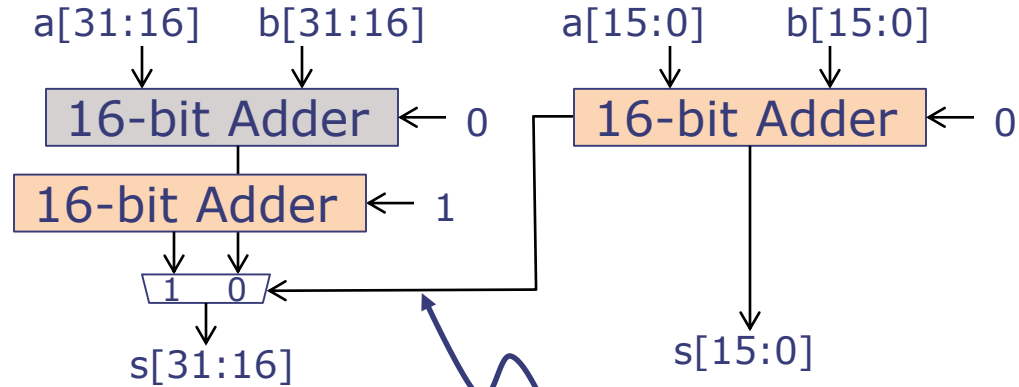
Two copies of the high half of the adder: one assumes carry-in of "0", the other carry-in of "1"



The carry-out of the low half selects the correct version of the high-half addition.

Carry-Select Adder Trades Area for Speed

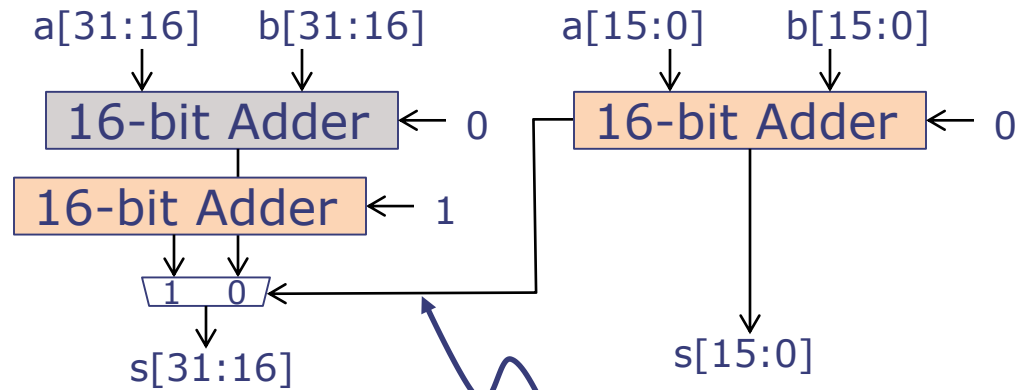
Two copies of the high half of the adder: one assumes carry-in of "0", the other carry-in of "1"



The carry-out of the low half selects the correct version of the high-half addition.


- Propagation delay: $t_{PD,32} = t_{PD,16} + t_{PD,MUX}$

Carry-Select Adder Trades Area for Speed

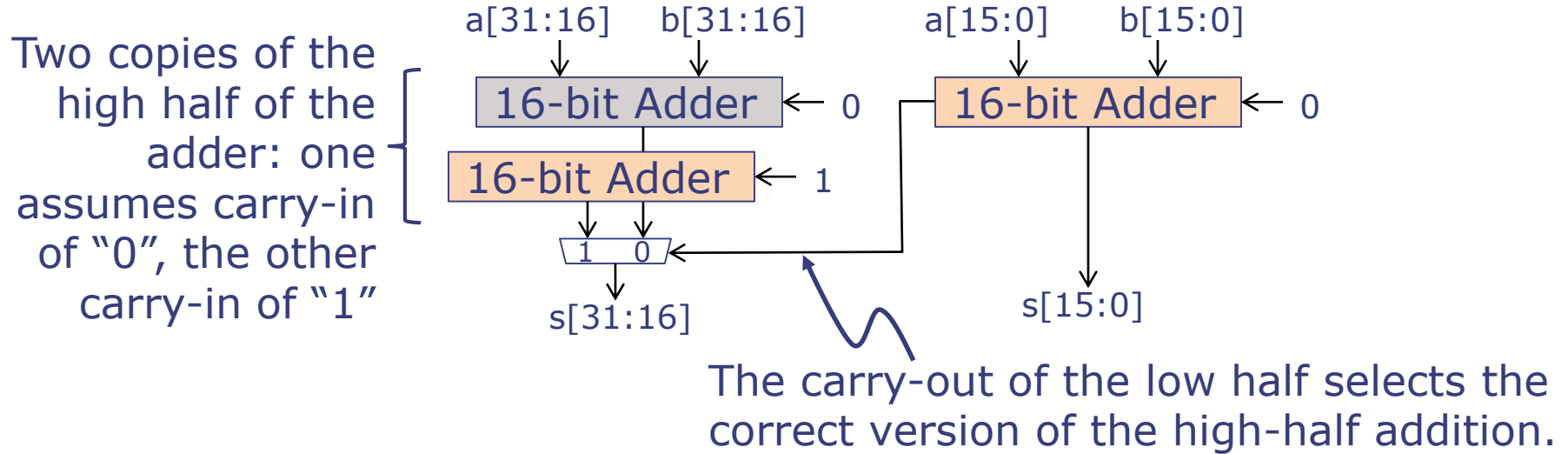


- Propagation delay: $t_{PD,32} = t_{PD,16} + t_{PD,MUX}$
 - If we used 16-bit ripple-carry adders, this would roughly halve delay over a 32-bit ripple-carry adder

Carry-Select Adder Trades Area for Speed

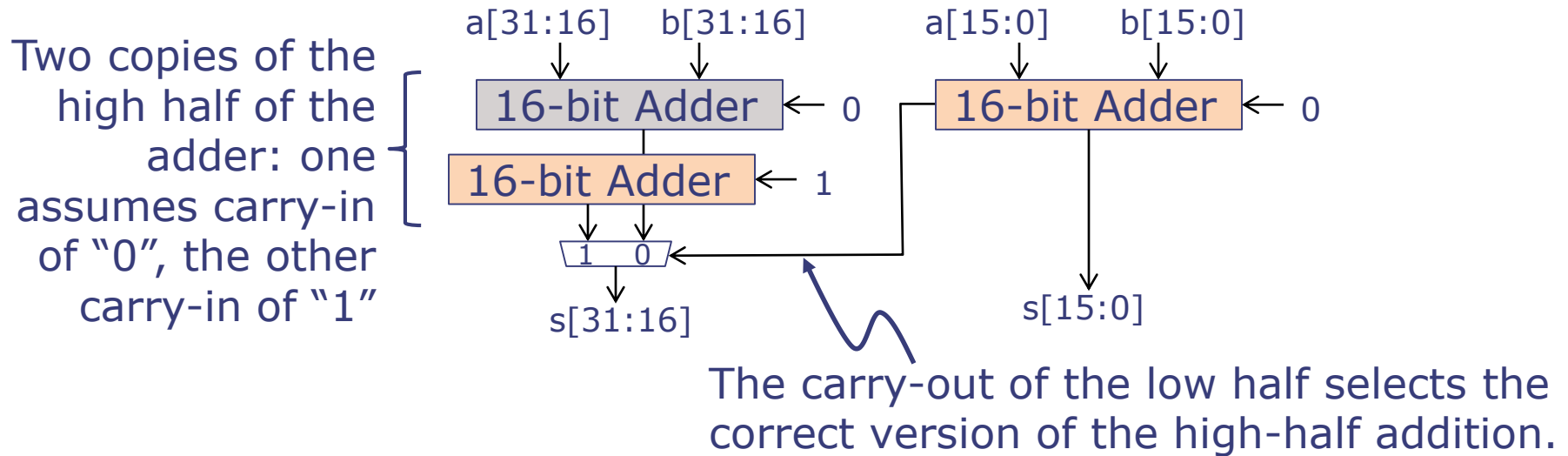

- Propagation delay: $t_{PD,32} = t_{PD,16} + t_{PD,MUX}$
 - If we used 16-bit ripple-carry adders, this would roughly halve delay over a 32-bit ripple-carry adder
 - If we apply the same strategy recursively (build each 16-bit adder from 8-bit carry-select adders, etc.), $t_{PD,n} = \Theta(\log n)$


Carry-Select Adder Trades Area for Speed

 

- Propagation delay: $t_{PD,32} = t_{PD,16} + t_{PD,MUX}$
 - If we used 16-bit ripple-carry adders, this would roughly halve delay over a 32-bit ripple-carry adder
 - If we apply the same strategy recursively (build each 16-bit adder from 8-bit carry-select adders, etc.), $t_{PD,n} = \Theta(\log n)$

Drawbacks?


Carry-Select Adder Trades Area for Speed

 

- Propagation delay: $t_{PD,32} = t_{PD,16} + t_{PD,MUX}$
 - If we used 16-bit ripple-carry adders, this would roughly halve delay over a 32-bit ripple-carry adder
 - If we apply the same strategy recursively (build each 16-bit adder from 8-bit carry-select adders, etc.), $t_{PD,n} = \Theta(\log n)$

Drawbacks? Consumes much more area than ripple-carry adder

Carry-Select Adder Trades Area for Speed

 

- Propagation delay: $t_{PD,32} = t_{PD,16} + t_{PD,MUX}$
 - If we used 16-bit ripple-carry adders, this would roughly halve delay over a 32-bit ripple-carry adder
 - If we apply the same strategy recursively (build each 16-bit adder from 8-bit carry-select adders, etc.), $t_{PD,n} = \Theta(\log n)$


*Drawbacks? Consumes much more area than ripple-carry adder
Wide mux adds significant delay (lab 4)*

Carry-Lookahead Adders (CLAs)

- CLAs compute all carry bits in $\Theta(\log n)$ delay


Carry-Lookahead Adders (CLAs)

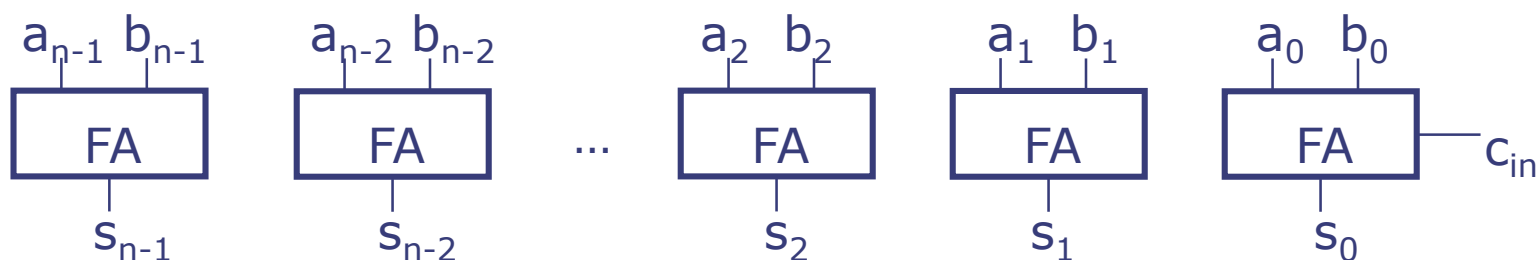- CLAs compute all carry bits in $\Theta(\log n)$ delay




Carry-Lookahead Adders (CLAs)

 - CLAs compute all carry bits in $\Theta(\log n)$ delay



Carry-Lookahead Adders (CLAs)

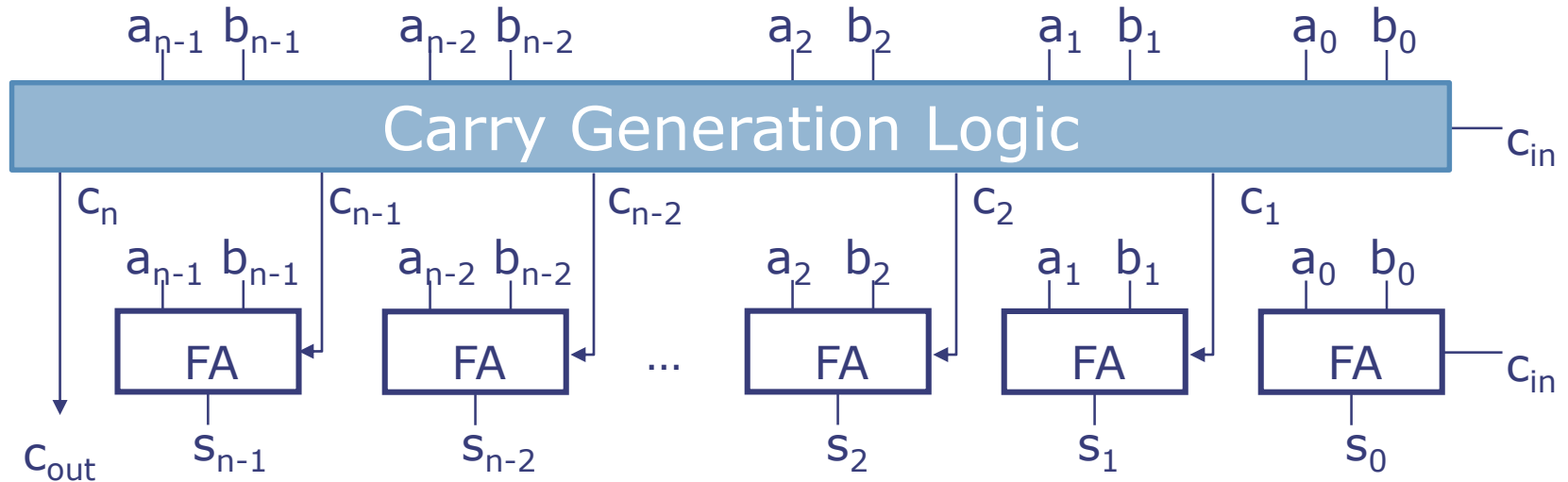
- CLAs compute all carry bits in $\Theta(\log n)$ delay



- Key idea: Transform chain of carry computations into a tree

Carry-Lookahead Adders (CLAs)

 - CLAs compute all carry bits in $\Theta(\log n)$ delay



- Key idea: Transform chain of carry computations into a tree
 - Transforming a chain of associative operations (e.g., AND, OR, XOR) into a tree is easy
 - But how to do this with carries?

Carry-Lookahead Adder Details

NOTE: Remaining slides are optional material that will not be on a quiz but will be helpful for Lab 4 and the Design Project

Building a Carry-Lookahead Adder

- Step 1: Generate the output carry in $\Theta(\log n)$ delay
- Step 2: Extend step 1 to generate all carries in $\Theta(\log n)$ delay

Building a Carry-Lookahead Adder

- Step 1: Generate the output carry in $\Theta(\log n)$ delay
- Step 2: Extend step 1 to generate all carries in $\Theta(\log n)$ delay
- We will use two main ideas that are broadly useful beyond CLAs!
 - Step 1 leverages that **function composition is associative**

Building a Carry-Lookahead Adder

- Step 1: Generate the output carry in $\Theta(\log n)$ delay
- Step 2: Extend step 1 to generate all carries in $\Theta(\log n)$ delay
- We will use two main ideas that are broadly useful beyond CLAs!
 - Step 1 leverages that **function composition is associative**
 - Step 2 uses the **parallel scan** (a.k.a. parallel prefix) algorithm

Function composition is associative

Basic math reminder ☺

Function compo

Function composition is associative

Basic math reminder ☺


$$\begin{array}{c} f_1 \circ f_2 \circ f_3 = (f_1 \circ f_2) \circ f_3 = f_1 \circ (f_2 \circ f_3) \\ \text{Fu} \\) \\ 3 \ 3 \ 3 \ 2 \ 2 \ 2 \ 1 \ 1 \ 3 \ 3 \ 3 \ 2 \ 2 \ 1 \ 1 \ 1 \ 3 \ 3 \ 2 \ 2 \ 2 \ 1 \ 1 \ 1 \end{array}$$

- Function composition is always associative:

$$f_1 \circ f_2 \circ f_3 = (f_1 \circ f_2) \circ f_3 = f_1 \circ (f_2 \circ f_3)$$


Deriving carry-out in $\Theta(\log n)$ delay

- Consider a ripple-carry adder:

 

Deriving carry-out in $\Theta(\log n)$ delay

- Consider a ripple-carry adder:

 


- Suppose all inputs (a , b , c_0) become valid and stable at $t=0$. If we focus on computing the output carry only, this circuit is equivalent to



Deriving carry-out in $\Theta(\log n)$ delay

- Consider a ripple-carry adder:

 


- Suppose all inputs (a , b , c_0) become valid and stable at $t=0$. If we focus on computing the output carry only, this circuit is equivalent to



- A chain of functions f_i , each with 1-bit input and output

Deriving carry-out in $\Theta(\log n)$ delay

- Consider a ripple-carry adder:

 

- Suppose all inputs (a , b , c_0) become valid and stable at $t=0$. If we focus on computing the output carry only, this circuit is equivalent to



- A chain of functions f_i , each with 1-bit input and output
- Each f_i is determined by the values of a_i and b_i


Turning function chains into trees

- Because function composition is associative, we can turn a chain of functions into a tree by first composing the functions...




Turning function chains into trees

 - Because function composition is associative, we can turn a chain of functions into a tree by first composing the functions...




Turning function chains into trees

 - Because function composition is associative, we can turn a chain of functions into a tree by first composing the functions...



Turning function chains into trees

 
- Because function composition is associative, we can turn a chain of functions into a tree by first composing the functions...



...and then evaluating the final function: $c_4 = f_{30}(c_0)$

Turning function chains into trees

 - Because function composition is associative, we can turn a chain of functions into a tree by first composing the functions...




...and then evaluating the final function: $c_4 = f_{30}(c_0)$

How does delay grow with chain length n ?

Turning function chains into trees

 - Because function composition is associative, we can turn a chain of functions into a tree by first composing the functions...




...and then evaluating the final function: $c_4 = f_{30}(c_0)$

How does delay grow with chain length n ? $\Theta(\log n)$

Turning function chains into trees

 - Because function composition is associative, we can turn a chain of functions into a tree by first composing the functions...



...and then evaluating the final function: $c_4 = f_{30}(c_0)$

How does delay grow with chain length n ? $\Theta(\log n)$

- Very general trick: Can turn any chain of functions into a tree, *if you can compose them efficiently*

1-bit input, 1-bit output functions

in	out
0	0
1	0

in	out
0	0
1	1

in	out
0	1
1	1

in	out
0	1
1	0

1-bit input, 1-bit output functions

kill

in	out
0	0
1	0

in	out
0	0
1	1

in	out
0	1
1	1

in	out
0	1
1	0

1-bit input, 1-bit output functions

kill

in	out
0	0
1	0

in	out
0	0
1	1

generate

in	out
0	1
1	1

in	out
0	1
1	0

1-bit input, 1-bit output functions

kill

in	out
0	0
1	0

propagate

in	out
0	0
1	1

generate

in	out
0	1
1	1

in	out
0	1
1	0

1-bit input, 1-bit output functions

kill

in	out
0	0
1	0

propagate

in	out
0	0
1	1

generate

in	out
0	1
1	1

invert

in	out
0	1
1	0

1-bit input, 1-bit output functions

kill	
in	out
0	0
1	0

propagate	
in	out
0	0
1	1

generate	
in	out
0	1
1	1

invert	
in	out
0	1
1	0

- *How many bits do we need to enumerate these functions?*

1-bit input, 1-bit output functions

kill	
in	out
0	0
1	0

propagate	
in	out
0	0
1	1

generate	
in	out
0	1
1	1

invert	
in	out
0	1
1	0

- How many bits do we need to enumerate these functions? **2 bits (only 4 choices!)**

Composing 1-bit functions

f	g	$f \circ g$
kill	kill	
kill	generate	
kill	propagate	
kill	invert	
generate	kill	
generate	generate	
generate	propagate	
generate	invert	
propagate	kill	
propagate	generate	
propagate	propagate	
propagate	invert	
invert	kill	
invert	generate	
invert	propagate	
invert	invert	

Composing 1-bit functions

f	g	$f \circ g$
kill	kill	kill
kill	generate	
kill	propagate	
kill	invert	
generate	kill	
generate	generate	
generate	propagate	
generate	invert	
propagate	kill	
propagate	generate	
propagate	propagate	
propagate	invert	
invert	kill	
invert	generate	
invert	propagate	
invert	invert	

Composing 1-bit functions

f	g	$f \circ g$
kill	kill	kill
kill	generate	generate
kill	propagate	
kill	invert	
generate	kill	
generate	generate	
generate	propagate	
generate	invert	
propagate	kill	
propagate	generate	
propagate	propagate	
propagate	invert	
invert	kill	
invert	generate	
invert	propagate	
invert	invert	

Composing 1-bit functions

f	g	$f \circ g$
kill	kill	kill
kill	generate	generate
kill	propagate	
kill	invert	
generate	kill	
generate	generate	
generate	propagate	
generate	invert	
propagate	kill	
propagate	generate	
propagate	propagate	
propagate	invert	
invert	kill	
invert	generate	
invert	propagate	invert
invert	invert	

Composing 1-bit functions

f	g	$f \circ g$
kill	kill	kill
kill	generate	generate
kill	propagate	
kill	invert	
generate	kill	
generate	generate	
generate	propagate	
generate	invert	
propagate	kill	
propagate	generate	
propagate	propagate	
propagate	invert	
invert	kill	
invert	generate	invert
invert	propagate	propagate
invert	invert	

Composing 1-bit functions

f	g	$f \circ g$
kill	kill	kill
kill	generate	generate
kill	propagate	kill
kill	invert	generate
generate	kill	kill
generate	generate	generate
generate	propagate	generate
generate	invert	kill
propagate	kill	kill
propagate	generate	generate
propagate	propagate	propagate
propagate	invert	invert
invert	kill	kill
invert	generate	generate
invert	propagate	invert
invert	invert	propagate

Composing 1-bit functions


f	g	$f \circ g$
kill	kill	kill
kill	generate	generate
kill	propagate	kill
kill	invert	generate
generate	kill	kill
generate	generate	generate
generate	propagate	generate
generate	invert	kill
propagate	kill	kill
propagate	generate	generate
propagate	propagate	propagate
propagate	invert	invert
invert	kill	kill
invert	generate	generate
invert	propagate	invert
invert	invert	propagate

This is just a
combinational
function with
two 2-bit inputs
and one 2-bit
output!

Composing 1-bit functions


f	g	$f \circ g$
kill	kill	kill
kill	generate	generate
kill	propagate	kill
kill	invert	generate
generate	kill	kill
generate	generate	generate
generate	propagate	generate
generate	invert	kill
propagate	kill	kill
propagate	generate	generate
propagate	propagate	propagate
propagate	invert	invert
invert	kill	kill
invert	generate	generate
invert	propagate	invert
invert	invert	propagate

 This is just a combinational function with two 2-bit inputs and one 2-bit output!




Deriving the initial functions

 - Remember, to derive the carry-out, a ripple-carry adder can be seen as a chain of functions f_i , each determined by the values of a_i and b_i



Deriving the initial functions

 
- Remember, to derive the carry-out, a ripple-carry adder can be seen as a chain of functions f_i , each determined by the values of a_i and b_i



- We can derive these functions from the full adder:

Deriving the initial functions

 - Remember, to derive the carry-out, a ripple-carry adder can be seen as a chain of functions f_i , each determined by the values of a_i and b_i




- We can derive these functions from the full adder:

a	b	c_{in}	c_{out}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Deriving the initial functions

 - Remember, to derive the carry-out, a ripple-carry adder can be seen as a chain of functions f_i , each determined by the values of a_i and b_i




- We can derive these functions from the full adder:

a	b	c_{in}	c_{out}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Deriving the initial functions

 - Remember, to derive the carry-out, a ripple-carry adder can be seen as a chain of functions f_i , each determined by the values of a_i and b_i




- We can derive these functions from the full adder:

a	b	c_{in}	c_{out}	
0	0	0	0	kill
0	0	1	0	
0	1	0	0	
0	1	1	1	
1	0	0	0	
1	0	1	1	
1	1	0	1	
1	1	1	1	

Deriving the initial functions

 - Remember, to derive the carry-out, a ripple-carry adder can be seen as a chain of functions f_i , each determined by the values of a_i and b_i




- We can derive these functions from the full adder:

a	b	c_{in}	c_{out}	
0	0	0	0	kill
0	0	1	0	
0	1	0	0	
0	1	1	1	
1	0	0	0	
1	0	1	1	
1	1	0	1	
1	1	1	1	

Deriving the initial functions

 - Remember, to derive the carry-out, a ripple-carry adder can be seen as a chain of functions f_i , each determined by the values of a_i and b_i




- We can derive these functions from the full adder:

a	b	c_{in}	c_{out}	
0	0	0	0	kill
0	0	1	0	
0	1	0	0	propagate
0	1	1	1	
1	0	0	0	
1	0	1	1	
1	1	0	1	
1	1	1	1	

Deriving the initial functions

 - Remember, to derive the carry-out, a ripple-carry adder can be seen as a chain of functions f_i , each determined by the values of a_i and b_i




- We can derive these functions from the full adder:

a	b	c_{in}	c_{out}	
0	0	0	0	kill propagate
0	0	1	0	
0	1	0	0	
0	1	1	1	
1	0	0	0	kill propagate
1	0	1	1	
1	1	0	1	
1	1	1	1	

Deriving the initial functions

 - Remember, to derive the carry-out, a ripple-carry adder can be seen as a chain of functions f_i , each determined by the values of a_i and b_i




- We can derive these functions from the full adder:

a	b	c_{in}	c_{out}	
0	0	0	0	kill
0	0	1	0	
0	1	0	0	propagate
0	1	1	1	
1	0	0	0	propagate
1	0	1	1	
1	1	0	1	
1	1	1	1	

Deriving the initial functions

 - Remember, to derive the carry-out, a ripple-carry adder can be seen as a chain of functions f_i , each determined by the values of a_i and b_i




- We can derive these functions from the full adder:

a	b	c_{in}	c_{out}	
0	0	0	0	kill
0	0	1	0	
0	1	0	0	propagate
0	1	1	1	
1	0	0	0	propagate
1	0	1	1	
1	1	0	1	
1	1	1	1	

Deriving the initial functions

 - Remember, to derive the carry-out, a ripple-carry adder can be seen as a chain of functions f_i , each determined by the values of a_i and b_i




- We can derive these functions from the full adder:

a	b	c_{in}	c_{out}	
0	0	0	0	kill
0	0	1	0	
0	1	0	0	propagate
0	1	1	1	
1	0	0	0	propagate
1	0	1	1	
1	1	0	1	generate
1	1	1	1	

Deriving the initial functions

 - Remember, to derive the carry-out, a ripple-carry adder can be seen as a chain of functions f_i , each determined by the values of a_i and b_i




- We can derive these functions from the full adder:

a	b	c_{in}	c_{out}	
0	0	0	0	kill
0	0	1	0	
0	1	0	0	propagate
0	1	1	1	
1	0	0	0	propagate
1	0	1	1	
1	1	0	1	generate
1	1	1	1	

This is a function with two 1-bit inputs and one 2-bit output

Deriving the initial functions

 
- Remember, to derive the carry-out, a ripple-carry adder can be seen as a chain of functions f_i , each determined by the values of a_i and b_i



- We can derive these functions from the full adder:

a	b	C_{in}	C_{out}	
0	0	0	0	kill
0	0	1	0	
0	1	0	0	propagate
0	1	1	1	
1	0	0	0	propagate
1	0	1	1	
1	1	0	1	generate
1	1	1	1	

 This is a function with two 1-bit inputs and one 2-bit output



Evaluating functions

- Given a function f (as a 2-bit input value), we need another function that applies f to an input carry to produce the output carry

Evaluating functions

- Given a function f (as a 2-bit input value), we need another function that applies f to an input carry to produce the output carry
- This is also a simple combinational circuit

Evaluating functions

- Given a function f (as a 2-bit input value), we need another function that applies f to an input carry to produce the output carry
- This is also a simple combinational circuit

f	c_{in}	c_{out}
kill	0	0
kill	1	0
generate	0	1
generate	1	1
propagate	0	0
propagate	1	1
invert	0	1
invert	1	0

Evaluating functions

- Given a function f (as a 2-bit input value), we need another function that applies f to an input carry to produce the output carry
- This is also a simple combinational circuit


f	c_{in}	c_{out}
kill	0	0
kill	1	0
generate	0	1
generate	1	1
propagate	0	0
propagate	1	1
invert	0	1
invert	1	0

invert not used in CLAs

Evaluating functions

- Given a function f (as a 2-bit input value), we need another function that applies f to an input carry to produce the output carry
- This is also a simple combinational circuit


f	C_{in}	C_{out}
kill	0	0
kill	1	0
generate	0	1
generate	1	1
propagate	0	0
propagate	1	1
invert	0	1
invert	1	0

 

invert not used in CLAs


Step 1: Generating the output carry

Putting it all together

 


Step 1: Generating the output carry

Putting it all together

 


Step 1: Generating the output carry

Putting it all together

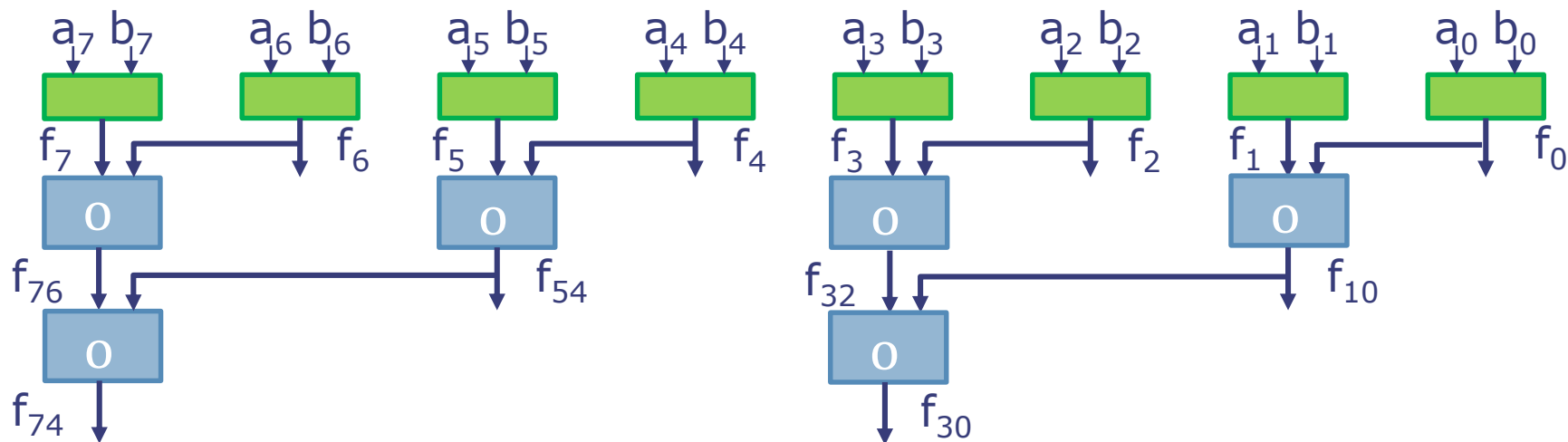


Step 1: Generating the output carry

Putting it all together

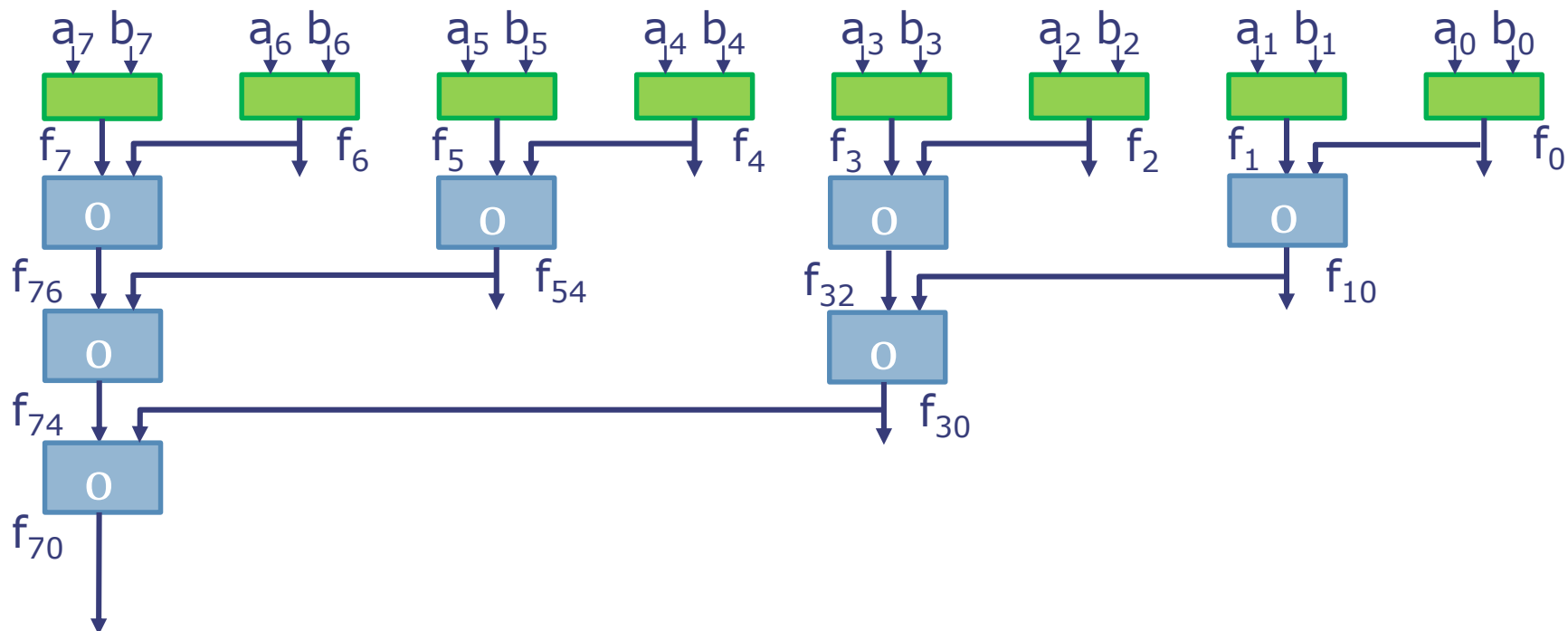


Step 1: Generating the output carry

Putting it all together

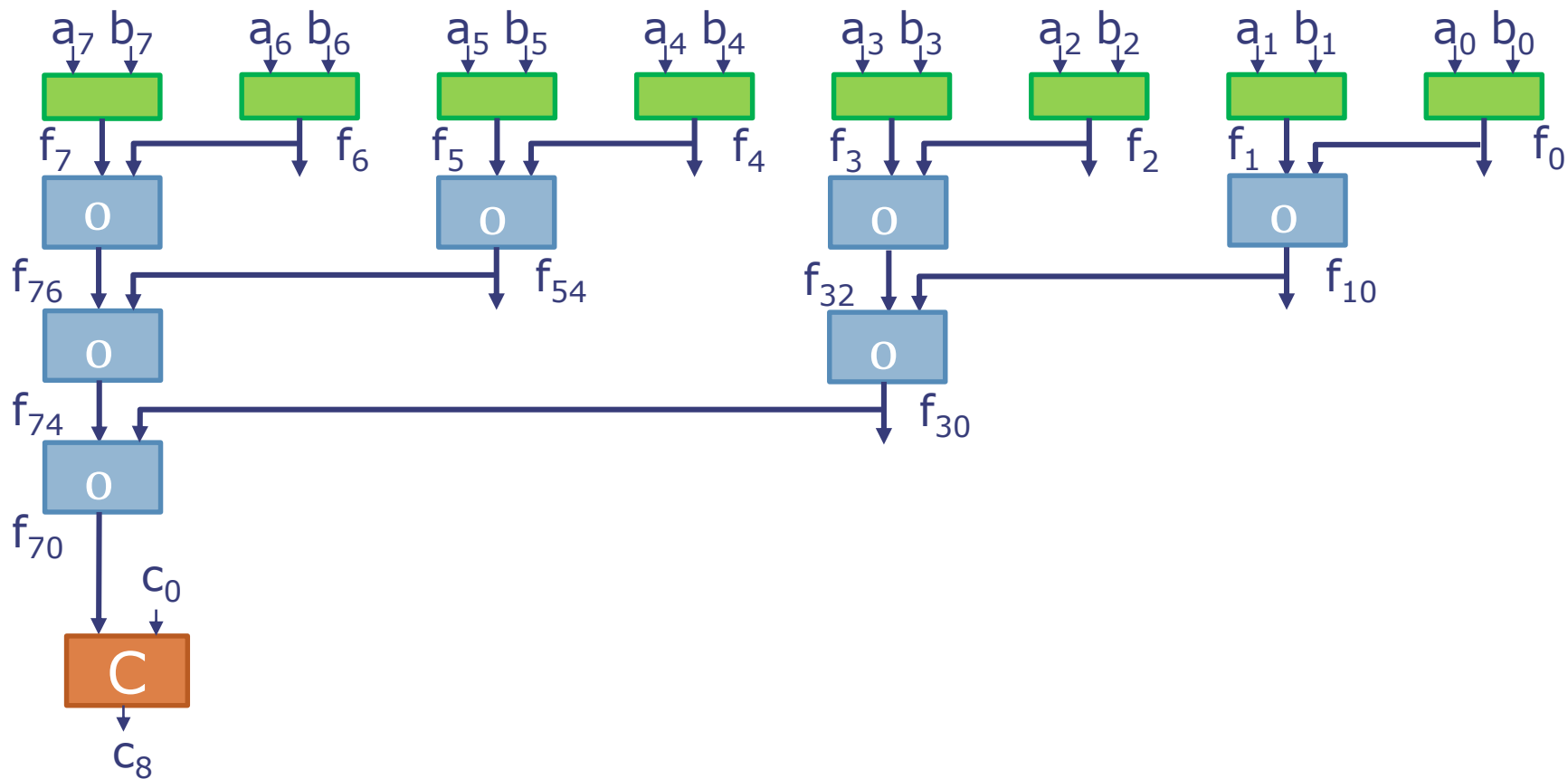


Step 1: Generating the output carry

Putting it all together

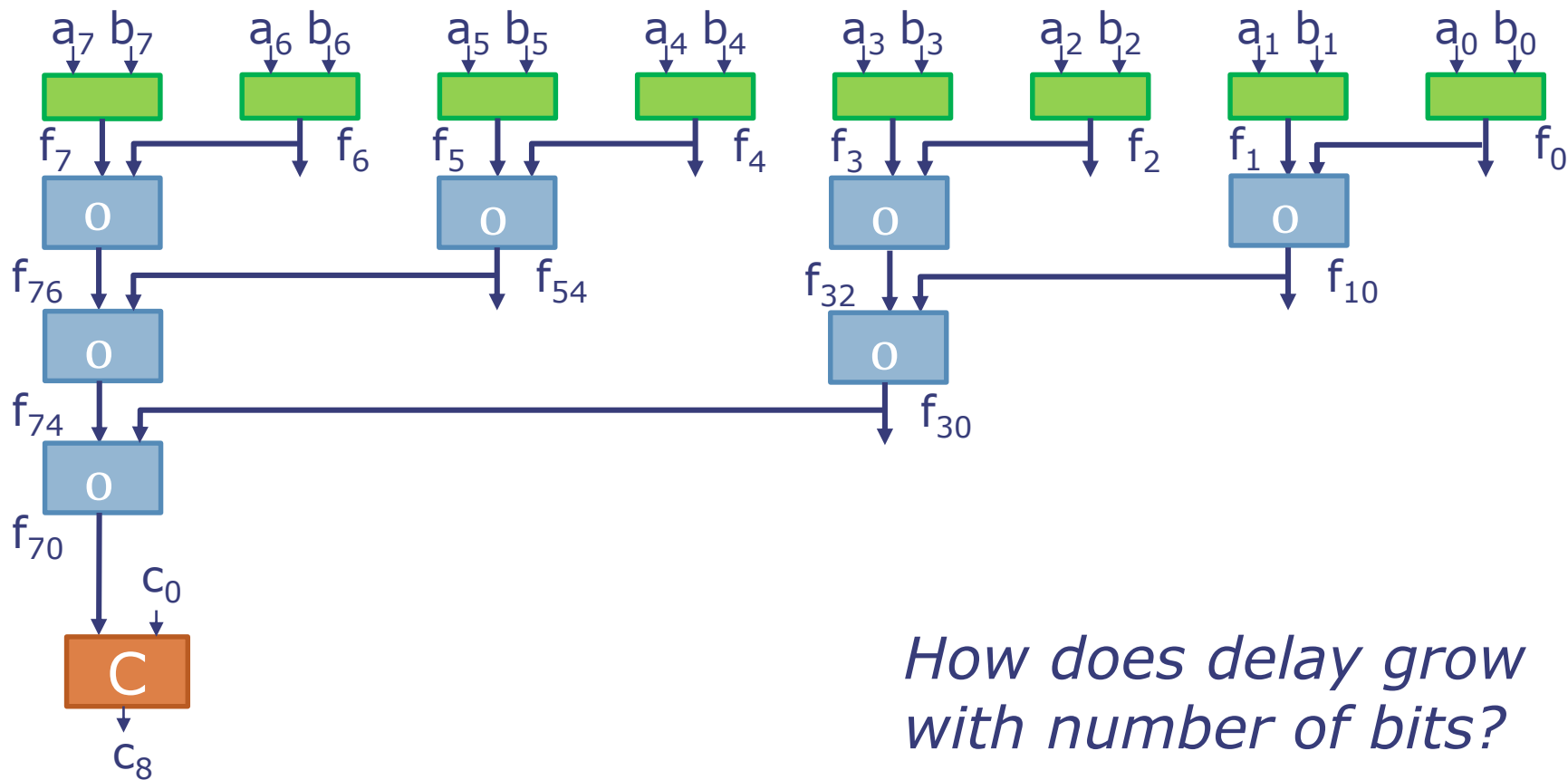

Step 1: Generating the output carry

Putting it all together

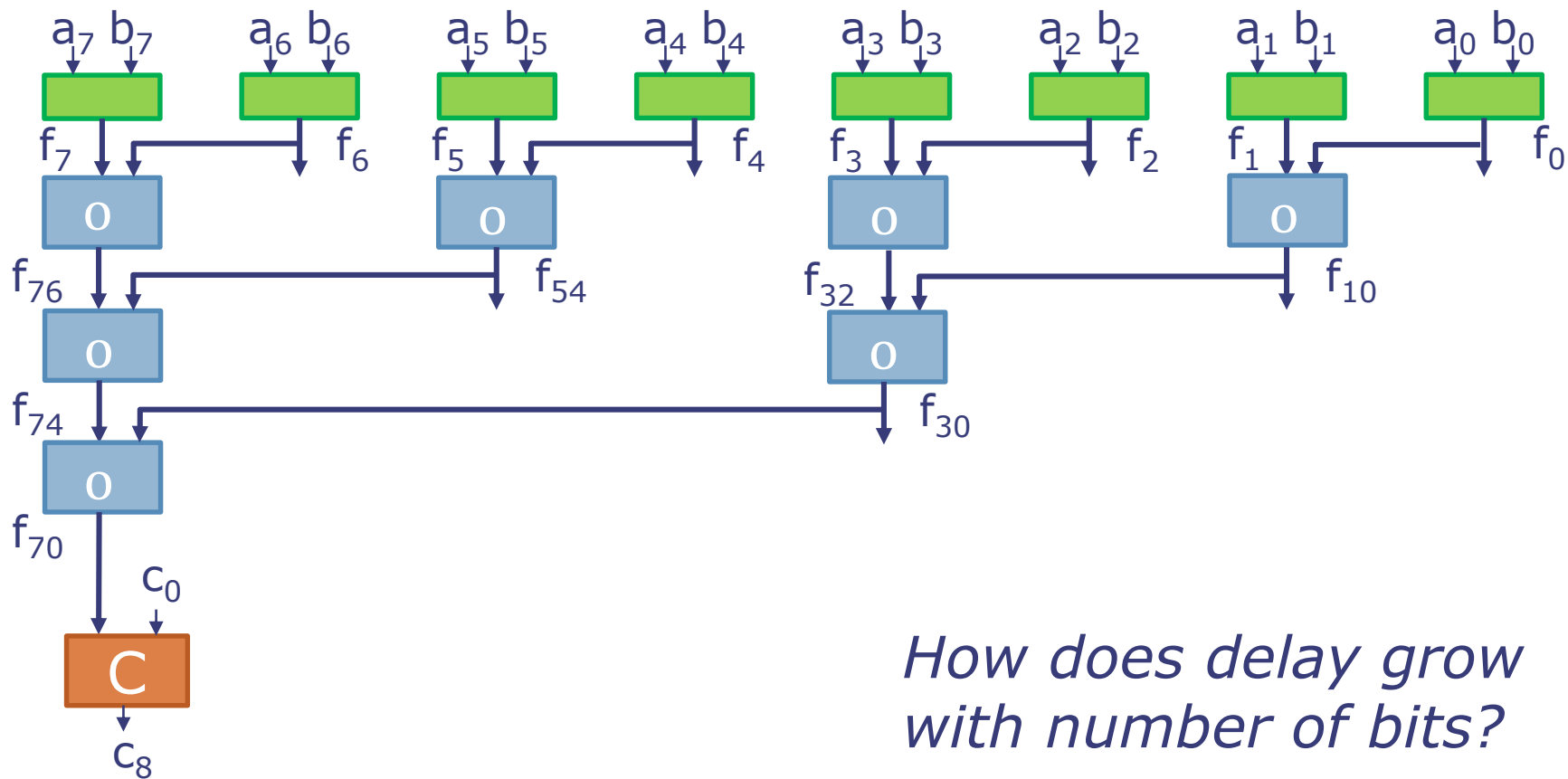


How does delay grow with number of bits?

$\Theta(\log n)$

Step 1: Generating the output carry

Putting it all together

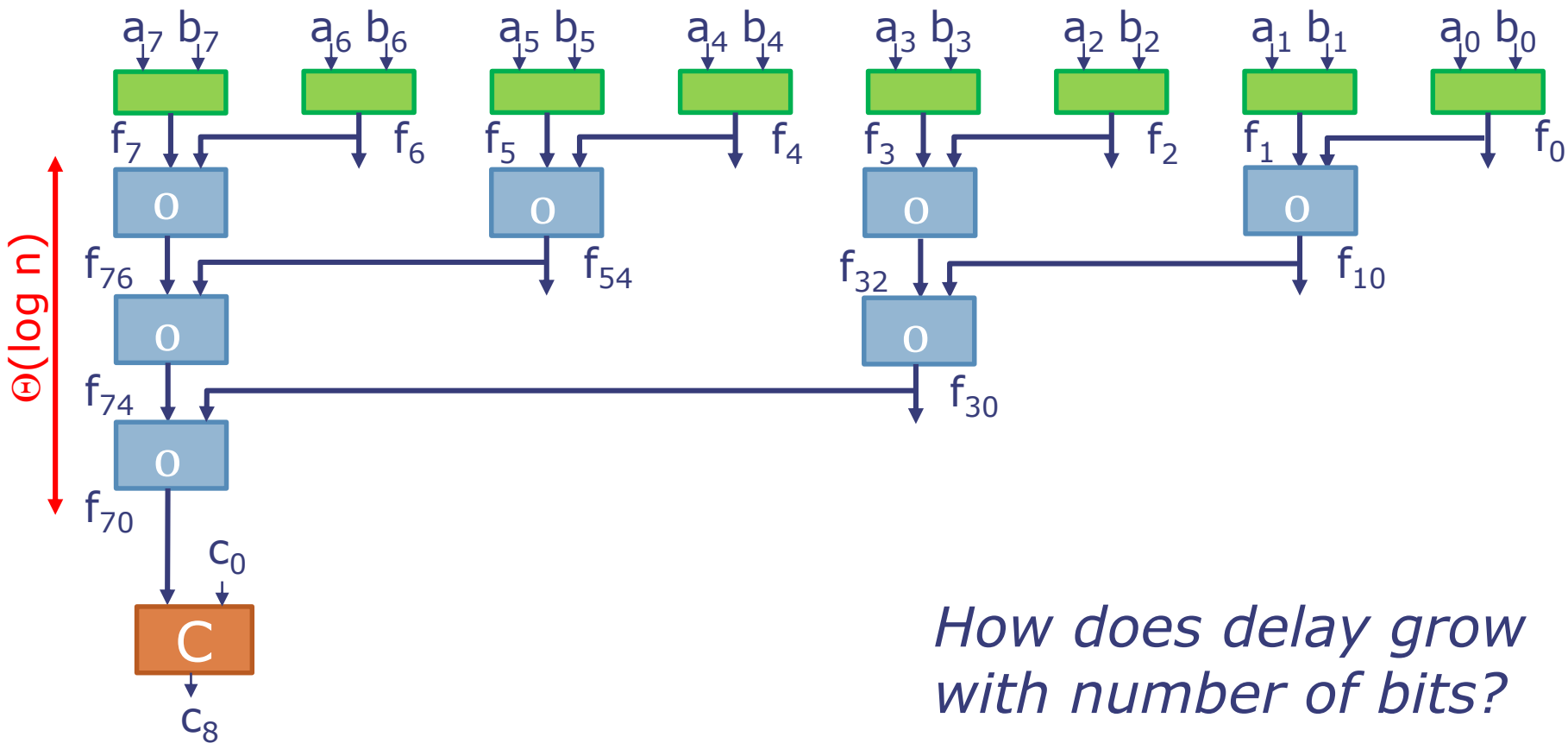

$\Theta(\log n)$


Step 2: Generating all carries

- So far we have seen how to generate a single output carry, but we need all intermediate ones too
- This is a specific application of the parallel scan (a.k.a. parallel prefix) algorithm


Step 2: Generating all carries

- So far we have seen how to generate a single output carry, but we need all intermediate ones too
- This is a specific application of the parallel scan (a.k.a. parallel prefix) algorithm
- Two main options:
 - Brent-Kung CLA: Low area but some extra delay
 - Kogge-Stone CLA: High area but lower delay


Option 1: Brent-Kung CLA

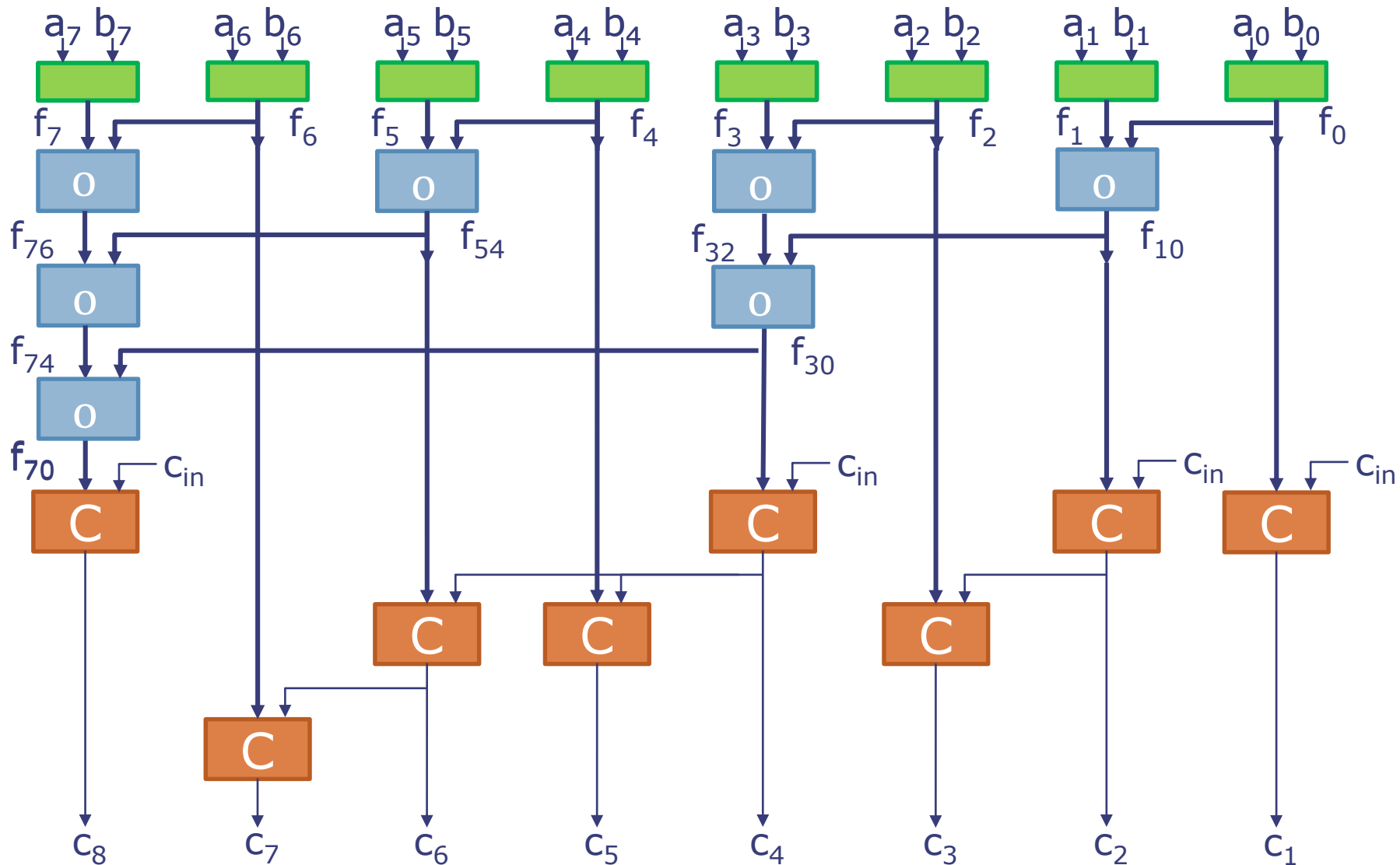


Option 1: Brent-Kung CLA

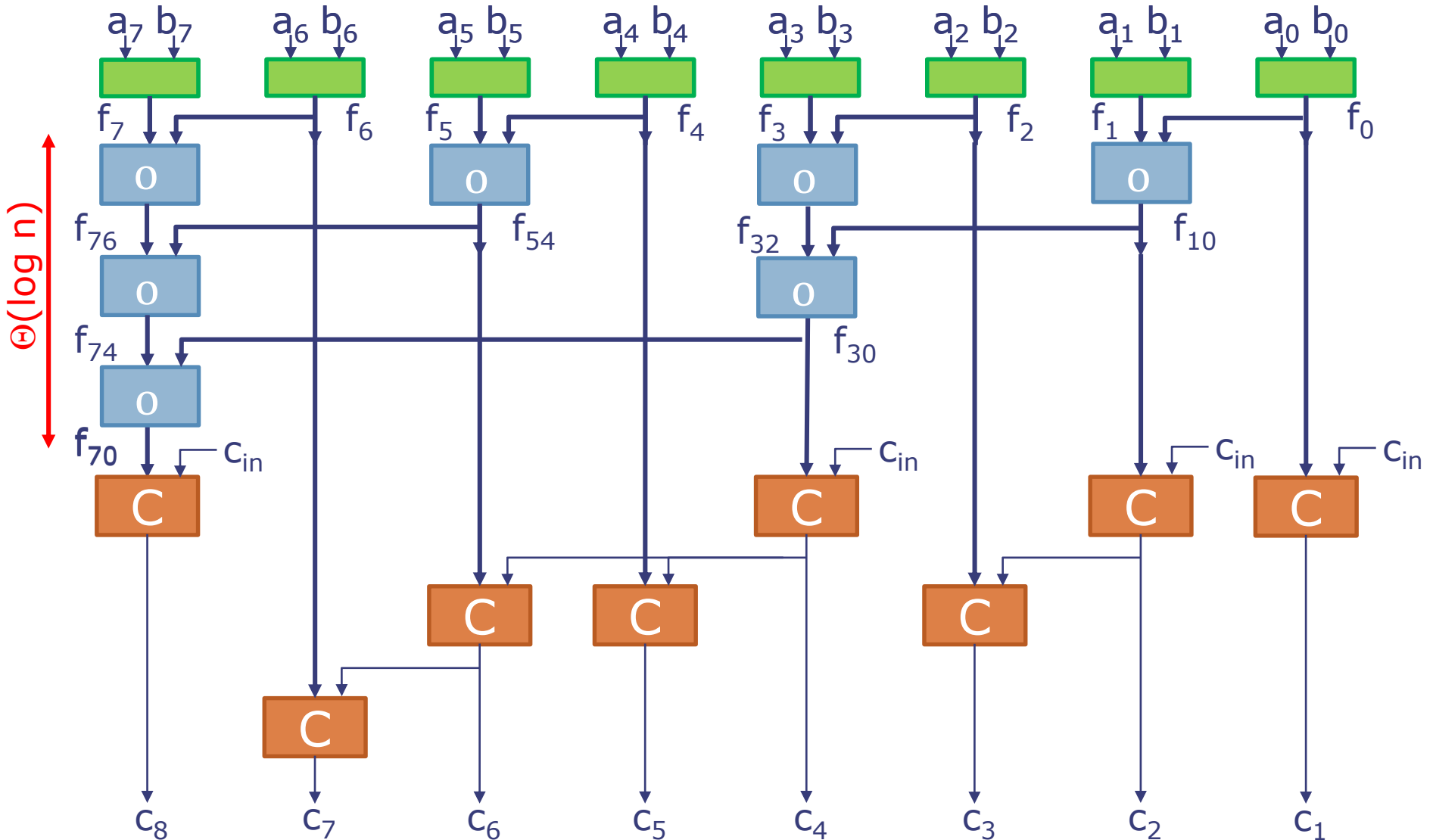


Option 1: Brent-Kung CLA

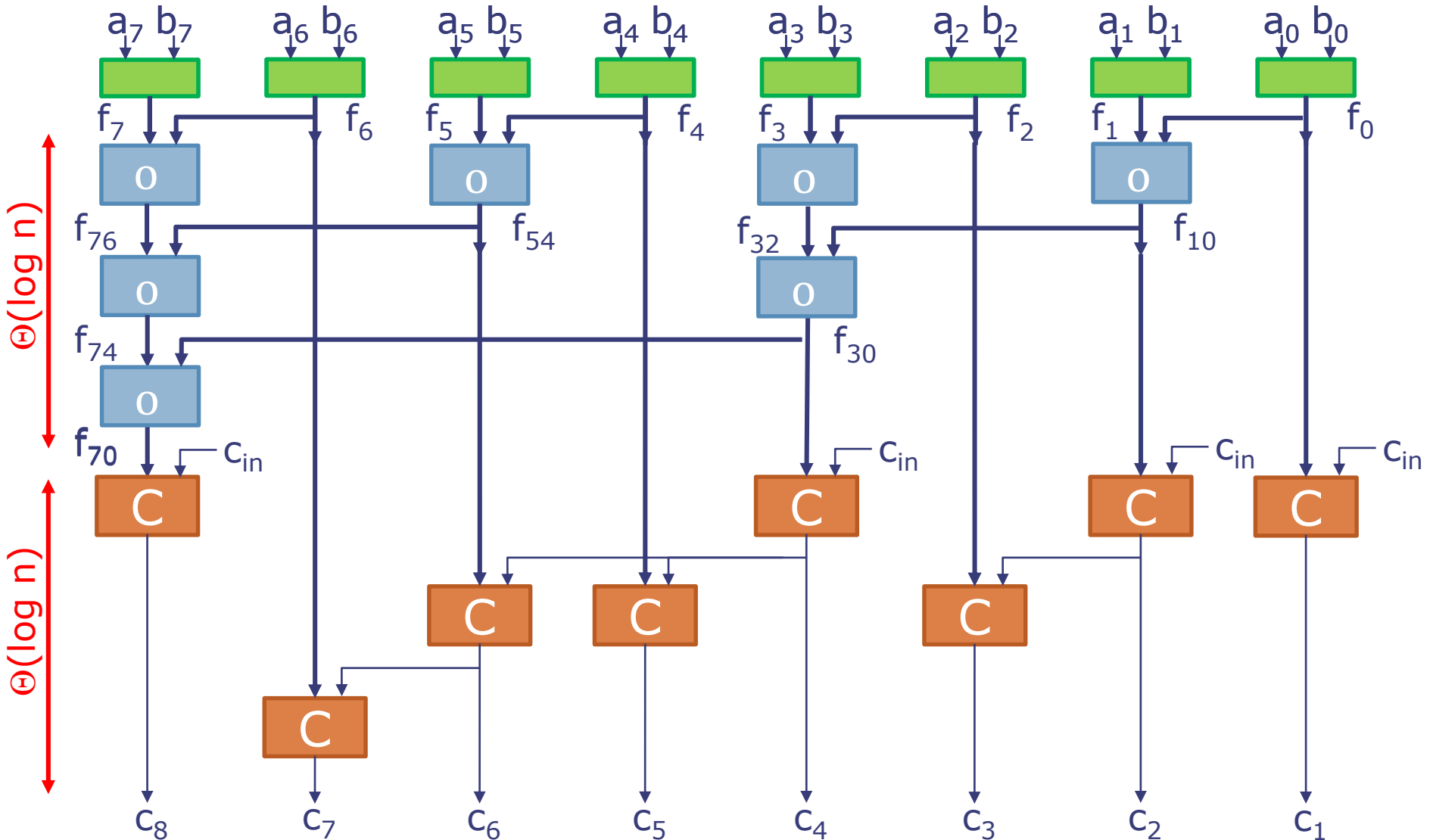


Option 2: Kogge-Stone CLA

 

Option 2: Kogge-Stone CLA

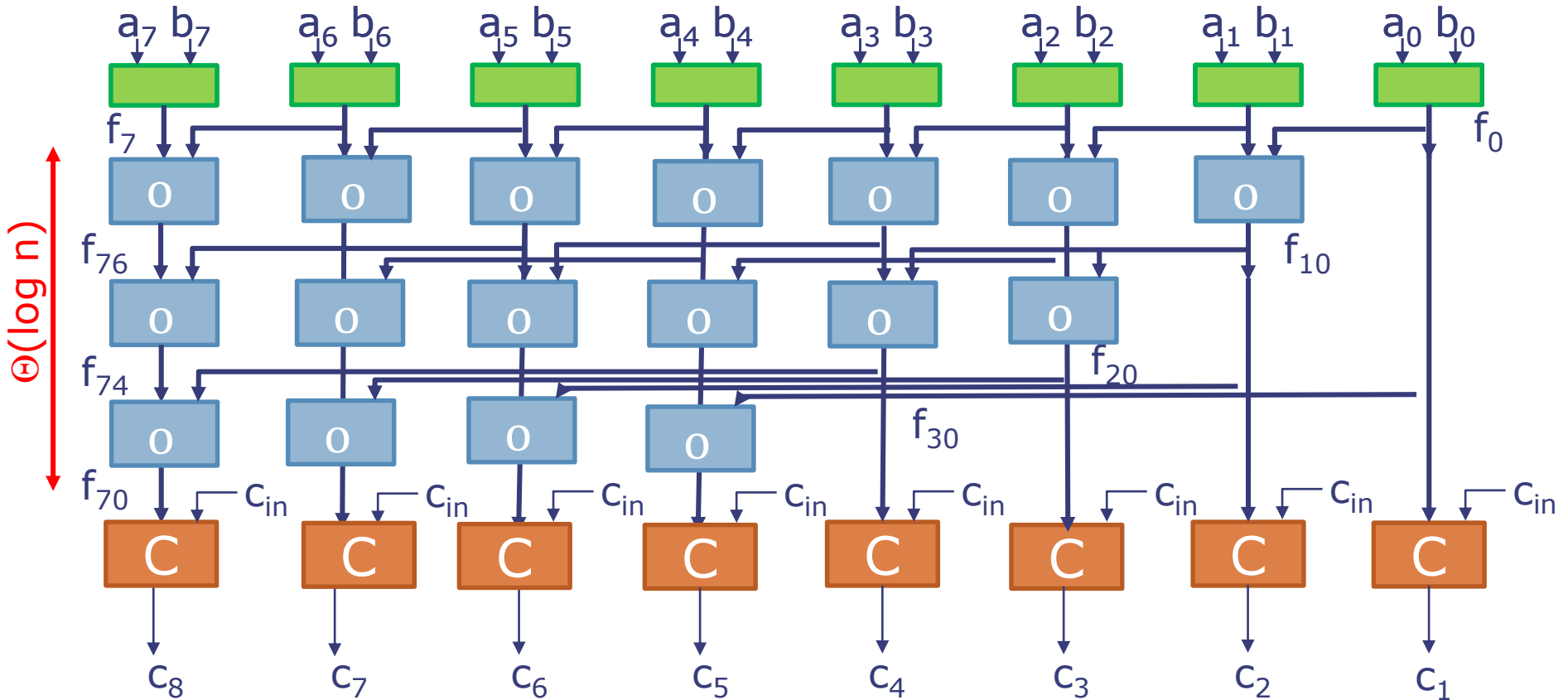

Option 2: Kogge-Stone CLA

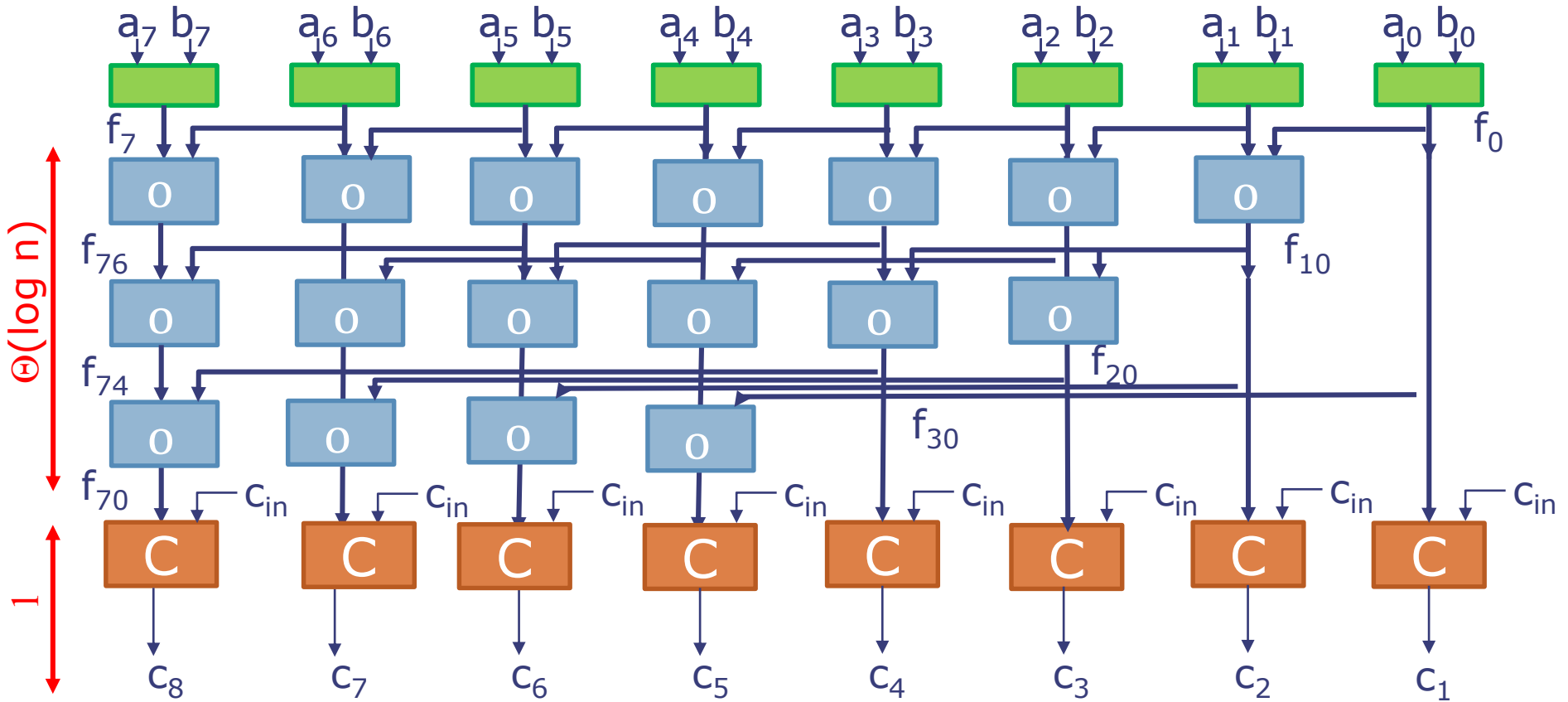

CLA Nitty-Gritty: Choosing a good encoding for functions

- CLAs need to encode three possible functions: kill, propagate, generate (invert is not used)
- 2-bits required per function, but 3 values, so how they are encoded can affect logic cost

CLA Nitty-Gritty: Choosing a good encoding for functions

- CLAs need to encode three possible functions: kill, propagate, generate (invert is not used)
- 2-bits required per function, but 3 values, so how they are encoded can affect logic cost
- A common encoding is $f = \{g, p\}$, where:
 - $g = ab$ (generate bit)
 - $p = a+b$ (propagate bit)


CLA Nitty-Gritty: Choosing a good encoding for functions

- CLAs need to encode three possible functions: kill, propagate, generate (invert is not used)
- 2-bits required per function, but 3 values, so how they are encoded can affect logic cost
- A common encoding is $f = \{g, p\}$, where:
 - $g = ab$ (generate bit)
 - $p = a+b$ (propagate bit)
- With this encoding,
 - $g = 0, p = 0 \rightarrow \text{kill}$
 - $g = 0, p = 1 \rightarrow \text{propagate}$
 - $g = 1, p = X \rightarrow \text{generate}$

CLA Building Blocks

with $f = \{g, p\}$ encoding

- Produce initial f signals

 

$$g = ab$$
$$p = a+b$$


CLA Building Blocks

with $f = \{g, p\}$ encoding

- Produce initial f signals



- Compose f signals

 


CLA Building Blocks

with $f = \{g, p\}$ encoding


- Produce initial f signals



- Compose f signals

 

- Produce individual carries

 

Carry-Lookahead Adder Takeaways

- There are many CLA designs
 - We've seen Brent-Kung and Kogge-Stone CLAs
 - Some other types

Carry-Lookahead Adder Takeaways

- There are many CLA designs
 - We've seen Brent-Kung and Kogge-Stone CLAs
 - Some other types
 - Different variants for each type, e.g., using higher-radix trees to reduce depth

Carry-Lookahead Adder Takeaways

- There are many CLA designs
 - We've seen Brent-Kung and Kogge-Stone CLAs
 - Some other types
 - Different variants for each type, e.g., using higher-radix trees to reduce depth
- This technique is useful beyond adders: computes any one-dimensional recurrence in $\Theta(\log n)$ delay
 - e.g., comparators, priority encoders, etc.

Summary

- Parametric functions let us write a generic description of a function that is then instantiated on demand
- Use for loops and if-else statements with care: their similarity to software can be confusing and they can lead to poor circuits

Summary

- Parametric functions let us write a generic description of a function that is then instantiated on demand
- Use for loops and if-else statements with care: their similarity to software can be confusing and they can lead to poor circuits
- Choosing the right algorithms is crucial to design good digital circuits—tools can only do so much!
- Carry-select and carry-lookahead adders achieve $\Theta(\log n)$ delay, but at the cost of extra area

Thank you!

Next lecture: Sequential Circuits