

6.004 Worksheet Questions
L14 – RISC-V Processor

Single-Cycle RISC-V Processor

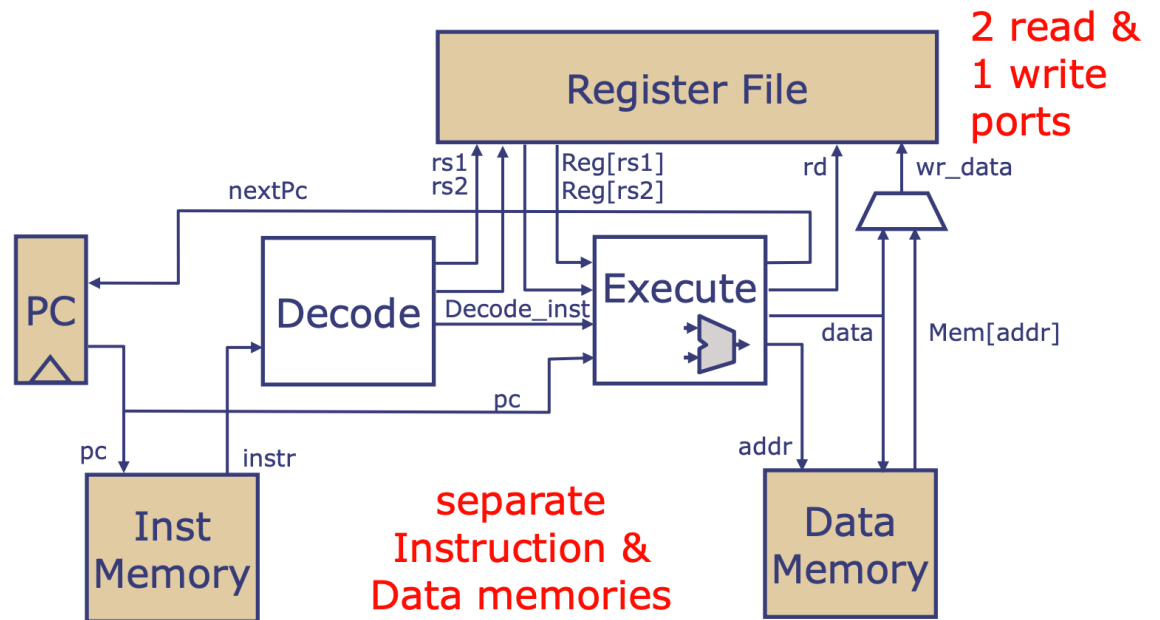


Diagram 1: Abstract Version

- Contains all major components: PC Register, Instruction and Data memories, Decode logic, Execute logic (including the ALU), and Register file
- Skips some details in the wiring of signals to increase readability

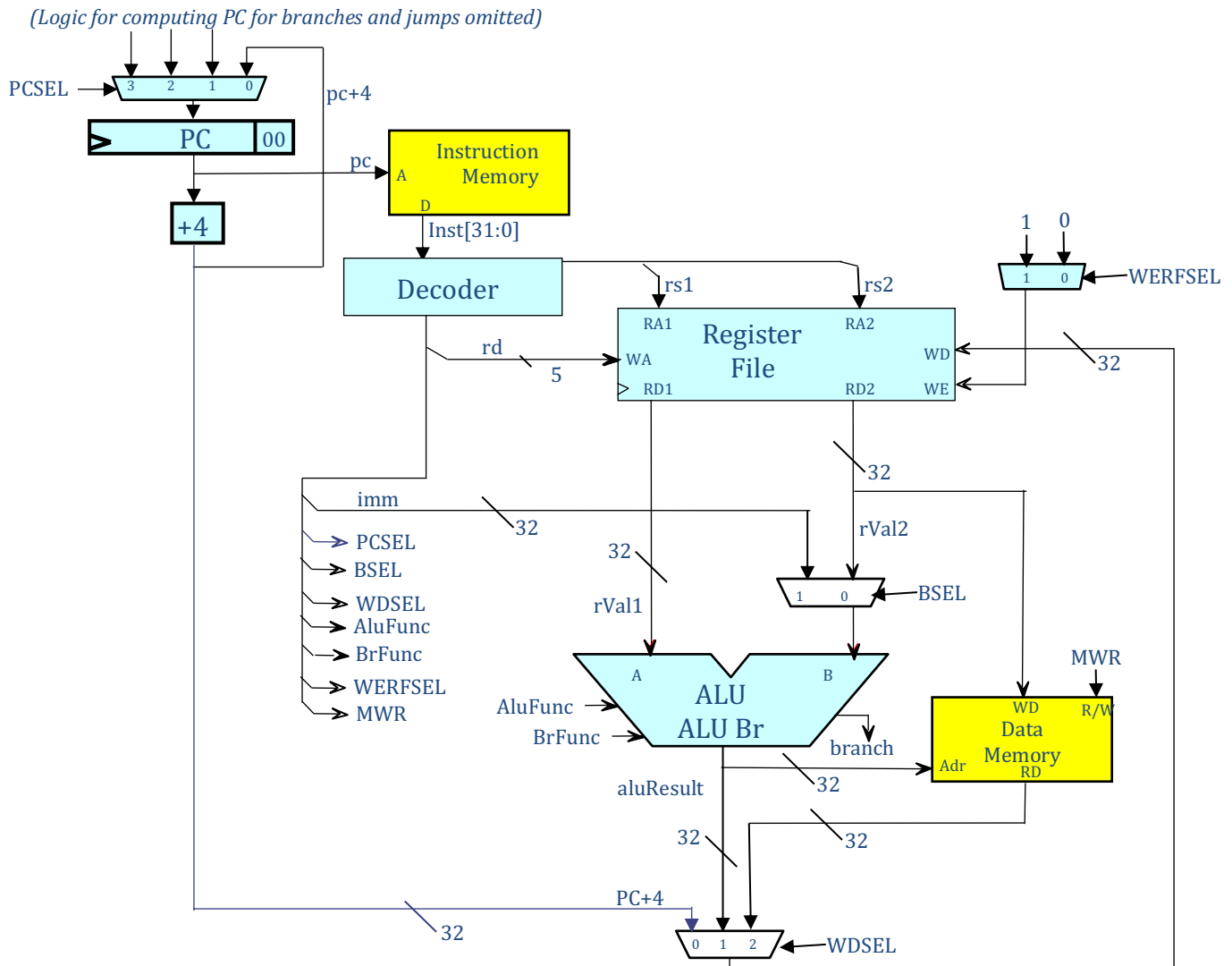


Diagram 2: Detailed Version

- Also contains all of the major components, as well as additional details like muxes on inputs, descriptions of various signal contents and bit widths
- Both diagrams are equivalent! Differ only in level of detail

RISC-V Processor: Components

Refer to the 6.004 ISA Reference Tables (Website > Resources) for details about each instruction.

ProcTypes

```
typedef Bit#(32) Word;

// Branch function enumeration
typedef enum {
    Eq,
    Neq,
    Lt,
    Ltu,
    Ge,
    Geu,
    Dbr
} BrFunc;

typedef enum {
    OP,
    OPIMM,
    BRANCH,
    LUI,
    JAL,
    JALR,
    LOAD,
    STORE,
    AUIPC,
    Unsupported
} IType;

// Return type for decode()
typedef struct {
    IType iType;
    AluFunc aluFunc;
    BrFunc brFunc;
    Maybe#(RIndx) dst;
    RIndx src1;
    RIndx src2;
    Word imm;
} DecodedInst;

// Register Index Type
typedef Bit#(5) RIndx;

// Register File writes
typedef struct {
    RIndx index;
    Word data;
} RegWriteArgs;

// Return type for execute()
typedef struct {
    IType iType;
    Maybe#(RIndx) dst;
    Word data;
    Word addr;
    Word nextPc;
} ExecInst;

// Memory writes
typedef struct {
    Word addr;
    Word data;
} MemWriteReq;
```

Decode

```
function DecodedInst decode(Bit#(32) inst);
    let opcode = inst[6:0];
    let funct3 = inst[14:12];
    let funct7 = inst[31:25];
    let dst     = inst[11:7];
    let src1    = inst[19:15];
    let src2    = inst[24:20];

    Maybe#(RIndx) validDst = Valid(dst);
    Maybe#(RIndx) dDst = Invalid; // default value
    RIndx dSrc = 5'b0;

    // DEFAULT VALUES - Use the following for your default values:
    // dst: dDst, src1: dSrc, src2: dSrc, imm: immD, BrFunc: Dbr, AluFunc: ?

    // We have provided a default value and done immB for you.
    Word immD32 = signExtend(1'b0); // default value
    Bit#(12) immB = { inst[31], inst[7], inst[30:25], inst[11:8] };
    Word immB32 = signExtend({immB, 1'b0});
    Bit#(20) immU = 0; // TODO
    Word immU32 = 0; // TODO
    Bit#(12) immI = 0; // TODO
    Word immI32 = 0; // TODO
    Bit#(20) immJ = 0; // TODO
    Word immJ32 = 0; // TODO
    Bit#(12) immS = 0; // TODO
    Word immS32 = 0; // TODO

    DecodedInst dInst = unpack(0);
    dInst.iType = Unsupported; // unsupported by default

    case (opcode)
        opAuipc: begin
            dInst = DecodedInst {
                iType: AUIPC,
                dst: validDst,
                src1: dSrc,
                src2: dSrc,
                imm: immU32,
                brFunc: Dbr,
                aluFunc: ?
            };
        end
        opLui: // TODO
```

Decode (continued)

```
    opOpImm: begin
        dInst.iType = OPIMM;
        dInst.src1  = src1;
        dInst.imm   = immI32;
        dInst.dst   = validDst;

        case (funct3)
            fnAND : dInst.aluFunc = And; // Decode ANDI instructions
            fnOR  : dInst.iType = Unsupported; // TODO
            fnXOR : dInst.iType = Unsupported; // TODO
            fnADD : dInst.iType = Unsupported; // TODO
            fnSLT : dInst.iType = Unsupported; // TODO
            fnSLTU: dInst.iType = Unsupported; // TODO
            fnSLL : case (funct7)
                7'b0000000: dInst.aluFunc = Sll;
                // Otherwise we must say the instruction is invalid:
                default:    dInst.iType = Unsupported;
            endcase
            fnSR  : // TODO
                dInst.iType = Unsupported;
                default: dInst.iType = Unsupported;
        endcase
    end
    opOp: // TODO
    opBranch: // TODO
    opJal: // TODO
    opLoad: // TODO
    opStore: // TODO
    opJalr: // TODO
endcase
return dInst;
endfunction
```

Execute

```
function ExecInst execute(DecodedInst dInst, Word rVal1, Word rVal2, Word pc);
    let imm = dInst.imm;
    let brFunc = dInst.brFunc;
    let aluFunc = dInst.aluFunc;
    let aluVal2 = dInst.iType == OPIMM ? imm : rVal2;

    Word data = case (dInst.iType)
        AUIPC:    pc + imm;
        LUI:      0; // TODO
        OP, OPIMM: 0; // TODO
        JAL, JALR: 0; // TODO
        STORE:    0; // TODO
        default:  0;
    endcase;

    Word nextPc = case (dInst.iType)
        BRANCH: 0; // TODO Replace 0 with the correct expression
        JAL:     0; // TODO Replace 0 with the correct expression
        JALR: (rVal1 + imm) & ~1; // "& ~1" clears the bottom bit.
        default: pc + 4;
    endcase;

    Word addr = 0; // TODO Replace 0 with the correct expression

    return ExecInst{iType: dInst.iType, dst: dInst.dst, data: data,
                    addr: addr, nextPc: nextPc};
endfunction
```

Processor

```
module Processor;
    Reg#(Word) pc(0);
    RegisterFile rf;
    MagicMemory iMem; // Memory for loading instructions
    MagicMemory dMem; // Memory for loading and storing data

    rule doSingleCycle;
        // Load the instruction from instruction memory (iMem)
        Word inst = 0; // TODO

        // Decode the instruction
        DecodedInst dInst = unpack(0); // TODO

        // Read the register values used by the instruction
        Word rVal1 = 0; // TODO
        Word rVal2 = 0; // TODO

        // Compute all outputs of the instruction
        ExecInst eInst = unpack(0); // TODO

        if (eInst.iType == LOAD) begin
            // TODO: Load from data memory (dMem) if needed
        end else if (eInst.iType == STORE) begin
            // TODO: Store to data memory (dMem) if needed
        end

        if (isValid(eInst.dst)) begin
            // TODO: Write to a register if the instruction requires it
        end

        // TODO: Update pc to the next pc
    endrule
endmodule
```

Problem 1

Decode the following 32-bit RISC-V instructions:

1. 0100000 00001 00100 000 00011 0110011

2. 0100000 00101 00010 101 00111 0010011

Problem 2 ★

The RISC-V LUI instruction, Load Upper Immediate, loads a 20-bit immediate into the upper 20 bits of the specified destination register (and sets the lower 12 bits to zero). What modifications to the processor datapath are needed to implement the LUI instruction?

Problem 3 ★

We want to add the following instruction to the RISC-V ISA:

```
cmvz rd, rs1, rs2
```

This new `cmvz` instruction is a *conditional move*: it checks the contents of source register `rs1`, and if it's 0, copies the contents of source register `rs2` into `rd`. In other words:

```
if (reg[rs1] == 0) begin
    reg[rd] <= reg[rs2];
end
```

We would like to update the hardware diagram of the single-cycle processor to support this new instruction, reusing the existing **branch ALU** comparison logic to check if `rs1` is 0. In the diagram below, we have added extra inputs to the BSEL and WDSEL, and WERFSEL muxes to support reusing the branch ALU in this way.

Assume that when the decoder decodes CMVZ, it outputs `BrFunc = Eq`, `BSEL = 2`, `WDSEL = 3`, and `WERFSEL = 2`. It also outputs `PCSEL = 0` so that the next value of PC will be `PC + 4`.

- (a) For each of the missing mux inputs X, Y, and Z, write down either a constant or the name of a different wire or port in the processor hardware diagram that should be connected to each input, so that the processor executes CMVZ correctly.

X: _____

Y: _____

Z: _____

- (b) We would like to check that our processor can still decode and execute the old RISC-V instructions correctly. Suppose the processor is decoding an OPIMM instruction, such as ADDI. For each of the select signals we changed (shown in **bold** in the diagram), write down the correct signals that the decoder should produce for such an instruction.

Decoded value of BSEL: _____

Decoded value of WDSEL: _____

Decoded value of WERFSEL: _____

Problem 4

(a) The RISC-V MUL instruction multiplies two 32-bit values together and places the **lower** 32 bits of the product in the destination register. It has an opcode of 7'b0110011, which is the same as the other OP type instructions, and a funct7 of 7'b0000001, and a funct3 of 3'b000. What changes to the processor datapath would be needed to support the MUL instruction? Use the combinational multiplier from Lecture 12.

(b) The RISC-V MULH instruction performs the same multiplication in (a), but returns the **upper** 32 bits of the product in the destination register. It has the same opcode and funct7 codes, but its funct3 is 3'b001. What modifications to 3(a) would be needed to support the MULH instruction?

Problem 5 ★

Add a branch if greater-than (BGT) instruction to the provided RISC-V processor. The instruction encoding should match other branch instructions, but have `funct3 = 3'b010`.

```
Bit#(7) opBranch = 7'b1100011;
```

```
_____ // TODO
```

```
function DecodedInst decode(Bit#(32) inst);
    let opcode = inst[6:0];
    let funct3 = inst[14:12];
    let funct7 = inst[31:25];
    let dst     = inst[11:7];
    let src1    = inst[19:15];
    let src2    = inst[24:20];

    Maybe#(RIdx) validDst = Valid(dst);
    Maybe#(RIdx) dDst = Invalid; // default value
    RIdx dSrc = 5'b0;

    // DEFAULT VALUES - Use the following for your default values:
    // dst: dDst, src1: dSrc, src2: dSrc, imm: immD, BrFunc: Dbr, AluFunc: ?

    // We have provided a default value and done immB for you.
    Word immD = signExtend(1'b0); // default value
    Word immB = 0; // TODO
    Word immU = 0; // TODO
    Word immI = 0; // TODO
    Word immJ = 0; // TODO
    Word immS = 0; // TODO

    DecodedInst dInst = unpack(0);
    dInst.iType = Unsupported; // unsupported by default

    case (opcode)
        Lots of omitted code from lab6

        _____: // TODO
            case (funct3): // TODO

                // Lots of omitted code from lab6
    endcase
    return dInst;
endfunction
```

```

// Branch function enumeration
typedef enum {Eq, Neq, Lt, Ltu, Ge, Geu, _____, Dbr} BrFunc; // TODO

function Bool aluBr(Word a, Word b, BrFunc brFunc);
    Bool res = case (brFunc)
        Eq:      (a == b);
        Neq:     (a != b);
        Lt:      signedLT(a, b);
        Ltu:     (a < b);
        Ge:      signedGE(a, b);
        Geu:     (a >= b);

        // TODO

        default: False;
    endcase;
    return res;
endfunction

```

Problem 6

Assume that `aluBr` has been replaced with the new branch ALU function, `newAluBr`, shown below. This new branch ALU is controlled by two control signals: `newBrFunc` and `negate`. When the result of this function is true, the next PC is going to be computed as `pc + imm`.

```
typedef enum {Eq, Lt, Ltu} NewBrFunc;
```

```
function Bool newAluBr(Word a, Word b, NewBrFunc newBrFunc, Bool negate);  
    Bool res = case (newBrFunc)  
        Eq:      (a == b);  
        Lt:      signedLT(a, b);  
        Ltu:     (a < b);  
    endcase;  
    return negate ? !res : res;  
endfunction
```

- A) Fill in the decoding table below to specify what the control signals should be for each `funct3`. Write an “X” in the table for entries that don’t matter. (Use the ISA [reference card](#) from the course website.)

funct3	newBrFunc	negate
3'b000		
3'b001		
3'b010		
3'b011		
3'b100		
3'b101		
3'b110		
3'b111		

Problem 7 (From Previous Quizzes)

Giuseppe is writing a large RISC-V assembly program, and is tired of getting confused by how to properly maintain the stack pointer **sp**. He's heard that other ISAs have **push** and **pop** instructions, which handle both allocating/freeing the space for a word on the stack, and storing it from/loading it to a register. Giuseppe decides that he'd like to implement them in the RISC-V ISA. Their syntaxes are as follows:

push rs2 pop rd

And the following is a Python-like description of how each works:

push:

```
reg[sp] = reg[sp] - 4
Mem[reg[sp]] = reg[rs2]
```

pop:

```
reg[rd] = Mem[reg[sp]]
reg[sp] = reg[sp] + 4
```

(A) (4 points) Giuseppe hopes to be able to simply add some new signals as inputs to the selection muxes in the existing RISC-V processor diagram. For each instruction being added, can this be done with **the existing processor components as described in lecture and shown on the following page? If not, describe the limitation that prevents it.**

(Label: 6A_push) Can push be implemented with existing components?

(Label: 6A_pop) Can pop be implemented with existing components?

Giuseppe's friend Jeffrey tells him that the **push** and **pop** instructions can cause issues when pipelining his processor later on. Giuseppe, knowing nothing about processor pipelining, decides to take his word for it and find a different solution to his problem.

His goal now is to remove a large amount of the uses of stack, so that he doesn't have as many opportunities to become confused. The main limitation that causes him to use the stack so much is that he's running out of registers to hold temporary values. In order to overcome this, he wants to combine multiple steps into a single instruction. In particular, he wants to combine the **ANDing** of two registers and **XORing** the result with an immediate into a single instruction. All immediates he uses are 10 bits or less, so he comes up with the following instruction syntax, definition, and encoding:

```
andxori:
    reg[rd] = ((reg[rs1] & reg[rs2]) ^ signExtend(imm))
```

31...25	24...20	19...15	14...12	11...7	6...0
imm[9:3]	rs2	rs1	imm[2:0]	rd	0110100

```
andxori x7, x1, x16, 0x1BC
```

In the diagram below, Giuseppe has decoded and sign extended the immediate used for the **andxori** instruction, labelling this signal **immA**. He also added an additional dedicated XOR module used in the instruction's computation. The output of this new XOR module is labelled **axRes**.

(C) (3 points) For each of the following signals, does the mux being controlled by that signal need an extra input to accommodate the new instruction? If so, indicate the name of **the signal that needs to be added as an input to the mux**. If not, indicate which existing value of **the mux control signal** is required to make the instruction work properly.

(Label: 6C_BSEL_1) BSEL: Needs new input? YES NO

(Label: 6C_BSEL_2) New input/Existing control signal: _____

(Label: 6C_WDSEL_1) WDSEL: Needs new input? YES NO

(Label: 6C_WDSEL_2) New input/Existing control signal: _____

(Label: 6C_WERFSEL_1) WERFSEL: Needs new input? YES NO

(Label: 6C_WERFSEL_2) New input/Existing control signal: _____

(D) (3 points) Additionally, decide for each of the following control signals what their values should be when executing the **andxori** instruction. If the value of the signal doesn't matter, then put N/A. The possible values for each signal are provided below.

AluFunc: Add, Sub, And, Or, Xor, Slt, Sltu, Sll, Srl, Sra

BrFunc: Eq, Neq, Lt, Ltu, Ge, Geu

MWR: Read, Write

(Label: 6D_alufunc) AluFunc: _____

(Label: 6D_brfunc) BrFunc: _____

(Label: 6D_mwr) MWR: _____

